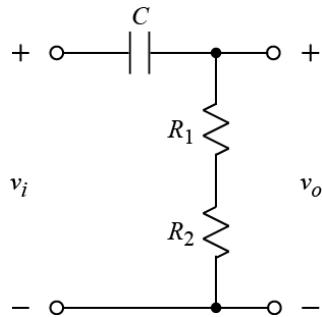


Ex:



$$R_1 = 120 \text{ k}\Omega \quad R_2 = 130 \text{ k}\Omega \quad C = 200 \text{ nF}$$

- a) Determine the transfer function V_o/V_i .
- b) Find ω such that $|V_o/V_i| = 1/\sqrt{2}$.
- c) Find ω such that $\angle V_o/V_i = 45^\circ$.
- d) Is it true that $\left| \frac{1}{j\omega C} \right| = |R_1 + R_2|$ at $\omega = \omega_C$?

sol'n: a) We need only combine R_1 and R_2 and treat this as a standard RC filter.

$$V_o = V_i \frac{R_1 + R_2}{R_1 + R_2 + \frac{1}{j\omega C}} \quad \text{V-divider}$$

$$H(j\omega) = \frac{V_o}{V_i} = \frac{R_1 + R_2}{R_1 + R_2 + \frac{1}{j\omega C}}$$

It is convenient, when finding cutoff frequencies, to write $H(j\omega)$ in the following form:

$$H(j\omega) = k \frac{1}{1 + jX} \quad \begin{matrix} \text{where } k \text{ is real} \\ \text{and constant} \\ \text{and } X \text{ is real} \end{matrix}$$

We obtain the desired form by dividing the top and bottom by $R_1 + R_2$.

$$H(j\omega) = \frac{1}{1 + \frac{1}{j\omega(R_1 + R_2)C}} = \frac{1}{1 + \frac{1}{j\omega 250k 200n}}$$

$$H(j\omega) = \frac{1}{1 - j \frac{1}{\omega(R_1 + R_2)C}} = \frac{1}{1 - j \frac{20}{\omega}}$$

b) To obtain $\left| \frac{V_o}{V_i} \right| = \sqrt{2}$ from the

above formula, we observe that
 $|1 \pm j| = \sqrt{2}$, (i.e., $|1 \pm j| = \sqrt{1^2 + 1^2}$)

Here, we have $H(j\omega) = \frac{1}{1 - jX}$
 where $X = \frac{1}{\omega(R_1 + R_2)C}$.

The sol'n we seek is where

$$X = 1.$$

$$\text{Thus, } \frac{1}{\omega(R_1 + R_2)C} = 1,$$

$$\text{or } \omega = \frac{1}{(R_1 + R_2)C} = 20 \text{ r/s}$$


This is just the calculation of the cutoff frequency.

c) $\angle(V_o/V_i) = \angle V_o - \angle V_i$ always.

Here $\angle\left(\frac{V_o}{V_i}\right) = \angle H(j\omega) = \angle 1 - jX$
 where $X = \frac{1}{\omega(R_1 + R_2)C}$ is real.

Now, $\angle 1 = 0^\circ$ since 1 is a real number.

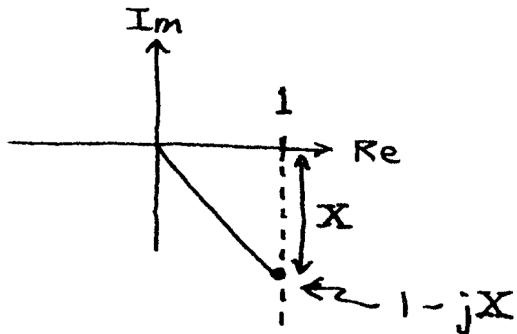To understand $\angle 1 - jX$, we may use a graph of $1 - jX$:



We want $\angle H(j\omega) = 45^\circ = 0^\circ - \angle(1 - jX)$

So we want $\angle(1 - jX) = -45^\circ$.

Thus, we want $X = 1$ since

$$\angle 1 - j = -45^\circ$$

$$\text{So } X \equiv \frac{1}{\omega(R_1 + R_2)C} = 1$$

This is the same problem as in (b).

$$\omega = \frac{1}{(R_1 + R_2)C}, \text{ (which is cutoff freq)}$$

$$\omega = 20 \text{ r/s}$$

$$d) \quad \left| \frac{1}{j\omega C} \right| = \frac{1}{|j\omega C|} = \frac{1}{\omega C}$$

$$|R_1 + R_2| = R_1 + R_2$$

$$\text{So } \frac{1}{\omega C} = R_1 + R_2$$

$$\text{or } \omega = \frac{1}{(R_1 + R_2)C} = 20 \text{ r/s}$$

This is indeed the same as ω_d .