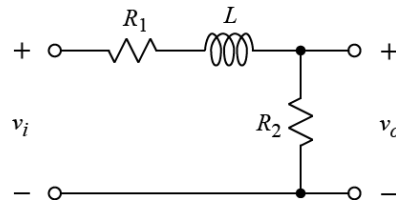


Ex:



$$R_1 = 150 \, \Omega \quad R_2 = 750 \, \Omega \quad L = 1 \, \mu\text{H}$$

- Determine the transfer function V_o/V_i . **Hint:** switch the order of R_1 and L and use a voltage divider.
- Express the maximum of $|V_o/V_i|$ as a function of R_1 and R_2 .

sol'n: a) If we ignore the hint, we have the following calculation:

$$H(j\omega) = \frac{V_o}{V_i} = \frac{V_i}{V_i} \frac{R_2}{R_1 + R_2 + j\omega L}$$

Putting this in the form $H(j\omega) = k \frac{1}{1 \pm jX}$

is achieved by factoring out R_2 from the numerator and $R_1 + R_2$ from the denominator.

$$H(j\omega) = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + j \frac{\omega L}{R_1 + R_2}}$$


$$\text{So } k = \frac{R_2}{R_1 + R_2} \quad \text{and } X = \frac{\omega L}{R_1 + R_2}.$$

$$k = \frac{750 \, \Omega}{150 + 750 \, \Omega} = \frac{5}{6}$$

$$X = \frac{\omega \, 1 \, \mu}{150 + 750 \, \Omega} = \frac{\omega}{900 \, \text{Mr/s}}$$

$$H(j\omega) = \frac{5}{6} \frac{1}{1 + j \frac{\omega}{900 \text{ Mr/s}}}$$

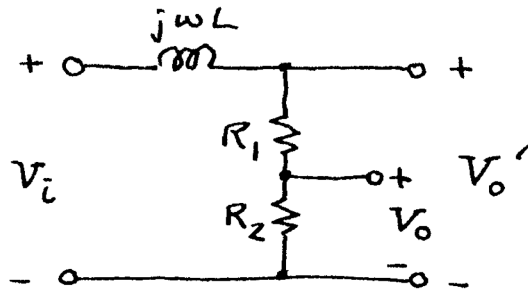If we use the hint, we view the filter as an RL filter, (with $R = R_1 + R_2$), and a V divider:



We have filter transfer function:

$$H'(j\omega) \equiv \frac{V_o'}{V_i} = \frac{R_1 + R_2}{R_1 + R_2 + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R_1 + R_2}}$$

We multiply this by a voltage-divider gain term to our desired $H(j\omega)$:

$$V_o = V_o' \cdot \frac{R_2}{R_1 + R_2}$$

$$\text{or } \frac{V_o}{V_o'} = \frac{R_2}{R_1 + R_2}$$


$$\text{So } H(j\omega) = \frac{V_o}{V_i} = \frac{V_o}{V_o'} \cdot \frac{V_o'}{V_i}$$

$$\text{or } H(j\omega) = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + j\omega \frac{L}{R_1 + R_2}}$$

$$H(j\omega) = \frac{5}{6} \frac{1}{1 + j \frac{\omega}{900 \text{ Mr/s}}}$$

$$\begin{aligned} \text{b) } \max_{\omega} \left| \frac{V_o}{V_i} \right| &\equiv \max_{\omega} |H(j\omega)| \\ &= \frac{5}{6} \max_{\omega} \left| \frac{1}{1 + j \frac{\omega}{900 \text{ Mr/s}}} \right| \\ &= \frac{5}{6} \max_{\omega} \frac{1}{\left| 1 + j \frac{\omega}{900 \text{ Mr/s}} \right|} \\ &= \frac{5}{6} \frac{1}{\min_{\omega} \left| 1 + j \frac{\omega}{900 \text{ Mr/s}} \right|} \end{aligned}$$

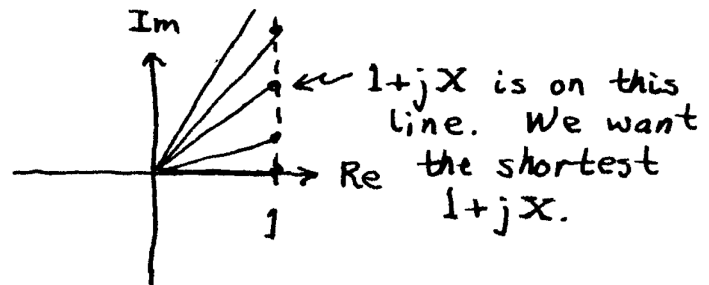We observe that X ranges from 0 to ∞ as ω ranges from 0 to ∞ .



The shortest $1 + jX$ is $1 + j0$, with $|1 + j0| = 1$.

$$\text{So } \max_{\omega} \left| \frac{V_o}{V_i} \right| = \frac{5}{6} \frac{1}{1} = \frac{5}{6} = \frac{R_2}{R_1 + R_2}$$