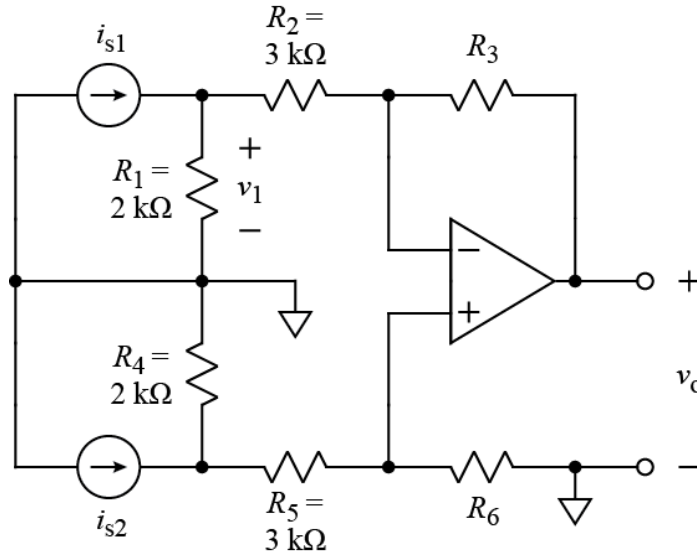


Ex:




- a) The above circuit operates in linear mode. Derive a symbolic expression for v_o . The expression must contain not more than the parameters i_{s1} , i_{s2} , R_1 , R_2 , R_3 , R_4 , R_5 , and R_6 .
- b) Assuming $R_1 = R_4$, $R_2 = R_5$, and $R_3 = R_6$ derive a symbolic expression for v_o in terms of common mode and differential input voltages:

$$i_{cm} \equiv \frac{(i_{s2} + i_{s1})}{2} \quad \text{and} \quad i_{dm} \equiv i_{s2} - i_{s1}$$

The expression must contain not more than the parameters i_{cm} , i_{dm} , R_1 , R_2 , and R_3 . Write the expression as i_{cm} times a term plus i_{dm} times a term.

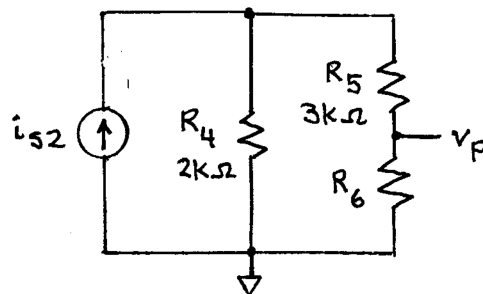sol'n: a) First, we find the voltage, v_p , at the + input of the op-amp. The circuit for finding v_p may be drawn as shown below.




Using the i -divider formula, we find the current flowing through R_5 and R_6 . We multiply this current by R_6 to get v_p :

$$v_p = i_{s2} \frac{R_4}{R_4 + R_5 + R_6} \cdot R_6$$

Second, we set the voltage, v_n , at the $-$ input of the op-amp equal to v_p .

$$v_n = v_p = i_{s2} \frac{R_4 R_6}{R_4 + R_5 + R_6}$$

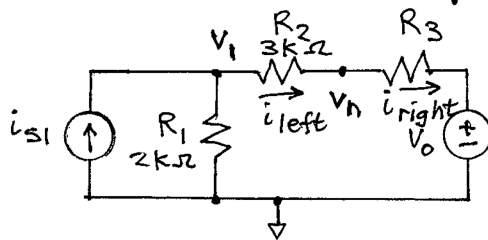Third, we find an expression for the current i_{left} flowing toward the $-$ input of the op-amp from the left. (This current is the current in R_2 measured with the arrow pointing to the right.) We also make sure that we use v_n in the expression for i_{left} .



using node-voltage to find v_1 , we have

$$-i_{s1} + \frac{v_1}{R_1} + \frac{v_1 - v_n}{R_2} = 0A$$

or

$$v_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = i_{s1} + \frac{v_n}{R_2}$$

or

$$v_1 = \left(i_{s1} + \frac{v_n}{R_2} \right) R_1 \parallel R_2$$

The value of i_{left} will be

$$\begin{aligned}i_{\text{left}} &= \frac{v_1 - v_n}{R_2} = \left(i_{s1} + \frac{v_n}{R_2} \right) \frac{R_1 \parallel R_2 - v_n}{R_2} \\&= i_{s1} \frac{R_1}{R_1 + R_2} + \frac{v_n}{R_2} \left(\frac{R_1}{R_1 + R_2} - 1 \right) \\&= i_{s1} \frac{R_1}{R_1 + R_2} + \frac{v_n}{R_2} \left(\frac{R_1}{R_1 + R_2} - \frac{R_1 + R_2}{R_1 + R_2} \right) \\&= i_{s1} \frac{R_1}{R_1 + R_2} - \frac{v_n}{R_1 + R_2}\end{aligned}$$

Note: We could obtain the same result by converting i_{s1} and R_1 into a Thevenin equivalent with voltage $i_{s1} R_1$ and resistance R_1 . The current is then obtained directly as the above formula.

Note: We could also obtain the same result by treating v_n as a source voltage and using superposition of sources i_{s1} and v_n . We would obtain $i_{\text{left}1} = i_{s1} \frac{R_1}{R_1 + R_2}$ (i-divider) + $i_{\text{left}2} = -\frac{v_n}{R_1 + R_2}$ (i in R_2)

Fourth, we find an expression for the current, i_{right} , flowing to the right in R_3 .

We make sure we use v_n and v_o in this expression.

$$i_{\text{right}} = \frac{v_n - v_o}{R_3}$$

Fifth, we equate i_{left} and i_{right} and solve for v_0 .

$$i_{\text{left}} = \frac{i_{s1} R_1 - v_n}{R_1 + R_2} = \frac{v_n - v_0}{R_3} = i_{\text{right}}$$

or

$$v_0 = -\left(i_{s1} R_1 - v_n\right) \frac{R_3}{R_1 + R_2} + v_n$$

or

$$v_0 = v_n \frac{R_1 + R_2}{R_1 + R_2} + v_n \frac{R_3}{R_1 + R_2} - \frac{i_{s1} R_1 R_3}{R_1 + R_2}$$

or

$$v_0 = v_n \frac{R_1 + R_2 + R_3}{R_1 + R_2} - i_{s1} \frac{R_1 R_3}{R_1 + R_2}$$

(where v_n formula is given earlier)

b)

$$\text{we have } v_n = i_{s2} \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$\text{and } v_0 = i_{s2} \frac{R_1 R_3}{R_1 + R_2} - i_{s1} \frac{R_1 R_3}{R_1 + R_2}$$

or

$$v_0 = (i_{s2} - i_{s1}) \frac{R_1 R_3}{R_1 + R_2}$$

Note that we obtain the above before we even begin substituting for i_{cm} and i_{dm} .

Since $i_{dm} = i_{s2} - i_{s1}$, we have

$$v_0 = i_{dm} \frac{R_1 R_3}{R_1 + R_2}$$