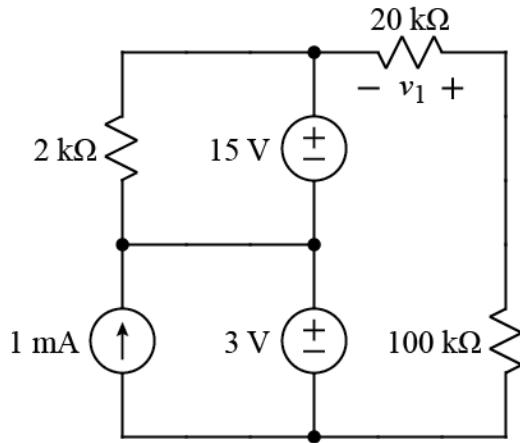


Ex:Calculate i_1 .

SOL'N: If we consider the voltage-loop on the right side, we have a voltage divider, but with a minus sign because of the polarity of the v_1 measurement.

$$v_1 = -(15 \text{ V} + 3 \text{ V}) \cdot \frac{20 \text{ k}\Omega}{20 \text{ k}\Omega + 100 \text{ k}\Omega} = -18 \text{ V} \cdot \frac{1}{6} = -3 \text{ V}$$