
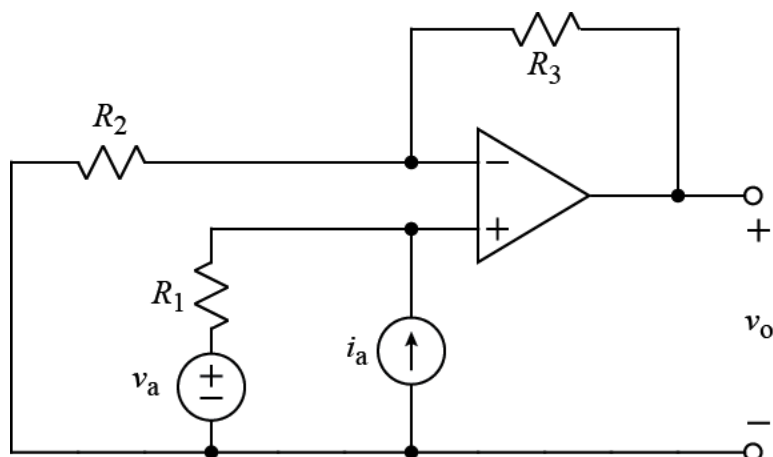


Ex:

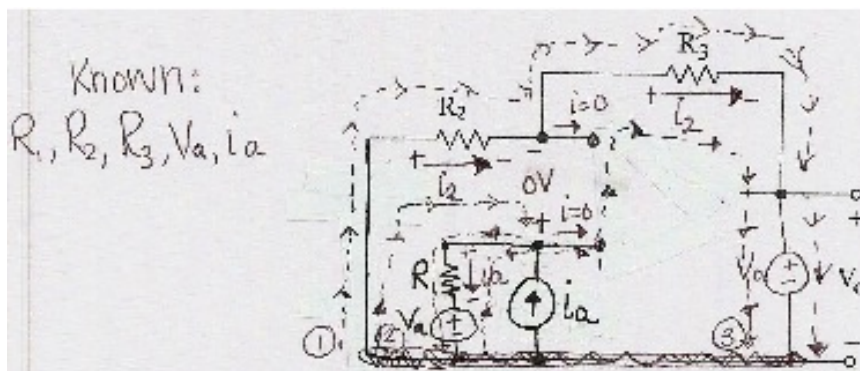

The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for  $v_o$  in terms of not more than  $v_a$ ,  $i_a$ ,  $R_1$ ,  $R_2$ , and  $R_3$ .

SOL'N:



KNOWN:  
 $R_1, R_2, R_3, v_a, i_a$

V-loop: ①  $-i_2 R_2 - i_2 R_3 - v_o = 0$   
 ②  $-i_2 R_2 - i_a R_1 + v_a = 0$   
 ③  $+v_a + i_a R_1 - i_2 R_3 - v_o = 0$

①  $v_o = -i_2 (R_2 + R_3)$

②  $i_2 = -\frac{(v_a + i_a R_1)}{R_2}$

plug ② into ①

$$v_o = \frac{(v_a + i_a R_1)}{R_2} (R_2 + R_3) = \left(1 + \frac{R_3}{R_2}\right) (v_a + i_a R_1)$$