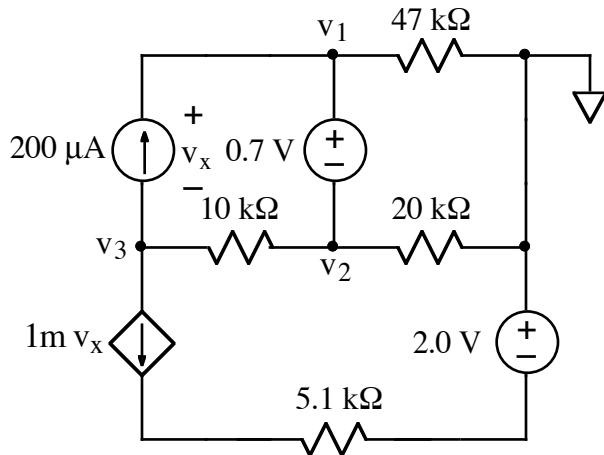


Ex:

Use the node-voltage method to find  $v_1$ ,  $v_2$ , and  $v_3$ .

*Sol'n:* We have  $v_1$ ,  $v_2$  supernode since  $v_3$  is a reference without resistor is between nodes. Thus, we sum all currents out of bubble, (arrows),

$$-200 \mu\text{A} + \frac{v_1 - 0V}{47 \text{k}\Omega} + \frac{v_2 - v_3}{10 \text{k}\Omega} + \frac{v_3 - 0V}{20 \text{k}\Omega} = 0A$$

We add a  $v$ -drop eq'n:

$$v_2 + 0.7V = v_1$$

Then we finish with the current sum for node  $v_3$ :

$$200 \mu\text{A} + \frac{v_3 - v_2}{10 \text{k}\Omega} + \frac{1m(v_1 - v_3)}{5.1 \text{k}\Omega} = 0A$$

↗  *$v_x$  in terms of node  $v_1$ 's*  
*added to make units correct*

Now we do the algebra: (1st & 3rd eqns first)

$$V_1 - \frac{1}{47k\Omega} + V_2 \left( \frac{1}{10k\Omega} + \frac{1}{20k\Omega} \right) + V_3 \left( \frac{-1}{10k\Omega} \right) = 200\mu A$$

$$V_1 - 1m + V_2 \frac{-1}{10k\Omega} + V_3 \left( \frac{1}{10k\Omega} - 1m \right) = -200\mu A$$

Multiply both sides by  $20k\Omega$  to clear most fractions:

$$V_1 \frac{20k\Omega}{47k\Omega} + V_2 \cdot 3 + V_3 (-2) = 4V$$

$$V_1 \cdot 20 + V_2 (-2) + V_3 (\underbrace{z - 20}_{-18}) = -4V$$

Use v-drop eqn to substitute for  $V_1$ :

$$(V_2 + 0.7V) \frac{20}{47} + V_2 (3) + V_3 (-2) = 4V$$

$$(V_2 + 0.7) \frac{20}{47} + V_2 (-2) + V_3 (-18) = -4V$$

Now multiply 1<sup>st</sup> eqn by (-9) and sum eqns:

$$\begin{aligned} &+ (-9)(V_2 + 0.7V) \frac{20}{47} + (-9)V_2 (3) + (-9)V_3 (-2) = (-9)4V \\ \hline \end{aligned}$$

$$\Rightarrow \frac{(V_2 + 0.7V)(-9) \frac{20}{47} + 20}{47} + V_2 (-29) = -40V$$

$$\Rightarrow V_2 \left( \frac{-9}{47} \frac{20}{47} + 20 - 29 \right) = -40V - 0.7 \left[ (-9) \frac{20}{47} + 20 \right] V$$

$$\text{or } V_2 \left( \frac{-9}{47} \left( \frac{20}{47} + 1 \right) \right) = -40V - 0.7 \left[ (-9) \left( \frac{20}{47} + 1 \right) + 20 \right] V$$

$$\text{or } V_2 (-9) \left[ \frac{20}{47} + 1 \right] = -40V - 0.7(29)V - 0.7 \left[ \frac{20}{47} + 1 \right] V$$

$$\text{or } V_2 = \frac{-40V - 0.7(29)V - 0.7V}{-9 \left( \frac{20}{47} + 1 \right)}$$

$$= \frac{-\frac{400}{10}V - \frac{29}{10}(29)V - 0.7V}{-9 \cdot \frac{67}{47}}$$

$$= \frac{-603}{(-9)10} \cdot \frac{47}{67} V - 0.7V$$

$$= -\frac{9}{-9} \cdot \frac{47}{10} V - 0.7V$$

$$= 4.7V - 0.7V$$

$$V_2 = 4.0V$$

$$V_1 = V_2 + 0.7V = 4.7V$$

$$V_1 \left( \frac{20}{47} \right) + V_2 (+3) + V_3 (-2) = 4V$$

$$4.7 \left( \frac{20}{47} \right) + 4.0 + V_3 (-2) = 4V$$

$$\text{or } V_3 = 5V$$