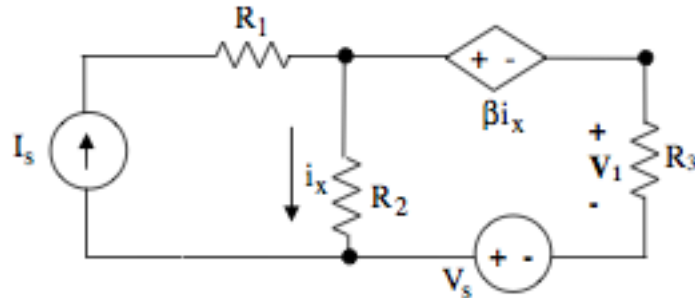





1.




Using superposition, derive an expression for v_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , R_3 , and β , where $\beta < 0$.

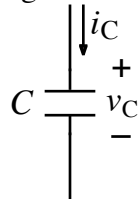2. In (a)-(c), the voltage $v_C(t)$ across a $0.2 \mu\text{F}$ capacitor is listed. Find the current, $i_C(t)$, flowing in the capacitor in each case as a function of time:



- a) $v_C(t) = 3 \text{ V}$
- b) $v_C(t) = 1000t \text{ V/s}$
- c) $v_C(t) = 1 - e^{-t/4\text{ms}} \text{ V}$

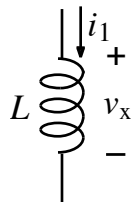3. In (a)-(c), the current $i_L(t)$ flowing into a 0.5 mH inductor is listed. Find the voltage, $v_L(t)$, across the inductor in each case as a function of time:



- a) $i_L(t) = 5 \text{ mA}$
- b) $i_L(t) = 5t \text{ mA/s}$
- c) $i_L(t) = 5 \sin(2\pi \cdot 100t) \text{ mA}$

4. The following equation describes the voltage, v_C , across a capacitor as a function of time. Find the time, t , at which v_C is equal to 2 V .

$$v_C(t) = 1 + 3(1 - e^{-t/8\text{ms}}) \text{ V}$$

5. The following equation describes the voltage, v_L , across an inductor as a function of time. Find an expression for the current, $i_L(t)$, through the inductor as a function of time. Assume that $i_L(t = 0) = 0$ A and $L = 10$ mH.

$$v_L(t) = 2 + 6(1 - e^{-t/12.5\mu\text{s}}) \text{ kV}$$

Answers:

$$1. \quad v_1 = \left(1 - \frac{\beta}{R_2}\right) \frac{i_s R_2 R_3}{R_2 + R_3 - \beta} + \frac{v_s R_3}{R_2 + R_3 - \beta}$$

$$2.c. \quad i_C = 50 \mu\text{A} e^{-t/4\text{ms}}$$

$$3.c. \quad v_L = \frac{\pi}{2} \cos(2\pi \cdot 100t) \text{ mV}$$

$$4. \quad t = 3.24 \text{ ms}$$

$$5. \quad \text{Hint: } i_L(t) = \frac{1}{L} \int_0^t [2 + 6(1 - e^{-t/12.5\mu\text{s}}) \text{kV}] dt + 0 \text{ A} \text{ and compute the integral}$$