
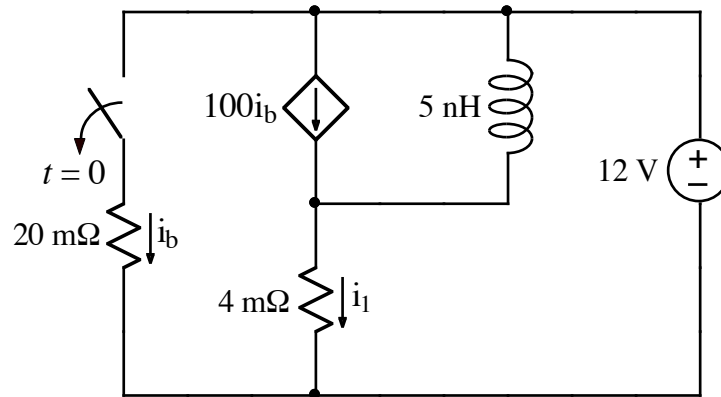


Ex:

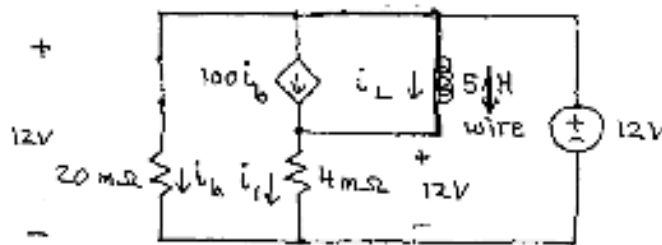

After being closed for a long time, the switch opens at  $t = 0$ . Find  $i_1(t)$  for  $t > 0$ .

sol'n:  $t = 0^-$  model: (to find  $i_L(0^-)$ ) L acts like wire



We see that the 12V source is across the  $20\text{ m}\Omega$  and the  $4\text{ m}\Omega$ .

$$\therefore i_b = \frac{12\text{ V}}{20\text{ m}\Omega} = 600\text{ A}$$

$$\text{and } 100 i_b = 100 \cdot 600\text{ A} = 60\text{ kA.}$$

$$i_1 = \frac{12\text{ V}}{4\text{ m}\Omega} = 3\text{ kA}$$


We find  $i_L$  from a current sum at the center node.

$$-100i_b + i_1 - i_L(0^-) = 0A$$

$$-60kA + 3kA = i_L(0^-)$$

$$\text{or } i_L(0^-) = -57kA$$

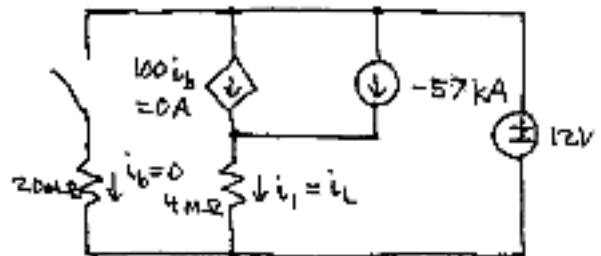$t = 0^+$  model:  $i_L(0^+) = i_L(0^-) = -57kA$   
 $L$  modeled as current source




Because of the open circuit on the left, we have  $i_b = 0$  and  $100i_b = 0$ .

From a current summation at the center node, we have  $i_1(0^+) = i_L(0^+) = -57kA$ .

$$i_1(0^+) = -57kA$$

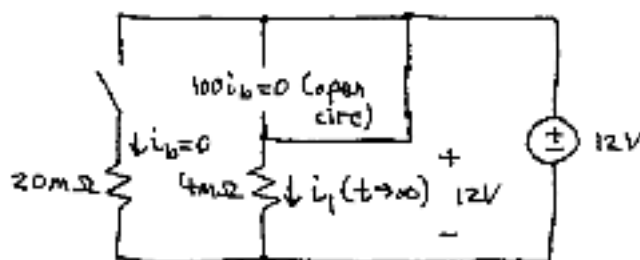
$t \rightarrow \infty$  model: (to find  $i_1(t \rightarrow \infty)$ )  $L$  acts like wire




We have 12V across the  $4\text{ m}\Omega$ .

$$i_1(t \rightarrow \infty) = \frac{12\text{V}}{4\text{ m}\Omega} = 3\text{ kA}$$

model for  $\tau = L/R_{\text{Th}}$ :

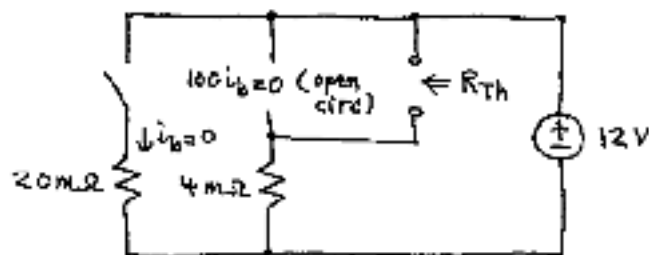

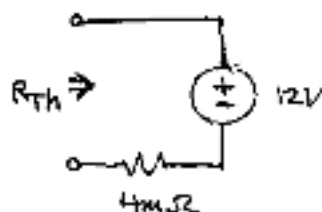We observe that the Thevenin equivalent seen from the terminals where the  $L$  is connected is just the  $4\text{ m}\Omega$  and 12V:



We find  $R_{\text{Th}}$  by turning off the 12V source, causing it to be a wire. We see  $R_{\text{Th}} = 4\text{ m}\Omega$ . (The circuit is already a Thevenin equivalent.)

$$\therefore \tau = \frac{L}{R_{\text{Th}}} = \frac{5\text{ nH}}{4\text{ m}\Omega} = 1.25\text{ }\mu\text{s}$$

---

Now we use the general form of solution:

$$i_1(t) = i_1(t \rightarrow \infty) + [i_1(0^+) - i_1(t \rightarrow \infty)] e^{-t/\tau}$$

$$\text{or } i_1(t) = 3\text{kA} + [-57\text{kA} - 3\text{kA}] e^{-t/1.25\mu\text{s}}$$

$$\text{or } i_1(t) = 3\text{kA} + -60\text{kA} e^{-t/1.25\mu\text{s}}$$