
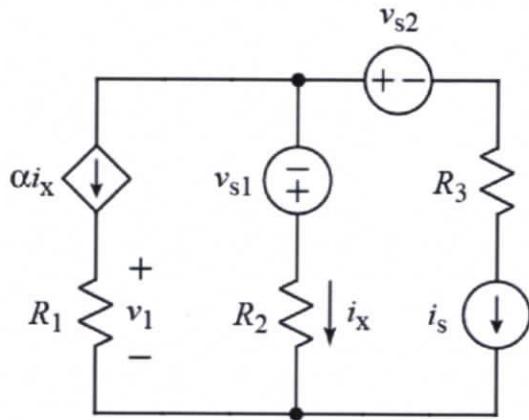


Ex:

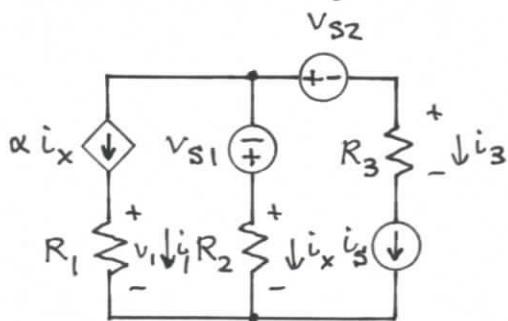

- Derive an expression for v_1 . The expression must not contain more than the circuit parameters v_{s1} , v_{s2} , i_s , R_1 , R_2 , R_3 and α . Note: $\alpha > 0$.
- Derive an expression for the power dissipated by resistor R_3 . The expression must not contain more than the circuit parameters v_{s1} , v_{s2} , i_s , R_1 , R_2 , R_3 and α .

sol'n: a) Using Kirchhoff's laws and Ohm's law, we start by labeling v and i for each R . One way of labeling the circuit is shown below.



We have no v -loops, since every v -loop would pass through a current source.

For the top node, we have this i -sum:

$$\alpha i_X + i_X + i_s = 0A$$

We can solve the i-sum eq'n for i_x .

$$(1 + \alpha) i_x = -i_s$$


or

$$i_x = \frac{-i_s}{(1 + \alpha)}$$

To find v_1 , we use Ohm's law. R_1 is in series with the αi_x source. Thus, v_1 is $\alpha i_x \cdot R_1$:

$$v_1 = \alpha i_x R_1 = -\frac{\alpha i_s R_1}{1 + \alpha}$$

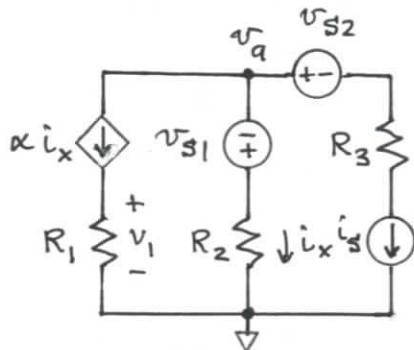As an alternative, we may use the Node-V method. In the circuit below, we have a reference on the bottom and node v_a on the top.



$$\text{Eq'n for node } v_a: \alpha i_x + \frac{v_a + v_{S1}}{R_2} + i_s = 0 \text{ A}$$

We replace i_x with an expression in terms of v_a :

$$i_x = \frac{v_a + v_{S1}}{R_2}$$

$$\text{New node } v_a \text{ eq'n: } \alpha \frac{v_a + v_{S1}}{R_2} + \frac{v_a + v_{S1}}{R_2} + i_s = 0 \text{ A}$$

Now we do the algebra to find v_a .

$$v_a \frac{(1+\alpha)}{R_2} = -i_s - \frac{(1+\alpha)}{R_2} v_{s1}$$

or

$$v_a = -i_s \frac{R_2}{1+\alpha} - v_{s1}$$

From v_a , we find i_x , then αi_x , then v_i .

$$i_x = \frac{v_a + v_{s1}}{R_2} = -\frac{i_s}{1+\alpha}$$

then

$$\alpha i_x = -\frac{\alpha i_s}{1+\alpha}$$

then

$$v_i = \alpha i_x R_1 = -\frac{\alpha i_s}{1+\alpha} R_1.$$

- b) Power is $i^2 R$ for a resistor. The i is i_s for R_3 .

$$P_{R3} = i_s^2 R_3$$