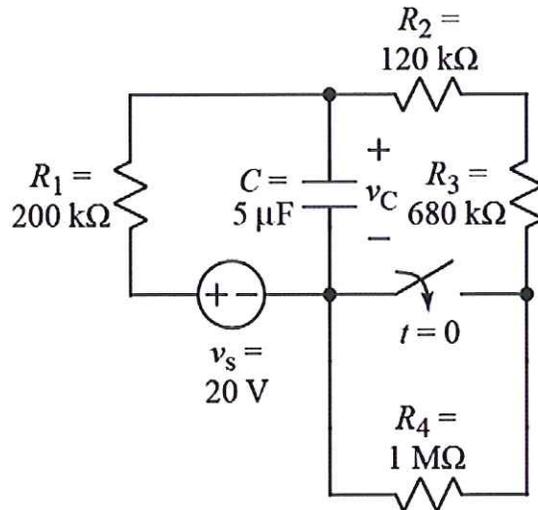



Ex:



After being open for a long time, the switch closes at $t = 0$.

Write a numerical time-domain expression for $v_C(t > 0)$, the voltage across C .

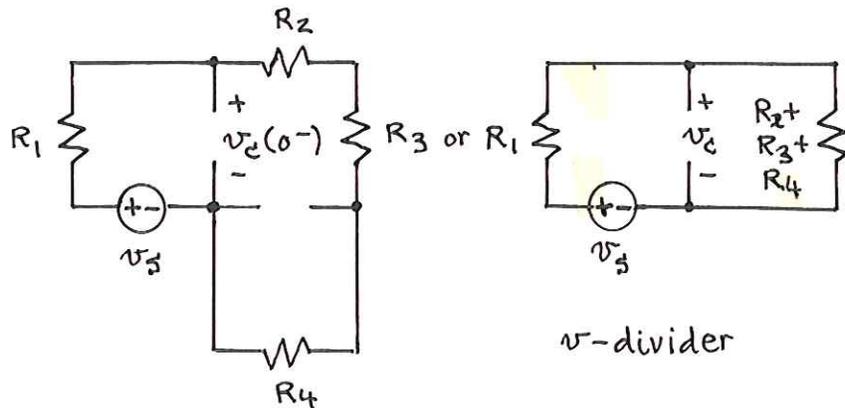sol'n: $t = 0^-$: $C =$ open, switch open, find $v_C(0^-)$



Using v -divider: $v_C(0^-) = v_s \frac{R_2 + R_3 + R_4}{R_1 + R_2 + R_3 + R_4}$

or


$$v_C(0^-) = 20V \cdot \frac{1.8 M\Omega}{2 M\Omega}$$

or

$$v_C(0^-) = 18V$$

$t=0^+$: $v_c(0^+) = v_c(0^-) = 18V$ No circuit work this time.

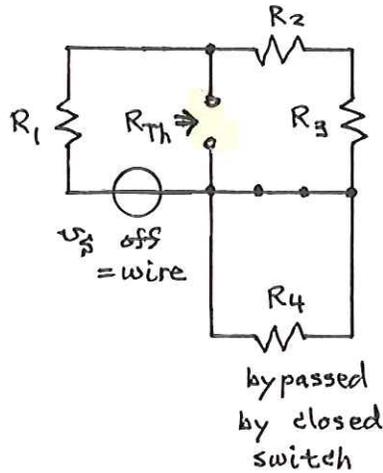$t>0$: Find R_{Th} for circuit where C is connected. Turn off independent source v_3 . Look into circuit from where C is connected.



R_1 is in parallel with $R_2 + R_3$.


$$R_{Th} = R_1 \parallel (R_2 + R_3) = 200k\Omega \parallel (120k\Omega + 680k\Omega)$$

or

$$R_{Th} = 200k\Omega \parallel 800k\Omega = 200k\Omega \cdot \frac{1}{1+4} = 160k\Omega$$

$$\text{So } \tau = R_{Th}C = 160k\Omega \cdot 5\mu F = 800 \text{ ms.}$$

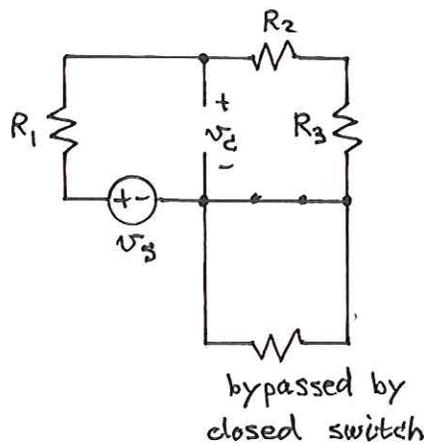$t \rightarrow \infty$: $C = \text{open}$, switch closed, find $v_c(t \rightarrow \infty)$



v_c is across $R_2 + R_3$ in a v -divider

$$\begin{aligned} v_c(t \rightarrow \infty) &= v_3 \frac{R_2 + R_3}{R_1 + R_2 + R_3} \\ &= 20V \cdot \frac{120k + 680k\Omega}{200k + 120k + 680k\Omega} \\ &= 20V \cdot \frac{800k}{1M\Omega} = 16V \end{aligned}$$

Summary of results:

$$v_c(0^+) = 18V$$

$$\tau = 800 \text{ ms}$$

$$v_c(t \rightarrow \infty) = 16V$$

Now we use the general sol'n for RC circuits:

$$v_c(t > 0) = v_c(t \rightarrow \infty) + [v_c(0^+) - v_c(t \rightarrow \infty)] e^{-t/\tau}$$

or

$$v_c(t > 0) = 16V + (18V - 16V) e^{-t/800 \text{ ms}}$$

or

$$v_c(t > 0) = 16V + 2V e^{-t/800 \text{ ms}}$$