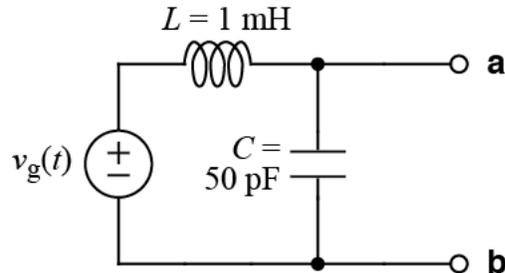


Ex:



$$v_g(t) = 6 \cos(20Mt) \text{ V}$$

- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $i_g(t)$, and show numerical impedance values for R , L , and C . Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit relative to terminals **a** and **b**. Give the numerical phasor value for \mathbf{V}_{Th} and the numerical impedance value of z_{Th} .


SOL'N: a) The phasor for the voltage source is a real number (no phase shift).

$$\mathbf{V}_g = 6 \angle 0^\circ \text{ V}$$

From the expression for $v_g(t)$, we have $\omega = 20 \text{ Mr/s}$. We use this to calculate the impedance of the L and C .

$$j\omega L = j20\text{M}(1\text{m})\Omega = j20\text{k}\Omega$$
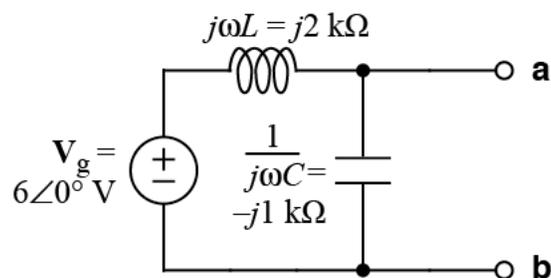
$$\frac{1}{j\omega C} = \frac{1}{j20\text{M}(50\text{pF})} \Omega = \frac{1}{j1\text{m}} = -j1\text{k}\Omega$$



- The Thevenin voltage is the voltage across **a** and **b** with no load attached. We have a simple **V**-divider.

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_{\text{ab}} \frac{-j1\text{k}\Omega}{j20\text{k}\Omega + -j1\text{k}\Omega} = 6\angle 0^\circ \text{V} \frac{-1}{20-1} = \frac{6}{19} \angle \pm 180^\circ \text{V}$$

To find the Thevenin impedance, we turn off the voltage source, which becomes a wire, and look in from the **a** and **b** terminals. We see the impedances in parallel.

$$z_{\text{Th}} = -j1\text{k}\Omega \parallel j20\text{k}\Omega = j1\text{k}\Omega \cdot (-1 \parallel 20) = j1\text{k}\Omega \cdot \frac{-20}{19} = -j \frac{20}{19} \text{k}\Omega$$

