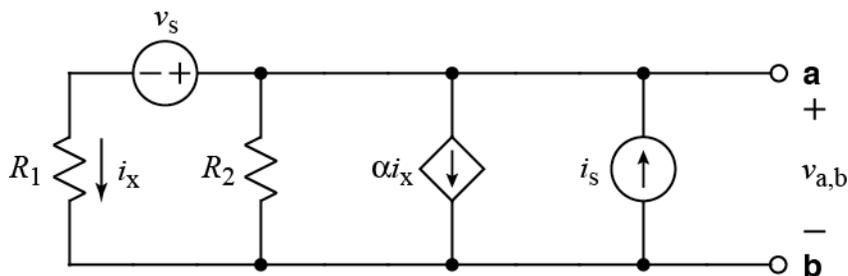


Ex:



- Using superposition, derive an expression for  $v_{a,b}$  that contains no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ , and  $\alpha$ . Current  $i_x$  must not appear in your solution. **Note:**  $\alpha \geq 0$ .
- Make a consistency check on your expression for  $v_{a,b}$  by setting resistors and sources to numerical values for which the value of  $v_{a,b}$  is obvious. State the values of resistors and sources for your consistency check, and show that your expression for  $v_{a,b}$  is satisfied for these values. (In other words, plug the values into your expression from part (a) and show that it agrees with the value from your consistency check.)
- Find the Thevenin equivalent circuit at terminals **a** and **b**. Express the Thevenin voltage,  $v_{Th}$ , and Thevenin resistance,  $R_{Th}$  in terms of no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ , and  $\alpha$ .  $i_x$  must not appear in your solution. **Note:**  $\alpha \geq 0$ .
- Find an expression for the value of  $R_L$  connected from **a** to **b** that would absorb maximum power. Your answer must be written in terms of no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ , and  $\alpha$ . **Note:**  $\alpha \geq 0$ .

**SOL'N:** a) In superposition, we turn on one independent source at a time, and we keep dependent sources on all the time.

Case I: Turn on  $v_s$  and turn off  $i_s$  (which becomes an open circuit).

Using the node-voltage method, we label the entire top wire to the right of  $v_s$  as  $v_{a,b}$  and we label the bottom wire as reference. We then write an expression for  $i_x$  in terms of node-voltage  $v_{a,b}$  and write an equation for the sum of currents out of the  $v_{a,b}$  node.

$$i_x = \frac{v_{a,b} - v_s}{R_1}$$

Now the sum-of-currents equation:

$$\frac{v_{a,b1} - v_s}{R_1} + \frac{v_{a,b1}}{R_2} + \alpha \frac{v_{a,b1} - v_s}{R_1} = 0 \text{ A}$$

We factor out  $v_{a,b}$  and move constants to the other side of the equation:

$$v_{a,b1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \alpha \frac{1}{R_1} \right) = v_s \left( \frac{1}{R_1} + \alpha \frac{1}{R_1} \right)$$

or

$$v_{a,b1} = v_s \frac{\frac{1+\alpha}{R_1}}{\frac{1+\alpha}{R_1} + \frac{1}{R_2}} = v_s \frac{(1+\alpha)R_2}{(1+\alpha)R_2 + R_1}$$

An alternative approach is to model the dependent source as a resistor,  $R_{eq}$ . We observe that  $v_{a,b}$  may then be computed by using a voltage divider:

$$v_{a,b1} = v_s \frac{R_2 \parallel R_{eq}}{R_1 + R_2 \parallel R_{eq}}$$

To find the equivalent resistance of the dependent source, we observe that current  $i_x$  flows through  $R_2$  in parallel with  $R_{eq}$ , so we have a current divider with currents  $(1 + \alpha)i_x$  in  $R_2$  and  $-\alpha i_x$  in  $R_{eq}$ . The ratio of the currents is the inverse of the ratio of the resistances:

$$\frac{(1 + \alpha)i_x}{-\alpha i_x} = \frac{R_{eq}}{R_2}$$

or

$$R_{eq} = -R_2 \frac{1 + \alpha}{\alpha}$$

Now we can compute the parallel resistance of  $R_2$  and  $R_{eq}$ .

$$R_2 \parallel R_{eq} = R_2 \parallel -\frac{R_2(1 + \alpha)}{\alpha} = R_2 \cdot 1 \parallel -\frac{1 + \alpha}{\alpha} = R_2 \frac{-\frac{1 + \alpha}{\alpha}}{1 - \frac{1 + \alpha}{\alpha}}$$

or

$$R_2 \parallel R_{\text{eq}} = R_2 \frac{-(1+\alpha)}{\alpha - (1+\alpha)} = R_2(1+\alpha)$$

We use this result in the voltage divider, obtaining the same result as before:

$$v_{\text{a,b1}} = v_s \frac{R_2 \parallel R_{\text{Eq}}}{R_1 + R_2 \parallel R_{\text{Eq}}} = v_s \frac{R_2(1+\alpha)}{R_1 + R_2(1+\alpha)}$$

Case II: Turn off  $v_s$  (which becomes a wire) and turn on  $i_s$ .

Using node voltage, we proceed as in Case I but have a simpler equations because  $v_s$  is off.

$$i_{\text{x2}} = \frac{v_{\text{a,b2}}}{R_1}$$

Now the sum-of-currents equation:

$$\frac{v_{\text{a,b2}}}{R_1} + \frac{v_{\text{a,b2}}}{R_2} + \alpha \frac{v_{\text{a,b2}}}{R_1} - i_s = 0 \text{ A}$$

We factor out  $v_{\text{a,b}}$  and move constants to the other side of the equation:

$$v_{\text{a,b2}} \left( \frac{1}{R_1} + \frac{1}{R_2} + \alpha \frac{1}{R_1} \right) = i_s$$

or

$$v_{\text{a,b2}} [R_2(1+\alpha) + R_1] = i_s R_1 R_2$$

or

$$v_{\text{a,b2}} = i_s \frac{R_1 R_2}{(1+\alpha)R_2 + R_1}$$

An alternative approach is to model the dependent source as a resistor. We have the dependent source in parallel with  $R_1$ , and we may calculate the voltage across  $R_1$  as  $i_x R_1$ . This voltage is also across the dependent source, allowing us to define an equivalent resistance for the dependent source using Ohm's law:

$$R_{\text{Eq2}} = \frac{i_x R_1}{\alpha i_x} = \frac{R_1}{\alpha}$$

---

It is interesting to note that this equivalent resistance is different than the equivalent resistance from Case I.

Now we have current source  $i_s$  in parallel with three resistors that we can combine into one resistance, and Ohm's law gives  $v_{a,b2}$  in terms of current times resistance:

$$v_{a,b2} = i_s \cdot R_1 \parallel R_2 \parallel R_{Eq2} = i_s \cdot R_1 \parallel R_2 \parallel \frac{R_1}{\alpha}$$

or

$$v_{a,b2} = i_s \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{\alpha}{R_1}} = i_s \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}$$

Now we sum the two  $v_{a,b}$ 's to get the total  $v_{a,b}$ :

$$v_{a,b} = v_{a,b1} + v_{a,b2} = v_s \frac{R_2(1 + \alpha)}{R_1 + R_2(1 + \alpha)} + i_s \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}$$

- b) One consistency check is to set  $v_s = 0$  V and set  $\alpha = 1$ , causing  $R_1$  and the dependent source to be in parallel and have the same current, implying that they are the same resistance. In parallel, they have resistance  $R_1/2$ .

In this case, our circuit will have the following output voltage:

$$v_{a,b} = i_s \cdot \frac{R_1}{2} \parallel R_2 = i_s \cdot \frac{\frac{R_1}{2} R_2}{\frac{R_1}{2} + R_2} = i_s \cdot \frac{R_1 R_2}{R_1 + 2R_2}$$

Now we check what value our formula from part (a) gives:

$$v_{a,b} = 0 \cdot \frac{R_2(1+1)}{R_1 + R_2(1+1)} + i_s \frac{R_1 R_2}{(1+1)R_2 + R_1} = i_s \frac{R_1 R_2}{2R_2 + R_1}$$

This agrees with what we expect, so the consistency check is satisfied. Many other checks are possible.

- c) The voltage  $v_{a,b}$  found in part (a) is the Thevenin equivalent voltage, so all we need now is  $R_{Th}$ . Perhaps the simplest way to find  $R_{Th}$  is to turn off the independent sources and connect a current source to the output. We then determine  $v_{a,b}$  across the current source and use Ohm's law to find  $R_{Th}$ . For the source, we could use a value of  $i_s$ , in which case we have exactly Case II of the superposition from part (a). Our voltage will then be  $v_{a,b2}$ . Thus, we have the following value for  $R_{Th}$ :

$$R_{Th} = \frac{v_{a,b2}}{i_s} = \frac{i_s \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}}{i_s} = \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}$$

An alternative approach to finding  $R_{Th}$  is to use the short-circuit current,  $i_{sc}$ , that flows from **a** to **b** when a wire is connected across those terminals. In that case, the voltage on the top and bottom rails is zero. This means there is no voltage drop across  $R_2$ , and we may ignore  $R_2$ . Also, we have voltage  $-v_s$  on the top end of  $R_1$ , giving the current for  $i_x$  directly:

$$i_x = -\frac{v_s}{R_1}$$

Now we can write a current summation for the top rail:

$$-\frac{v_s}{R_1} + \alpha \left( -\frac{v_s}{R_1} \right) - i_s + i_{sc} = 0 \text{ A}$$

or

$$i_{sc} = \frac{v_s}{R_1} - \alpha \left( -\frac{v_s}{R_1} \right) + i_s = v_s \frac{1 + \alpha}{R_1} + i_s$$

Using this current, we find  $R_{Th}$ :

$$R_{Th} = \frac{v_{a,b}}{i_{sc}} = \frac{v_s \frac{R_2(1 + \alpha)}{R_1 + R_2(1 + \alpha)} + i_s \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}}{v_s \frac{1 + \alpha}{R_1} + i_s}$$

---

or

$$R_{\text{Th}} = \frac{v_{\text{a,b}}}{i_{\text{sc}}} = \frac{R_1 R_2}{R_1 + R_2(1 + \alpha)}$$

d) Maximum power is obtained by setting  $R_{\text{L}} = R_{\text{Th}}$ :

$$R_{\text{L}} = R_{\text{Th}} = \frac{R_1 R_2}{(1 + \alpha)R_2 + R_1}$$