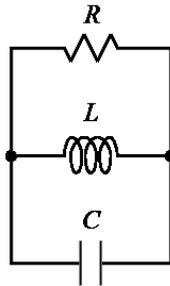


Ex:



$$R = 0.5 \, \Omega$$

$$L = 1.5 \, \mu\text{H}$$

$$C = 1.5 \, \mu\text{F}$$

- Find the characteristic roots, s_1 and s_2 , for the above circuit.
- Is the circuit over-damped, critically-damped, or under-damped? Explain.
- If the L and C values in the circuit are decreased by a factor of two, (and R remains the same), what kind of damping results?

SOL'N: a) We have a parallel RLC circuit. We use the equations for roots of a parallel RLC.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where

$$\alpha = \frac{1}{2RC} = \frac{1}{2(0.5)1.5\mu\text{s}} = \frac{1\text{M}}{1.5\text{s}} = \frac{2}{3}\text{Mr/s} \approx 667\text{kr/s}$$

and

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(1.5\mu)(1.5\mu)\text{s}^2} = \left(\frac{2}{3}\text{Mr/s}\right)^2$$

Using component values, we compute the numerical values of the roots.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\frac{2}{3}\text{Mr/s} \pm \sqrt{\left(\frac{2}{3}\text{Mr/s}\right)^2 - \left(\frac{2}{3}\text{Mr/s}\right)^2}$$

or

$$s_{1,2} = -\frac{2}{3}\text{Mr/s}$$

- The roots are both the same, so we have critical damping.

c) We reduce L and C by a factor of two and see what happens.

$$\alpha_{\text{new}} = \frac{1}{2RC/2} = 2 \cdot \frac{2}{3} \text{ Mr/s} \approx 1.33 \text{ Mr/s}$$

$$\omega_{\text{o_new}}^2 = \frac{1}{(L/2)(C/2)} = \frac{4}{(1.5\mu)(1.5\mu)\text{s}^2} = \left(2 \cdot \frac{2}{3} \text{ Mr/s}\right)^2$$

We see that the square root will once again be zero.

$$\sqrt{\alpha_{\text{new}}^2 - \omega_{\text{o_new}}^2} = \sqrt{\left(2 \cdot \frac{2}{3} \text{ Mr/s}\right)^2 - \left(2 \cdot \frac{2}{3} \text{ Mr/s}\right)^2} = 0 \text{ Mr/s}$$

Thus, the two roots are again the same, and we again have critical damping.

$$s_{1,2} = -\frac{4}{3} \text{ Mr/s}$$