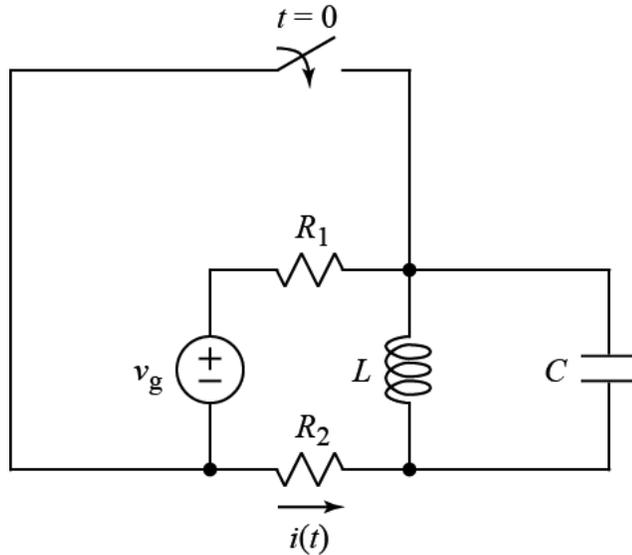


Ex:



After being open for a long time, the switch closes at $t = 0$.

- a) Give expressions for the following in terms of no more than v_g , R_1 , R_2 , L , and C :


$$i(t=0^+) \quad \text{and} \quad \left. \frac{di(t)}{dt} \right|_{t=0^+}$$

- b) Find the numerical value of R_2 given the following information:

$$R_1 = 150 \, \Omega \quad L = 40 \, \text{mH} \quad C = 3.2 \, \mu\text{F}$$

$$\alpha = 1250 \, \text{r/s} \quad \omega_d = 2500 \, \text{r/s}$$

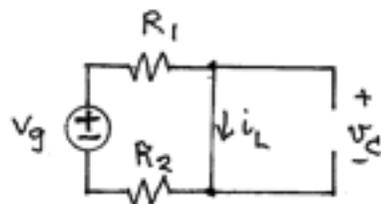SOL'N: a) We start with the circuit at $t=0^-$ to determine the state of the L and C . At $t=0^-$, $L = \text{wire}$, $C = \text{open}$




$$v_C(0^-) = 0V \text{ (shorted by } L)$$

$$i_L(0^-) = \frac{v_g}{R_1 + R_2}$$

At $t=0^+$, the switch is closed and $i_L(0^+) = i_L(0^-)$ and $v_C(0^+) = v_C(0^-)$.

V_g and R_1 are shorted out by the switch. This short divides the circuit into two halves that we may solve independently. The one we are interested in consists of R_2 , L , and C .

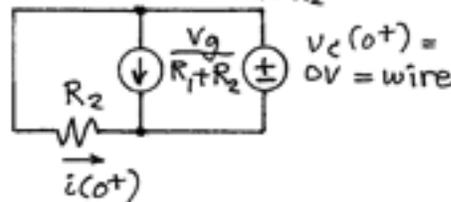$t=0^+$: $i_L(0^+) = \frac{V_g}{R_1+R_2}$ = current source



Because the C acts like a wire, all the current from the L will flow thru the C . So the current in R_2 is zero. (Another way to see this is to observe that R_2 has $0V = v_C$ across it, and by Ohm's law $i(0^+) = 0V/R_2 = 0A$.)

So $i(0^+) = 0A$.

For $\left. \frac{di}{dt} \right|_{t=0^+}$, we first write $i(t)$

in terms of i_L and/or v_C .

We observe that v_C is across R_2 :

$$i(t) = v_C / R_2$$

Now we differentiate the entire eq'n:

$$\frac{di(t)}{dt} = \frac{1}{R_2} \frac{dv_C}{dt} = \frac{1}{R_2} \frac{i_C}{C}$$

(We have used $i_C = C \frac{dv_C}{dt}$ rearranged.)

We evaluate i_C at $t=0^+$. We noted earlier that all the current from the L goes thru C. If we follow the direction of the current arrow for the L down, over, and up thru the C, we see that


$$i_C(0^+) = -i_L(0^+) = -\frac{V_0}{R_1 + R_2}$$

$$\text{Thus, } \left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{1}{R_2 C} i_C(0^+)$$

or

$$\left. \frac{di(t)}{dt} \right|_{t=0^+} = \frac{-V_0}{R_2 C (R_1 + R_2)}$$

b) We use the circuit for $t > 0$.

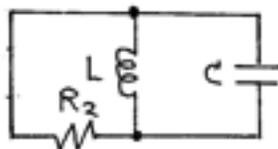

We have a parallel RLC.

$$\alpha = \frac{1}{2R_2 C}, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}, \quad \omega_0^2 = \frac{1}{LC}$$

$$\text{Use } \alpha: R_2 = \frac{1}{2\alpha C} = \frac{1}{2(1250)3.2\mu} = 125 \Omega$$