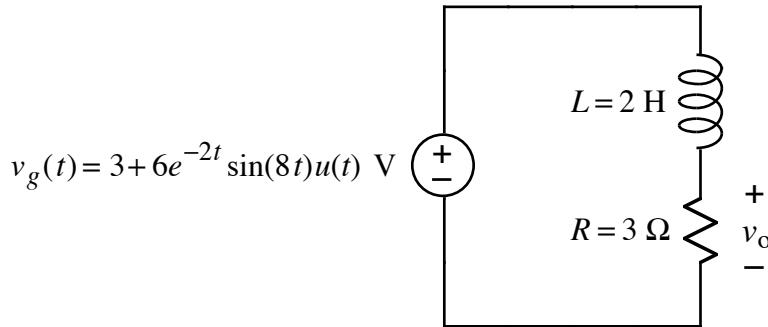



1.



Note: The 3 V in the $v_g(t)$ source is always on.

- a) Write the Laplace transform, $V_g(s)$, of $v_g(t)$.
- b) Draw the s -domain equivalent circuit, including source $V_g(s)$, components, initial conditions for L , and terminals for $V_o(s)$.
- 2. c) Write an expression for $V_o(s)$.
- d) Apply the initial value theorem to find $\lim_{t \rightarrow 0^+} v_o(t)$.

3.

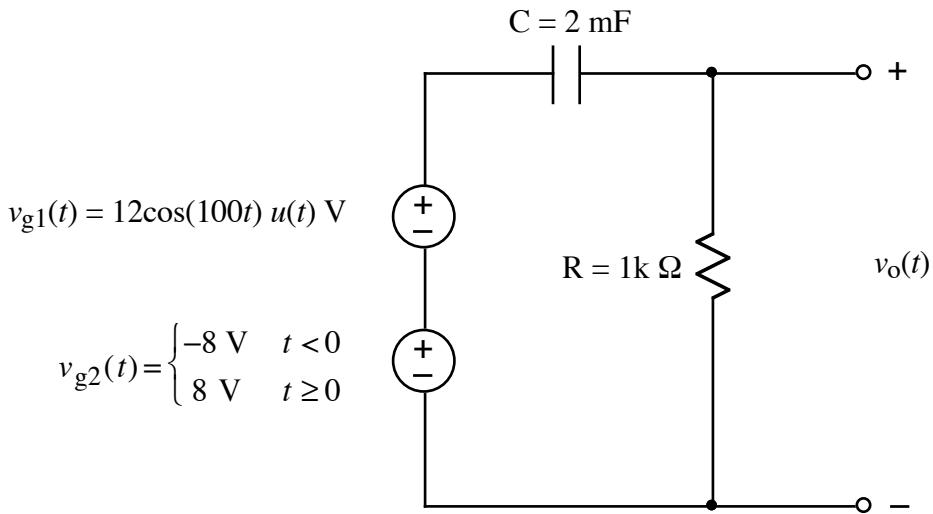


- a) Write the Laplace transform, $V_{g2}(s)$, of $v_{g2}(t)$.
- b) Draw the s -domain equivalent circuit, including sources $V_{g1}(s)$ and $V_{g2}(s)$, components, initial conditions for C , and terminals for $V_o(s)$.

4. a) For the circuit in problem 3, write an expression for $V_o(s)$.

b) Apply the final value theorem to $V_o(s)$ to find $\lim_{t \rightarrow \infty} v_o(t)$.

5.

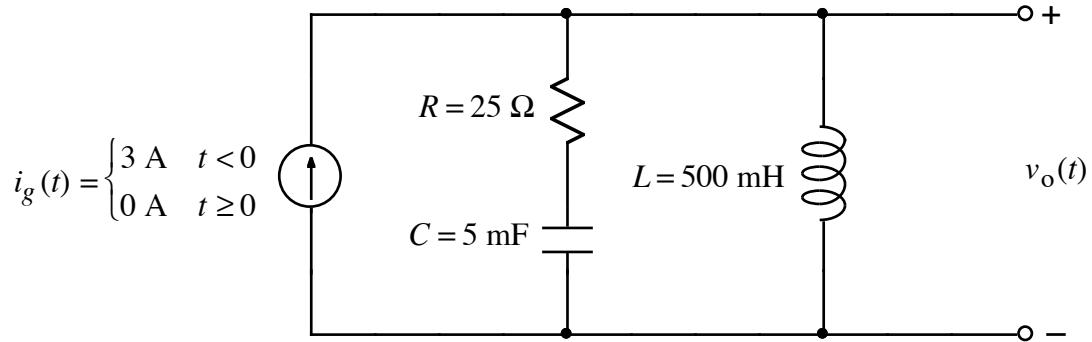


a) Write the Laplace transform $I_g(s)$ of $i_g(t)$.

b) Write the Laplace transform $V_o(s)$ of $v_o(t)$. Be sure to include the effects of initial conditions, if they are nonzero.

c) Write a numerical time-domain expression for $v_o(t)$ where $t \geq 0$.

Answers:

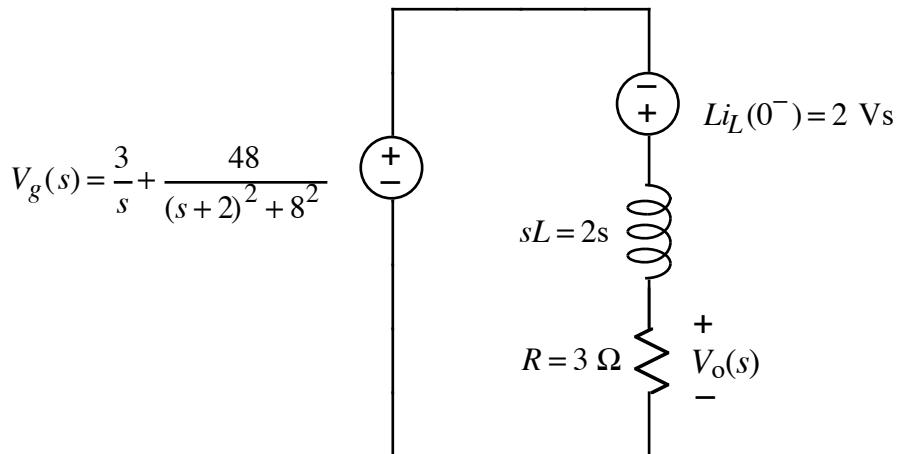1.a) $V_g(s) = \frac{3}{s} + 6 \cdot \frac{8}{(s+2)^2 + 8^2} = \frac{3}{s} + \frac{48}{(s+2)^2 + 8^2}$




b)

2.c) $V_o(s) = [V_g(s) + Li_L(0^-)] \frac{R}{sL + R} = \left[\frac{3}{s} + \frac{48}{(s+2)^2 + 8^2} + 2 \right] \frac{3}{2s+3}$

d) $\lim_{t \rightarrow 0^+} v_o(t) = 3 \text{ V}$

3.a) $V_{g2} = \frac{8}{s}$

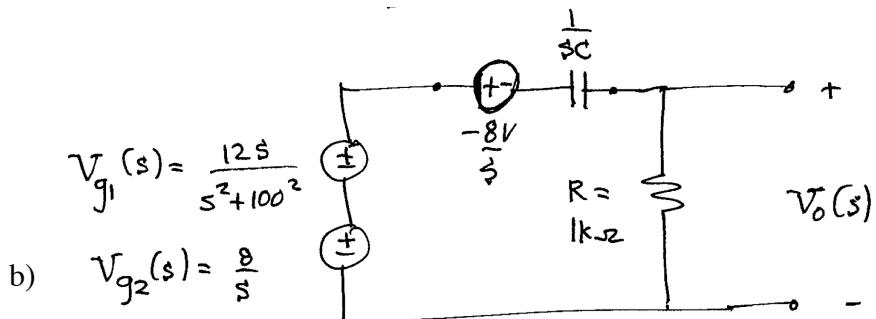

4.a) $V_o(s) = \left(\frac{8}{s} + \frac{12s}{s^2 + 100^2} - \frac{8}{s} \right) \frac{R}{R + \frac{1}{sC}}$

b) Thm does not apply because we have poles on the imaginary axis (solution oscillates forever).

5.a) $I_g(t) = \mathcal{L}\{i_g(t)\} = \mathcal{L}\{0\}A = 0 \text{ A}$

b) $V_o(s) = -75V \frac{s+8}{(s+10)(s+40)}$

c) $v_o(t \geq 0) = [5e^{-10t} - 80e^{-40t}]u(t) \text{ V}$