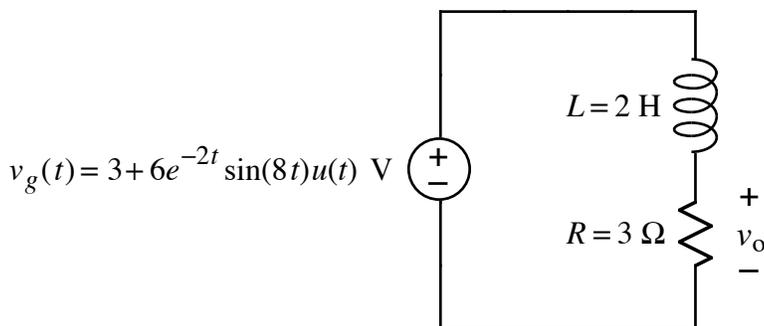


Ex:



**Note:** The 3 V in the  $v_g(t)$  source is always on.

- Write the Laplace transform,  $V_g(s)$ , of  $v_g(t)$ .
- Draw the  $s$ -domain equivalent circuit, including source  $V_g(s)$ , components, initial conditions for  $L$ , and terminals for  $V_o(s)$ .
- Write an expression for  $V_o(s)$ .
- Apply the initial value theorem to find  $\lim_{t \rightarrow 0^+} v_o(t)$ .


**SOL'N:** a) We treat the 3V as  $3u(t)$ :

$$V_g(s) = \frac{3}{s} + 6 \cdot \frac{8}{(s+2)^2 + 8^2} = \frac{3}{s} + \frac{48}{(s+2)^2 + 8^2}$$

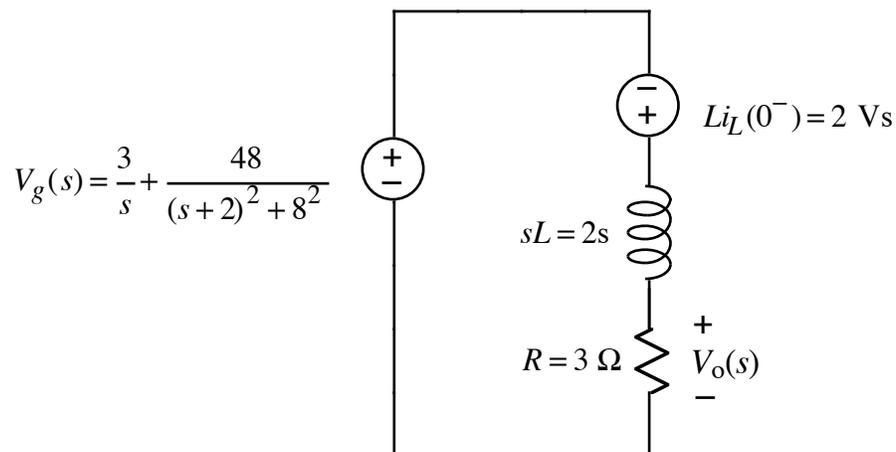- b) We find initial conditions by considering the circuit at  $t = 0^-$ . The source at that time is a constant 3V, and the  $L$  acts like a wire.

$$i_L(t = 0^-) = \frac{3\text{V}}{3\Omega} = 1\text{A}$$

For convenience, we use a series voltage source of value  $Li_L(0^-)$  for the initial conditions on the  $L$ :



---

c) We have a voltage-divider driven by the sum of the voltage sources:

$$V_o(s) = [V_g(s) + Li_L(0^-)] \frac{R}{sL + R} = \left[ \frac{3}{s} + \frac{48}{(s+2)^2 + 8^2} + 2 \right] \frac{3}{2s+3}$$

d) We use the initial value theorem:

$$\lim_{t \rightarrow 0^+} v_o(t) = \lim_{s \rightarrow \infty} sV_o(s) = \lim_{s \rightarrow \infty} s \left[ \frac{3}{s} + \frac{48}{(s+2)^2 + 8^2} + 2 \right] \frac{3}{2s+3}$$

We multiply through by  $s$ :

$$\lim_{s \rightarrow \infty} sV_o(s) = \lim_{s \rightarrow \infty} \left[ 3 + \frac{48s}{(s+2)^2 + 8^2} + 2s \right] \frac{3}{2s+3}$$

We need a polynomial over a polynomial so we can identify the highest power of  $s$  on the top and bottom:

$$\lim_{s \rightarrow \infty} sV_o(s) = \lim_{s \rightarrow \infty} \left[ \frac{[3+2s][(s+2)^2 + 8^2] + 48s}{(s+2)^2 + 8^2} \right] \frac{3}{2s+3}$$

The result is as follows:

$$\lim_{s \rightarrow \infty} sV_o(s) = \frac{2s^3}{s^2} \cdot \frac{3}{2s} = 3$$

The above is the same as what we seek:

$$\lim_{t \rightarrow 0^+} v_o(t) = 3 \text{ V}$$