

EX: Given $\omega = 10\text{k rad/s}$, for each of the following impedances, determine which of the following the impedance is from: a capacitor, an inductor, or a resistor. Also, find the value of that capacitor, inductor, or resistor. Recall that $z_R = R$, $z_L = j\omega L$, and $z_C = 1/j\omega C$.

- a) $j40 \Omega$
- b) $-j1 \text{ k}\Omega$
- c) $2 \text{ k}\Omega$
- d) $j8 \text{ k}\Omega$
- e) $-j100 \text{ k}\Omega$

SOL'N: a) A purely imaginary and positive value of impedance originates from an inductor, and the value of the impedance in the frequency-domain is proportional to the inductor in the time-domain.

$$z_L = j\omega L$$

or

$$j40 \Omega = j\omega L$$

or

$$L = \frac{j40 \Omega}{j10\text{k r/s}} = 4 \text{ mH}$$

b) A purely imaginary and negative value of impedance originates from a capacitance, and the value of the impedance in the frequency-domain is inversely proportional to the capacitance in the time-domain.

$$z_C = \frac{1}{j\omega C}$$

or

$$-j1 \text{ k}\Omega = \frac{1}{j10\text{k r/s} \cdot C}$$

or

$$C = \frac{1}{(j10\text{ k r/s})(-j1\text{ k}\Omega)} = \frac{1}{10\text{M}}\text{F} = 0.1\text{ }\mu\text{F}$$

- c) A real value of impedance originates from a resistance, and the value of the impedance in the frequency-domain is the same as the resistance in the time-domain.

$$R = 2\text{ k}\Omega$$

- d) This impedance is 200 times as high as that in part (b). This requires an inductance that is 200 times *larger*.

$$L = 200(4\text{ mH}) = 800\text{ mH} = 0.8\text{ H}$$

- e) This impedance is 0.1 times as high as that in part (b). This requires a capacitance that is 10 times *larger*.

$$C = 1\text{ }\mu\text{F}$$