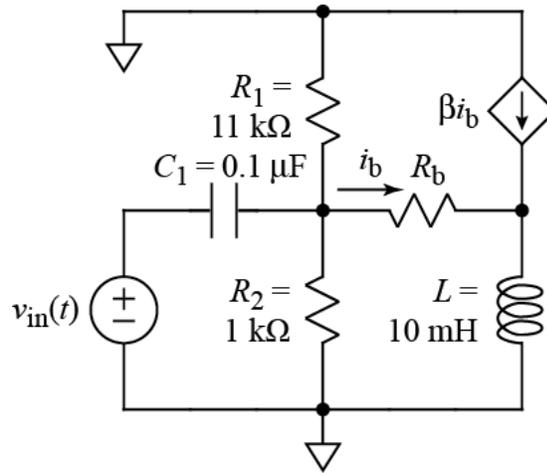




1. The circuit shown below is the small-signal model of an emitter follower incorporating an npn transistor (modeled by R_b and source βi_b). The input voltage in practice would be something like a music waveform. The capacitor couples the input to the input of the transistor, which is biased by R_1 and R_2 and a DC power supply that disappears in the small-signal model, (think superposition). The L represents a speaker coil (which has an impedance value that will look familiar to those who have worked with audio systems).



Note: $v_{in}(t) = 300 \cos(800t) \text{ mV}$

- a) The value of R_b for the small-signal model is found by linearizing the current-versus-voltage curve for a diode in the npn transistor. The equation for the diode is as follows:

$$i_D = I_0 \left(e^{v_D/v_T} - 1 \right)$$

where $I_0 = 0.010 \text{ pA}$ is the reverse saturation current of the diode

$$v_T = kT/q = 26 \text{ mV at room temperature}$$

$$v_D = \text{voltage across diode}$$

$$i_D = \text{current in diode}$$

The above values are deduced from a data sheet for a standard 1N914 diode (rather than an npn transistor). The URL for the diode data is <http://www.mouser.com/ds/2/149/1N914-192459.pdf>.


The formula for R_b is based on the slope of the nonlinear diode equation at an operating point of 0.7 V across the diode:

$$R_b = \frac{1}{\left. \frac{di_D}{dv_D} \right|_{v_D=0.70 \text{ V}}}$$


Using the above formula, find the value of R_b .

- b) Draw the frequency-domain circuit diagram (with numerical values for impedances and phasors [except the dependent source which is a multiple of the dependent variable]) for the circuit shown above.

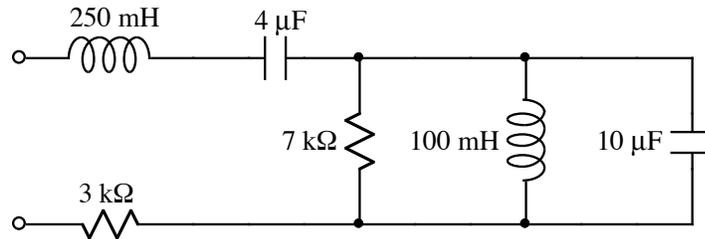
2. a) Find the total impedance of the circuitry shown below if $\omega = 1000 \text{ rad/s}$.



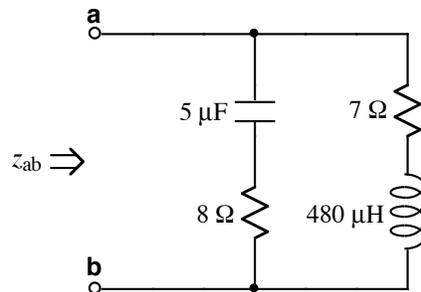- b) Given $\omega = 50 \text{ k rad/s}$, find z_{ab} .




- 3.

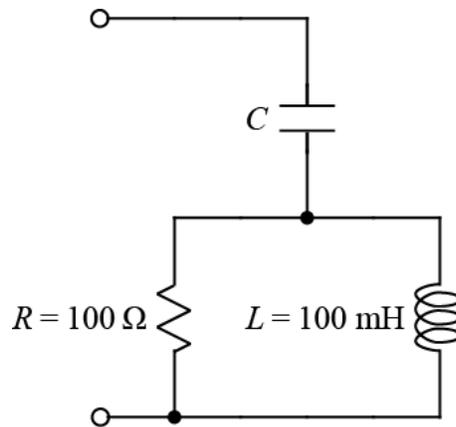

Given $\omega = 7 \text{ k rad/s}$, Find the value of C that makes the total impedance of the above circuit real. You may round off the value of C to the nearest standard value.

4.

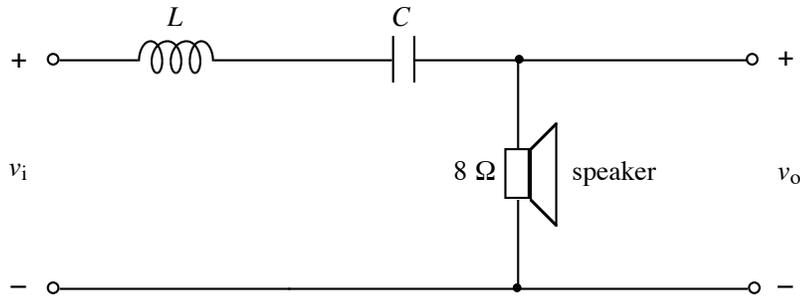

The above circuit is part of a simple crossover network for driving a midrange speaker having an impedance of 8Ω . The circuit is described at the following web site: <http://www.termpro.com/articles/xover2.html>. A more in-depth discussion of crossover networks may be found at <http://sound.westhost.com/lr-passive.htm>.


The web site describing the above bandpass filter suggests using cutoff frequencies of $f_{C1} = 130$ Hz and $f_{C2} = 4$ kHz. This results in the following values of L and C .

$$L = 330 \mu\text{H}$$

$$C = 150 \mu\text{F}$$

Plot $|V_o/V_i|$ versus ω .

5.

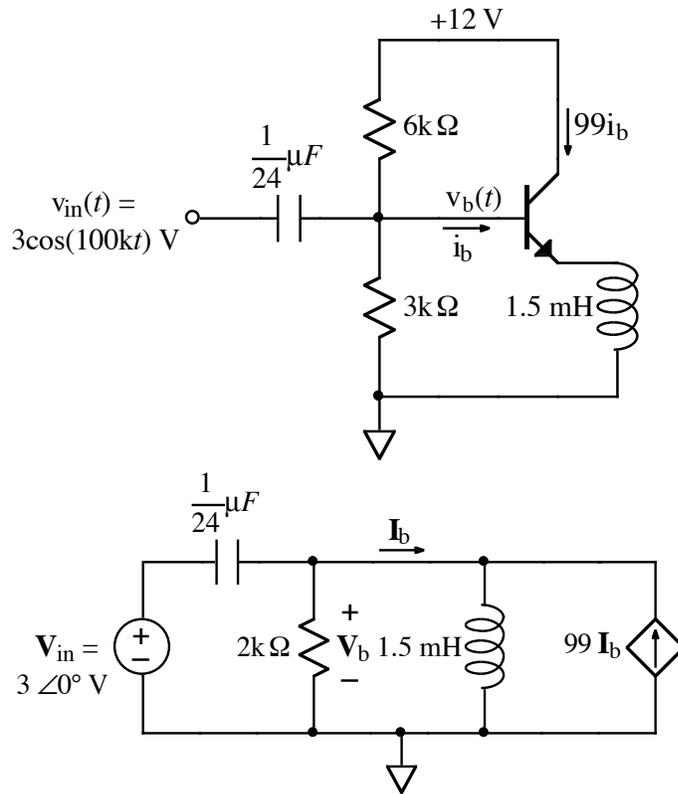

The above circuit diagrams show an emitter-follower amplifier and its high-frequency equivalent circuit. Find $v_b(t)$.


Answers:

1.a) $R_b = 5.28 \Omega$ b) $z_C = -j12.5k \Omega$, $z_L = j8 \Omega$, $V_{in} = 300 \angle 0^\circ \text{mV}$

2.a) $z_{tot} = 10 k\Omega$ b) $z_{ab} = 4\sqrt{5} \angle -6^\circ \Omega$

3. $C = 10 \mu\text{F}$

4.

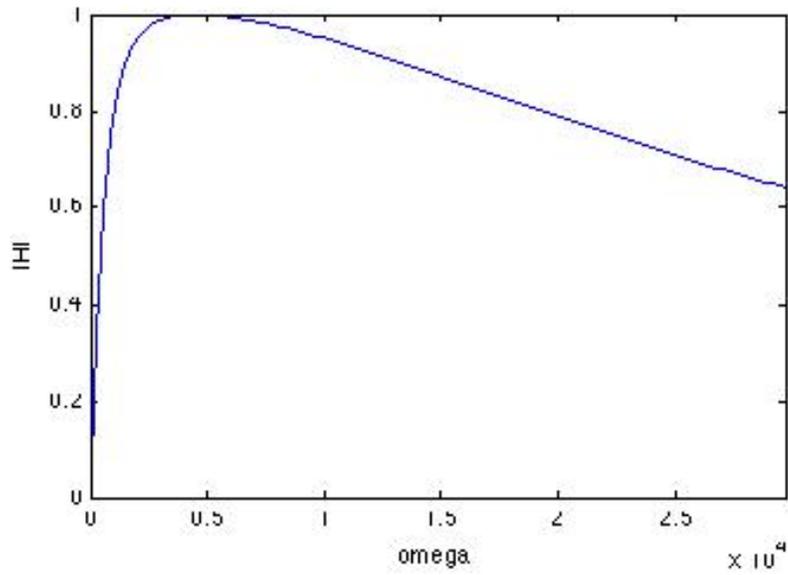

5. $v_b(t) \approx 3 \cos(100kt + 7^\circ) \text{V}$