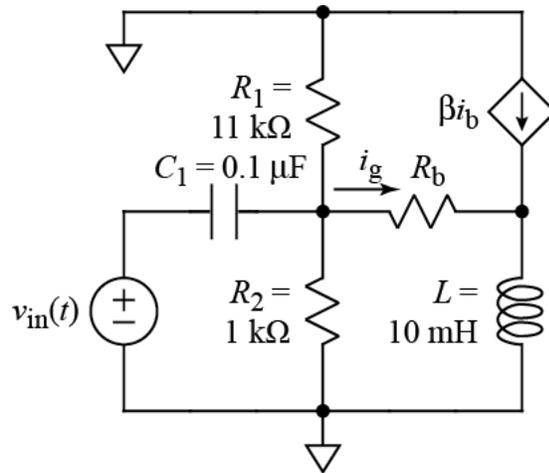


Ex: The circuit shown below is the small-signal model of an emitter follower incorporating an npn transistor (modeled by R_b and source βi_b). The input voltage in practice would be something like a music waveform. The capacitor couples the input to the input of the transistor, which is biased by R_1 and R_2 and a DC power supply that disappears in the small-signal model, (think superposition). The L represents a speaker coil (which has an impedance value that will look familiar to those who have worked with audio systems).



Note: $v_{in}(t) = 300 \cos(800t) \text{ mV}$

- a) The value of R_b for the small-signal model is found by linearizing the current-versus-voltage curve for a diode in the npn transistor. The equation for the diode is as follows:

$$i_D = I_0 \left(e^{v_D/v_T} - 1 \right)$$

where $I_0 = 0.010 \text{ pA}$ is the reverse saturation current of the diode

$$v_T = kT/q = 26 \text{ mV at room temperature}$$

$v_D =$ voltage across diode

$i_D =$ current in diode

The above values are deduced from a data sheet for a standard 1N914 diode (rather than an npn transistor). The URL for the diode data is <http://www.mouser.com/ds/2/149/1N914-192459.pdf>.

The formula for R_b is based on the slope of the nonlinear diode equation at an operating point of 0.7 V across the diode:

$$R_b = \frac{1}{\left. \frac{di_D}{dv_D} \right|_{v_D=0.70 \text{ V}}}$$

Using the above formula, find the value of R_b .

- b) Draw the frequency-domain circuit diagram (with numerical values for impedances and phasors [except the dependent source which is a multiple of the dependent variable]) for the circuit shown above.

SOL'N: a) The derivative is just the derivative of an exponential function, since the -1 is a constant with respect to v_D .

$$\left. \frac{di_D}{dv_D} \right|_{v_D=0.70 \text{ V}} = \left. \frac{dI_0 (e^{v_D/v_T} - 1)}{dv_D} \right|_{v_D=0.70 \text{ V}}$$

The derivative must be found before plugging in numbers. Otherwise, we would be differentiating a number and would get zero. Our derivative is like finding d/dx of Ae^{ax} , which gives aAe^{ax} .

$$\left. \frac{di_D}{dv_D} \right|_{v_D=0.70 \text{ V}} = \frac{1}{v_T} I_0 e^{v_D/v_T} \Big|_{v_D=0.70 \text{ V}}$$

Now that the derivative has been found, we may plug in values:

$$\left. \frac{di_D}{dv_D} \right|_{v_D=0.70 \text{ V}} = \frac{1}{26 \text{ mV}} (0.010 \text{ pA}) e^{0.70 \text{ V}/26 \text{ mV}} \approx 189.5 \text{ m}\Omega^{-1}$$

We now take the inverse, $(1/x)$, to get the small-signal resistance value.

$$R_b = \frac{1}{\left. \frac{di_D}{dv_D} \right|_{v_D=0.70 \text{ V}}} \approx \frac{1}{189.5 \text{ }\Omega^{-1}} \approx 5.28 \text{ }\Omega$$

b) In the frequency-domain, we use phasors for voltages and currents, and impedances for resistors, capacitors, and inductors.

The phasor transform is captured by the following equation:

$$P[A \cos(\omega t + \phi)] = Ae^{j\phi} \equiv A \angle \phi$$

We apply this equation to v_s and i_s using the same units in the frequency-domain as in the time-domain. The circuit diagram, below, shows the values.

The impedances are calculated with the following formulas:

$$z_R = R \qquad z_L = j\omega L \qquad z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

The value of $\omega = 800$ r/s is found in $v_{in}(t)$. Frequency domain circuit values are shown on the circuit diagram below. We may save some effort by noting that doubling the value of L increases the impedance by a factor of two, whereas doubling the value of C decreases the impedance by a factor of two.

