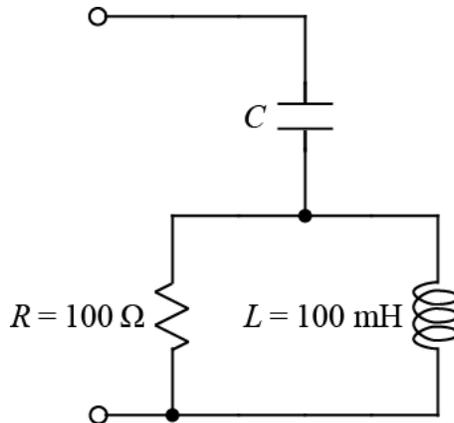



Ex:



Given  $\omega = 7\text{k rad/s}$ , Find the value of  $C$  that makes the total impedance of the above circuit real. You may round off the value of  $C$  to the nearest standard value.

**SOL'N:** We compute the impedance of the inductor and consider the frequency domain circuit shown below.
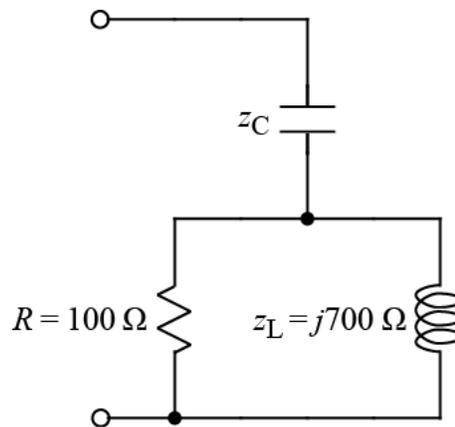
$$z_L = j\omega L = j7\text{kr/s} (100\text{mH}) = j700 \Omega$$



We compute the total impedance of the circuit and express it in  $a + jb$  form so that we can set the imaginary part, i.e.  $b$ , to zero.

$$z_{\text{Tot}} = \frac{1}{j\omega C} + R \parallel j\omega L = -j\frac{1}{\omega C} + \frac{j\omega LR}{R + j\omega L}$$

We rationalize the parallel impedance term to we can eliminate the imaginary part in its denominator.

$$z_{\text{Tot}} = -j\frac{1}{\omega C} + \frac{j\omega LR}{R + j\omega L} \frac{R - j\omega L}{R - j\omega L} = -j\frac{1}{\omega C} + \frac{-\omega^2 L^2 R + j\omega LR^2}{R^2 + (\omega L)^2}$$

---

or

$$z_{\text{Tot}} = -j \frac{1}{\omega C} + \frac{-\omega^2 L^2 R}{R^2 + (\omega L)^2} + j \frac{\omega L R^2}{R^2 + (\omega L)^2}$$

We extract the imaginary part and set it to zero.

$$\text{Im}[z_{\text{Tot}}] = -\frac{1}{\omega C} + \frac{\omega L R^2}{R^2 + (\omega L)^2} = 0$$

Now we solve for  $C$ .

$$\frac{1}{\omega C} = \frac{\omega L R^2}{R^2 + (\omega L)^2}$$

Inverting both sides saves time.

$$\omega C = \frac{R^2 + (\omega L)^2}{\omega L R^2}$$

or

$$C = \frac{R^2 + (\omega L)^2}{\omega^2 L R^2} = \frac{100^2 + 700^2}{(7\text{k})^2 (100\text{m}) 100^2} \text{F}$$

or, if we remove the factor of  $100^2$  top and bottom

$$C = \frac{1 + 49}{(7\text{k})^2 (100\text{m})} \text{F} \approx \frac{49}{(7\text{k})^2 (100\text{m})} \text{F} = \frac{1}{(1\text{k})^2 100\text{m}} \text{F}$$

or

$$C \approx \frac{1}{100\text{k}} \text{F} = 10 \mu\text{F}$$