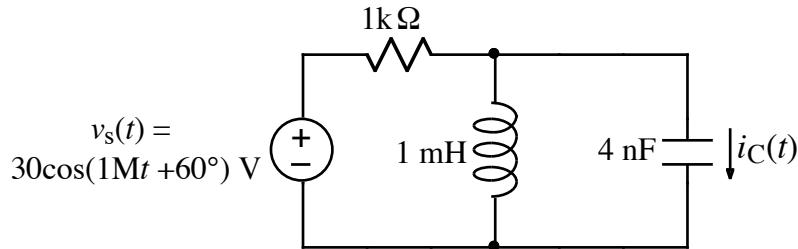



1.



- a) Find the phasor value for  $v_s(t)$ .
- b) Draw the frequency-domain circuit diagram, including the phasor value for  $v_s(t)$  and impedance values for components.

2. Find the phasor value for  $i_C(t)$ .


3.

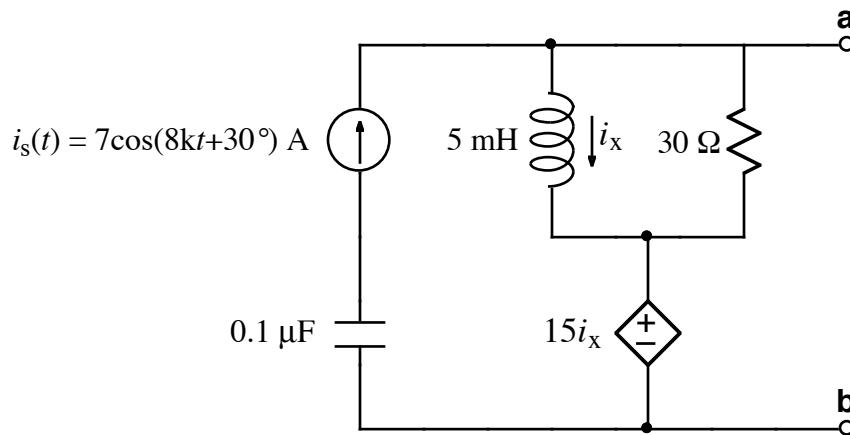

Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for  $i_s(t)$ , and show numerical impedance values for R, L, and C. Label the dependent source appropriately.

- 4. Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for  $\mathbf{V}_{Th}$  and the numerical rectangular form for the impedance value of  $z_{Th}$ .

5.

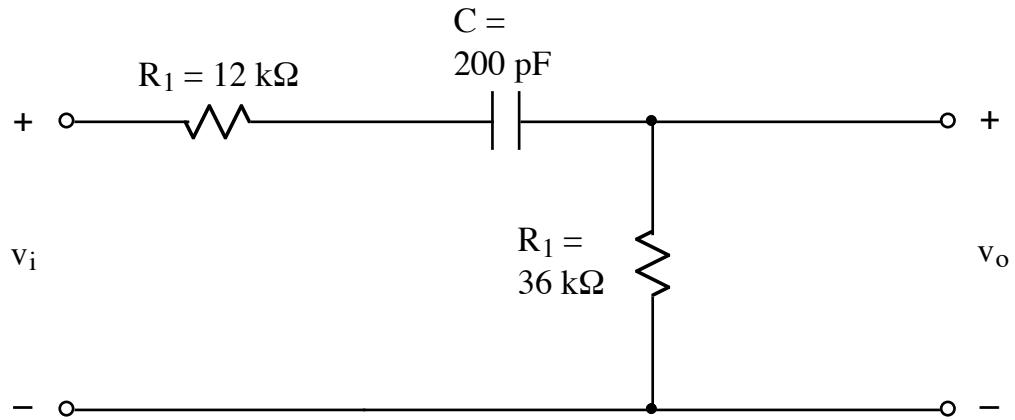

Note: vertical resistor should be labeled  $R_2$ .


- Determine the transfer function  $V_o/V_i$ . **Hint:** Reverse the order of  $R_1$  and  $C$ , and suppose the output were tapped from the point between  $C$  and  $R_1$ . Then use a voltage divider.
- Plot  $|V_o/V_i|$  versus  $\omega$ .
- Find the cutoff frequency,  $\omega_c$ .

Answers:


1.a)  $\mathbf{V}_{in} = 30\angle 60^\circ \text{V}$     b)  $z_C = -250 \Omega, z_L = j1k \Omega$     c)  $\mathbf{I}_C = 12\sqrt{10}\angle 78.4^\circ \text{mA}$

2.  $i_C(t) = 12\sqrt{10} \cos(1Mt + 78.4^\circ) \text{mA}$

3.

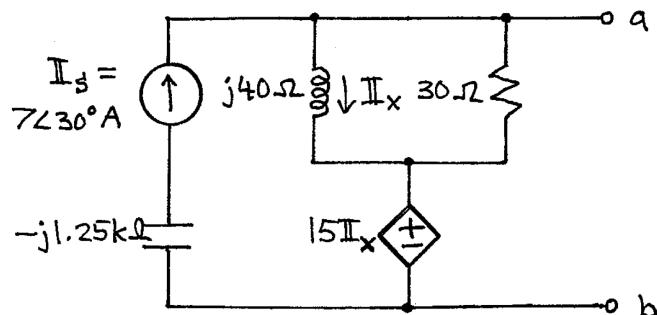


4.

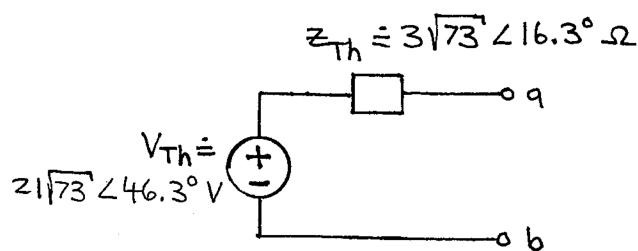

5.a)  $H(j\omega) \equiv \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 - j \frac{1}{\omega(R_1 + R_2)C}}$

b)

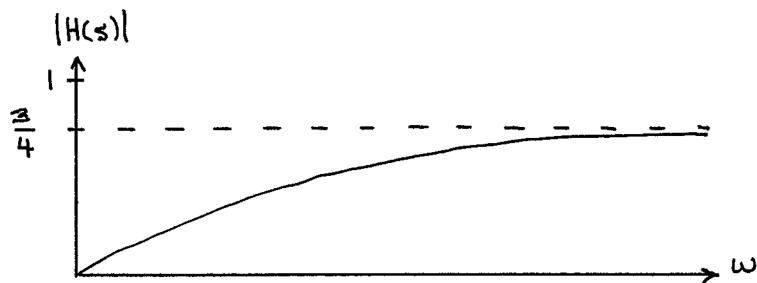

c)  $\omega_C = 104 \text{ kr/s}$