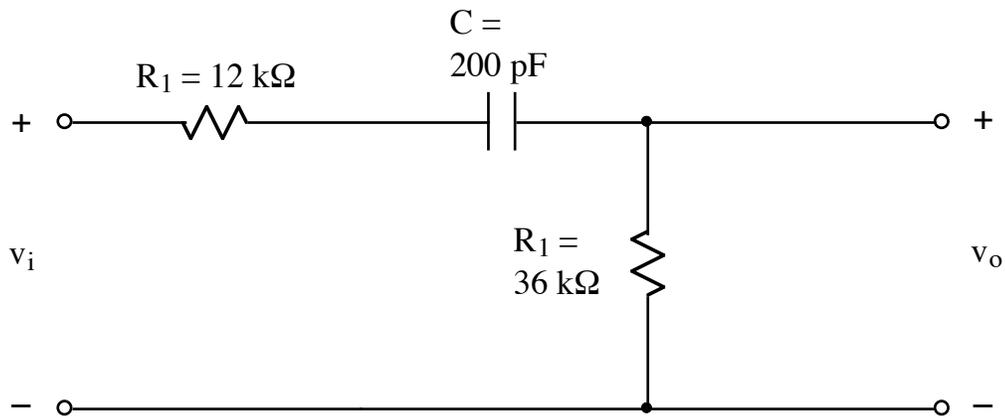


Ex:




Note: vertical resistor should be labeled R_2 .

- Determine the transfer function V_o/V_i . **Hint:** Reverse the order of R_1 and C , and suppose the output were tapped from the point between C and R_1 . Then use a voltage divider.
- Plot $|V_o/V_i|$ versus ω .
- Find the cutoff frequency, ω_c .

sol'n: a) We can switch the order of R_1 and C without changing $H(s) \equiv V_o(s)/V_i(s)$.

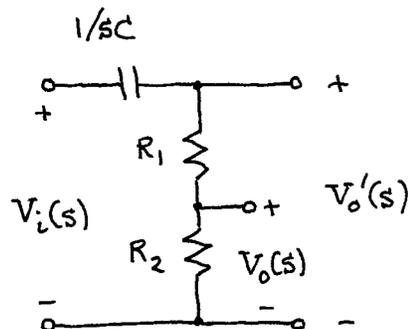We then consider taking the output, v_o' , from between C and R_1 .



We observe that $V_o(s) = V_o'(s) \cdot \frac{R_2}{R_1 + R_2}$.

$$\text{Thus, } H(s) \equiv \frac{V_o(s)}{V_i(s)} = H'(s) \cdot \frac{R_2}{R_1 + R_2}$$

$$\text{where } H'(s) \equiv \frac{V_o'(s)}{V_i(s)}.$$

This is convenient since $H'(s)$ is the transfer function of an RC filter, with $R = R_1 + R_2$.

$$H'(s) = \frac{V_o'(s)}{V_i(s)} = \frac{V_i(s) \cdot (R_1 + R_2)}{V_i(s) \cdot \frac{(R_1 + R_2) + 1/sC}{s}}$$

$$= \frac{R_1 + R_2}{R_1 + R_2 + \frac{1}{sC}}$$

$$= \frac{1}{1 + \frac{1}{s(R_1 + R_2)C}}$$

$$= \frac{1}{1 - j \frac{1}{\omega(R_1 + R_2)C}}$$

$$\text{Thus, } H(s) = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 - j \frac{1}{\omega(R_1 + R_2)C}}.$$

$$b) |H(s)| = \left| \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 - j \frac{1}{\omega(R_1 + R_2)C}} \right|$$

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{\left| 1 - j \frac{1}{\omega(R_1 + R_2)C} \right|}$$

↪ Since we can write $|a \cdot b| = |a| |b|$
and $|a/b| = |a|/|b|$.

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{\sqrt{1^2 + \frac{1}{\omega^2 (R_1 + R_2)^2 C^2}}}$$

We can sketch $|H(s)|$ by finding a few key values.

$$\text{For } \omega = 0 \text{ we have } |H| = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{\sqrt{1 + \frac{1}{0}}}$$

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{\sqrt{1 + \infty}}$$

$$= \frac{R_2}{R_1 + R_2} \cdot \frac{1}{\infty}$$


$$= 0$$

$$\text{For } \omega \rightarrow \infty \text{ we have } |H| = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{\sqrt{1 + \frac{1}{\infty}}}$$

$$= \frac{R_2}{R_1 + R_2} \frac{1}{\sqrt{1+0}}$$

$$= \frac{R_2}{R_1 + R_2} \cdot 1$$
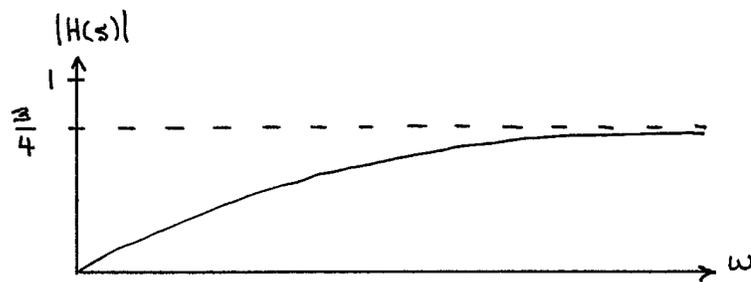
$$\text{Here, } \frac{R_2}{R_1 + R_2} = \frac{36 \text{ k}\Omega}{12 \text{ k}\Omega + 36 \text{ k}\Omega} = \frac{3}{4}$$



- c) The cutoff frequency, ω_c , is the frequency where $|H(s)| = \frac{1}{\sqrt{2}} \max_{\omega} |H(s)| = \frac{1}{\sqrt{2}} \cdot \frac{3}{4}$.

We could solve the problem this way, but it is helpful to observe that we get the same ω_c for $H'(s)$ because the factor of $\frac{3}{4}$ in $H(s)$ cancels out

$$\text{the } \frac{3}{4} \text{ in } \frac{1}{\sqrt{2}} \cdot \frac{3}{4}.$$

For $H'(s)$ we solve for ω_c where $|H'(s)| = \frac{1}{\sqrt{2}}$.

$$|H'(s)| = \frac{1}{\left| 1 - j \frac{1}{\omega_c (R_1 + R_2) C} \right|} = \frac{1}{\sqrt{2}}$$

This is equivalent to

$$\left| 1 - j \frac{1}{\omega_c (R_1 + R_2) C} \right| = \sqrt{2}$$

Since $\sqrt{1 + ja} = \sqrt{1^2 + a^2} = \sqrt{1 + a^2} = \sqrt{2}$
is solved by $a = \pm 1$, we must have

$$\frac{1}{\omega_c (R_1 + R_2) C} = \pm 1$$

$\omega_c > 0$ always, so we use +1 on the right:

$$\omega_c (R_1 + R_2) C = 1$$

or

$$\omega_c = \frac{1}{(R_1 + R_2) C} = \frac{1}{(12k + 36k) 200p} \text{ r/s}$$

$$= \frac{1}{48k \cdot 200p} \text{ r/s} = \frac{1}{9600n} \text{ r/s}$$

$$= \frac{1}{9.6 \mu} \text{ r/s} = \frac{1M}{9.6} \text{ r/s}$$

$$\omega_c \doteq 104 \text{ kr/s}$$