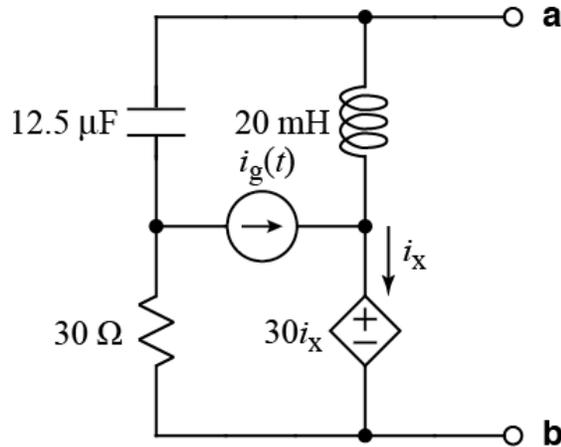


1.




$$i_g(t) = 20 \cos(2kt) \text{ A}$$

Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for  $i_g(t)$ , and show numerical impedance values for  $R$ ,  $L$ , and  $C$ . Label the dependent source appropriately.

2. Find the Thevenin equivalent (in the frequency domain) for the above circuit relative to terminals **a** and **b**. Give the numerical phasor value for  $V_{Th}$  and the numerical impedance value of  $z_{Th}$ .

3.

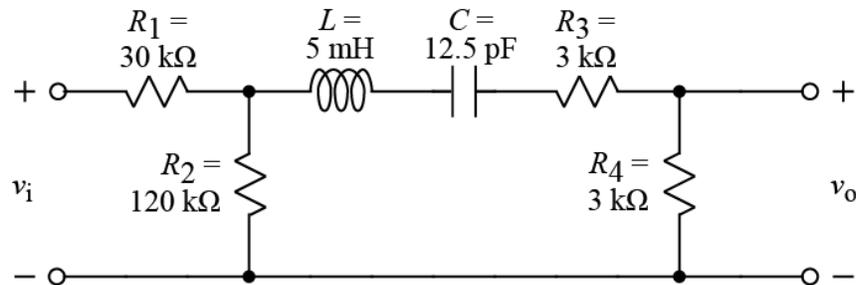

The above circuit is part of a simple crossover network for driving a midrange speaker having an impedance of  $8\Omega$ . The circuit is described at the following web site: <http://www.termpro.com/articles/xover2.html>. A more in-depth discussion of crossover networks may be found at <http://sound.westhost.com/lr-passive.htm>.



a) The above is what type of filter? (choose one of the following)  
band-pass    band-reject

b) Find the center frequency,  $\omega_0$ , of the above filter.

4. a) Find the maximum value of the gain,  $|H(j\omega)|$ , of the above filter.

b) Find the cutoff frequencies,  $\omega_{C1}$  and  $\omega_{C2}$ , of the above filter.

5.

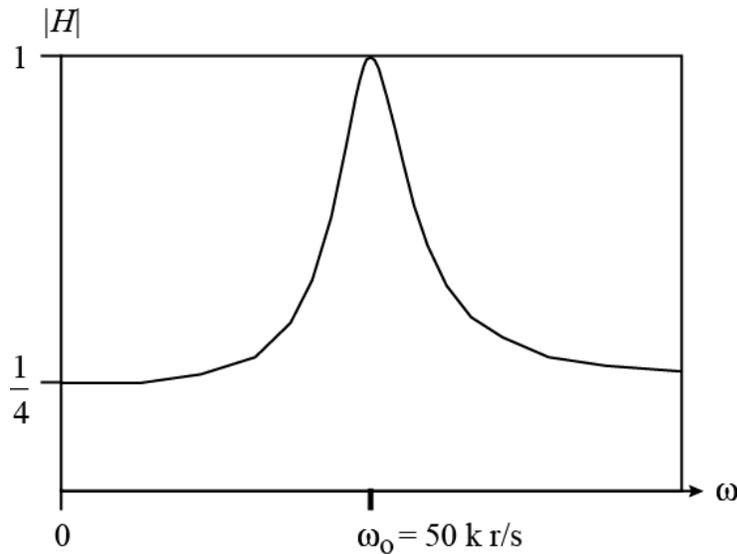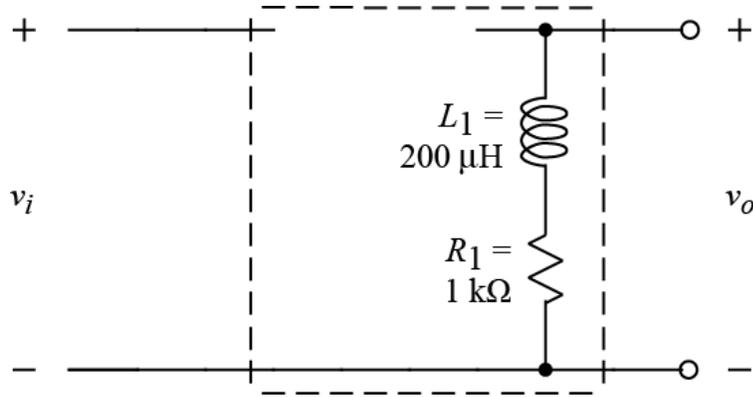

Given the resistor and inductor connected as shown with the following values,

$$R_1 = 1 \text{ k}\Omega \quad L_1 = 200 \mu\text{H}$$

and using not more than an additional one each  $R$ ,  $C$ , and  $L$  in the dashed-line box, design a circuit to go in the dashed-line box that will produce the **band-pass**  $|H(j\omega)|$  vs.  $\omega$  shown above. That is:


$$\max_{\omega} |H(j\omega)| = 1 \text{ and occurs at } \omega_0 = 50 \text{ k r/s}$$

$$|H(j\omega)| = \frac{1}{4} \text{ at } \omega = 0 \quad \text{and} \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = \frac{1}{4}$$

Specify values of  $R$ ,  $C$ , and/or  $L$ , and show how they would be connected in the circuit. Note that a bandwidth is not specified, and you do not have to satisfy any more than the three requirements specified above.

Answers:

1.

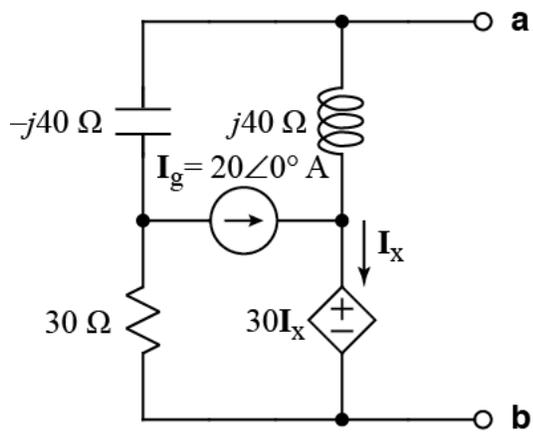

2.  $V_{Th} = -j800 \text{ V}$ ,  $z_{Th} \approx 41.67 \Omega$

3.a) **band-pass**    b)  $\omega_o = 4 \text{ Mr/s}$

4.a)  $|H(j\omega)| = 0.08$     b)  $\omega_{C1} = 2 \text{ Mr/s}$  and  $\omega_{C2} = 8 \text{ Mr/s}$

5.

