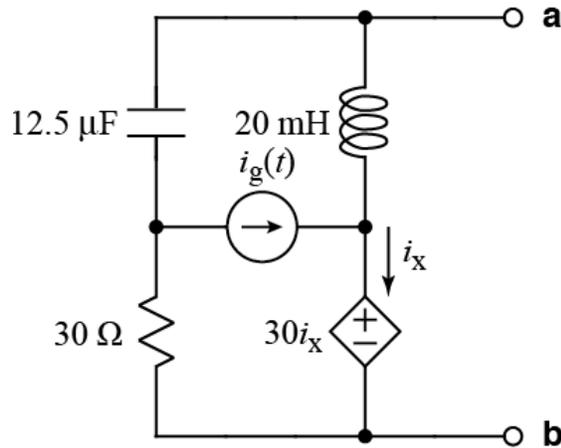


Ex:



$$i_g(t) = 20 \cos(2kt) \text{ A}$$

- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $i_g(t)$, and show numerical impedance values for R , L , and C . Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit relative to terminals **a** and **b**. Give the numerical phasor value for V_{Th} and the numerical impedance value of z_{Th} .

SOL'N: a) The phasor for the current source is a real number (no phase shift).


$$\mathbf{I}_g = 20 \angle 0^\circ \text{ A}$$

From the expression for $i_g(t)$, we see that $\omega = 2 \text{ kr/s}$. We use this to calculate the impedance of the L and C .

$$j\omega L = j2k(20\text{m}) \Omega = j40 \Omega$$


$$\frac{1}{j\omega C} = \frac{1}{j2k(12.5\mu)} \Omega = \frac{1}{j25\text{m}} = -j40 \Omega$$

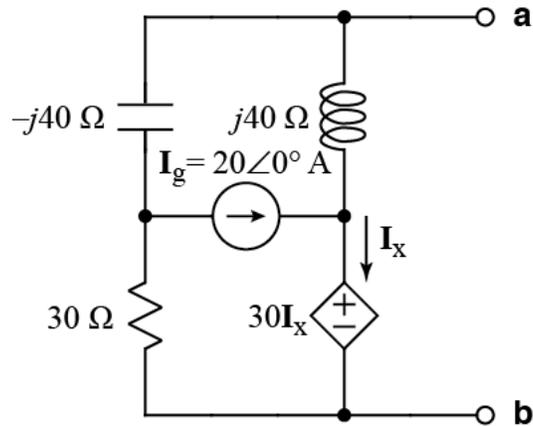The dependent source just outputs 30 times the phasor \mathbf{I}_x .



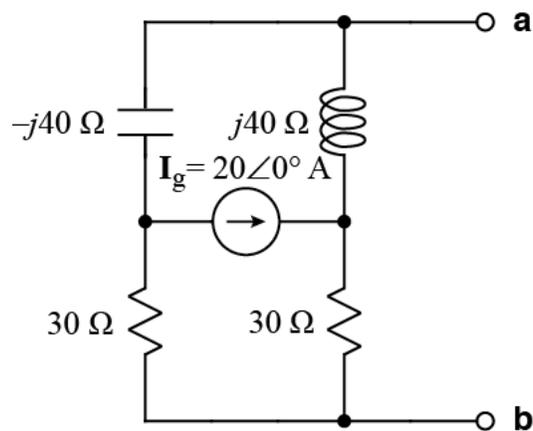- b) We may replace the dependent source with a resistance since we have both the voltage and the current in terms of the current.

$$z_{\text{eq}} = \frac{30\mathbf{I}_x}{\mathbf{I}_x} = 30 \Omega$$



The impedance in the top half of the circuit is 0Ω . Consequently, all the current from the current source will flow in the top half of the circuit, and no current will flow around the bottom half.

The Thevenin equivalent voltage is z_{ab} . The voltage drop from **a** to **b** will be the voltage drop across the bottom right 30Ω resistor, which is zero amps times 30Ω , plus the voltage drop across the top right $j40 \Omega$ impedance, which is $-\mathbf{I}_x(j40 \Omega)$.

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_{\text{ab}} = -20 \angle 0^\circ \text{ A} (j40 \Omega) = -j800 \text{ V}$$

To find the Thevenin impedance, we turn off the current source, which becomes an open circuit, and look in from the **a** and **b** terminals. We see the left and right branches in parallel.

$$z_{Th} = (30 - j40 \Omega) \parallel (30 + j40 \Omega)$$

or

$$z_{Th} = \frac{1}{\frac{1}{30 - j40 \Omega} + \frac{1}{30 + j40 \Omega}}$$

or

$$z_{Th} = \frac{1}{\frac{30 + j40}{30^2 + 40^2} + \frac{30 - j40}{30^2 + 40^2}} \Omega$$

or

$$z_{Th} = \frac{1}{\frac{30 + j40}{50^2} + \frac{30 - j40}{50^2}} \Omega$$

or

$$z_{Th} = \frac{50^2}{30 + j40 + 30 - j40} \Omega$$

or

$$z_{Th} = \frac{2500}{60} \Omega = \frac{125}{3} \Omega \approx 41.67 \Omega$$