
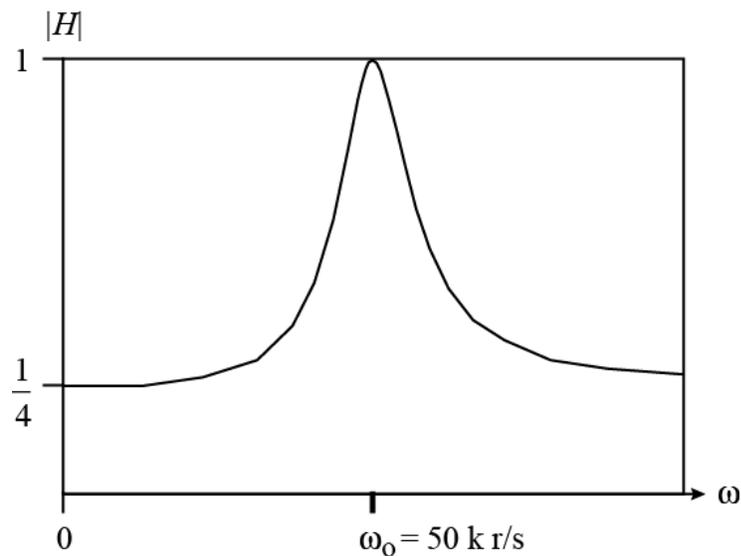


Ex:

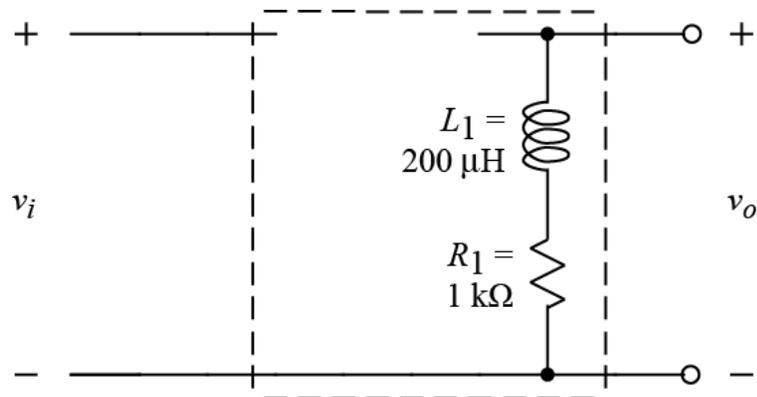

Given the resistor and inductor connected as shown with the following values,

$$R_1 = 1 \text{ k}\Omega \quad L_1 = 200 \text{ }\mu\text{H}$$

and using not more than an additional one each R , C , and L in the dashed-line box, design a circuit to go in the dashed-line box that will produce the **band-pass** $|H(j\omega)|$ vs. ω shown above. That is:

$$\max_{\omega} |H(j\omega)| = 1 \text{ and occurs at } \omega_0 = 50 \text{ k r/s}$$

$$|H(j\omega)| = \frac{1}{4} \text{ at } \omega = 0 \quad \text{and} \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = \frac{1}{4}$$

Specify values of R , C , and/or L , and show how they would be connected in the circuit. Note that a bandwidth is not specified, and you do not have to satisfy any more than the three requirements specified above.

SOL'N: If we use a series or parallel LC, our center frequency will be given by the standard formula. (Note that other configurations than a simple series or parallel LC will not necessarily obey this formula, so we need to reconsider this calculation if we choose some other configuration.)

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{200\mu \cdot C}} = 50 \text{ kr/s}$$

or

$$\omega_o^2 = \frac{1}{200\mu \cdot C} = (50 \text{ kr/s})^2$$

Rearranging, we compute the value of C .

$$C = \frac{1}{200\mu\text{H} \cdot \omega_o^2} = \frac{1}{200\mu(50\text{k})^2} \text{F} = \frac{1}{200\mu(50\text{k})(50\text{k})} \text{F}$$

or

$$C = \frac{1}{10(50\text{k})} \text{F} = 2\mu\text{F}$$

We can obtain a peak in the transfer function by having a parallel LC in the vertical segment on the right side. The LC will look like an open circuit at ω_o , meaning that the input will be connected to the output by a what is in the top rail with no current flow. This will give $\mathbf{V}_o = \mathbf{V}_i$ and $H(j\omega) = 1$.

At $\omega = 0$ and $\omega \rightarrow \infty$, the L or C will be a short circuit, and we need some resistance in the top rail to give a voltage divider such that the output voltage is 1/4 the input voltage. Thus, we need a resistor that is three times the value of R_1 .

We obtain the circuit shown below. As noted earlier, we should verify that we have a series or parallel LC. We do have a parallel LC, so our value for C is valid.

