


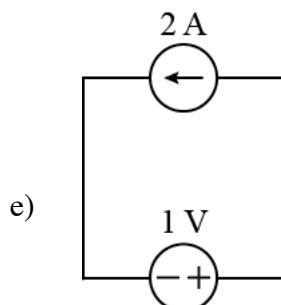
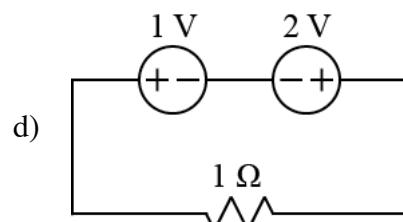
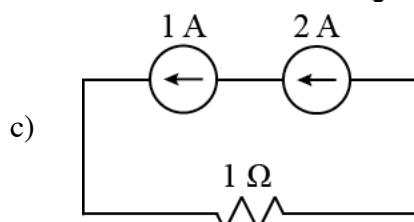


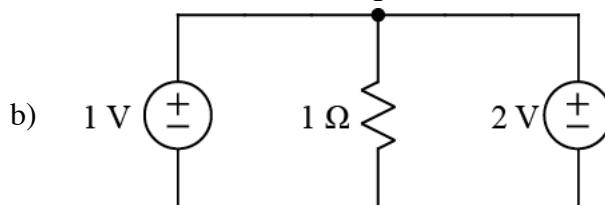

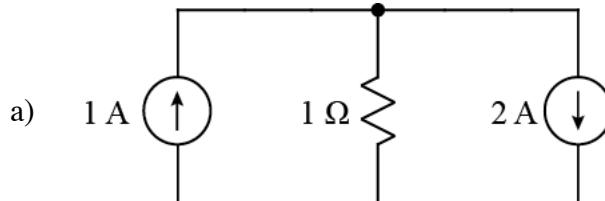1. Determine whether each of the following circuits is valid or invalid.




- 2.

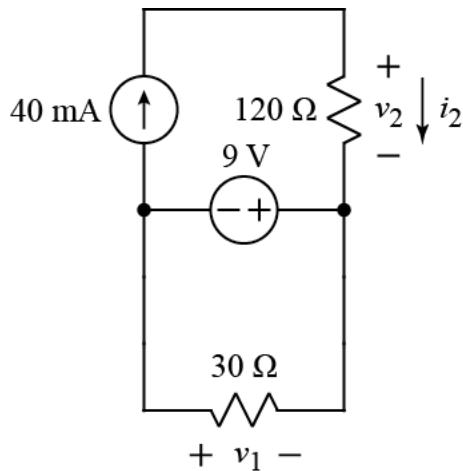


Use Kirchhoff's laws to find  $v_1$  and  $i_2$ .

3.

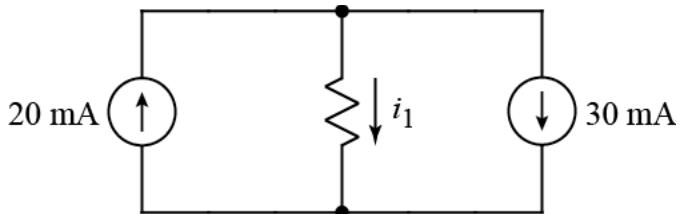


Use Kirchhoff's laws to find the value of  $i_1$ .

4.

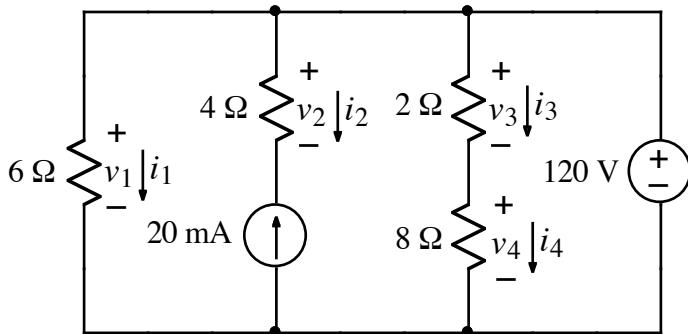

- For the circuit shown above, use Kirchhoff's laws to write equations relating voltages and currents.
- Find the value of  $v_1$  and  $i_2$ .

5.

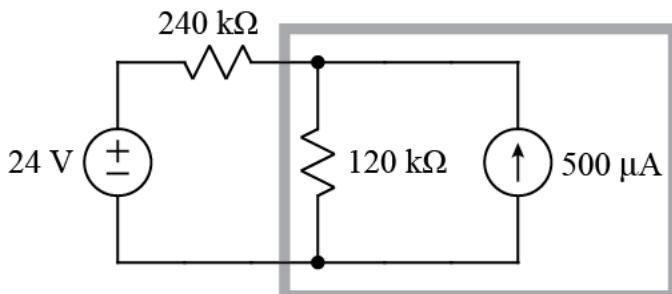

Find the total power dissipated by the components inside the box.

**ANS:** 1.a) val b) inv c) inv d) val e) val  
3.  $-10\text{ mA}$   
5.  $-4.8\text{ mW}$

2.  $v_1 = -9\text{ V}$ ,  $i_2 = 40\text{ mA}$   
4.  $v_1 = 120\text{ V}$ ,  $i_2 = -20\text{ mA}$