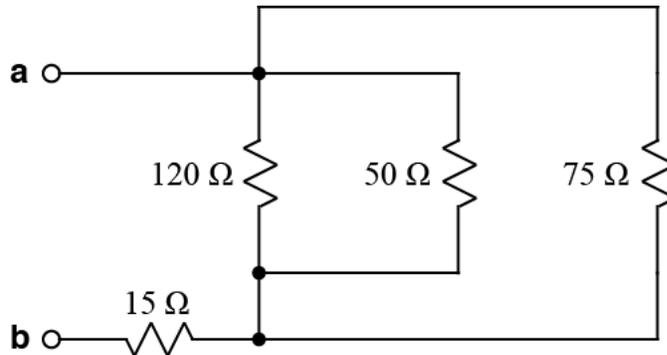


**Ex:**

Find the value of total resistance between terminals **a** and **b**.

**SOL'N:** The  $120\ \Omega$  and  $50\ \Omega$  resistors are in parallel because their opposite ends are connected directly to each other by wires. That is, they are connected by wires on the top side, and they are connected by wires on the bottom side. By the same argument, however, the  $75\ \Omega$  resistor is also in parallel with the  $120\ \Omega$  and  $50\ \Omega$  resistors. We may compute the parallel resistance in various ways, such as combining any two and using the product over sum formula—and then combining that answer with the third resistor using the product over sum formula (which is only correct for two resistors at a time). Alternatively, we may compute the parallel resistance for all three resistors at once using the sum-of-conductance formula, which works for any number of resistors. Both approaches are shown here. The product over sum approach is shown first. The  $50\ \Omega$  and  $75\ \Omega$  values are combined first because they have a large common factor:

$$50\ \Omega \parallel 75\ \Omega = 25\ \Omega \cdot 2 \parallel 3 = 25\ \Omega \cdot \frac{2 \cdot 3}{2 + 3} = 25\ \Omega \cdot \frac{6}{5} = 30\ \Omega$$

We replace the  $50\ \Omega$  and  $75\ \Omega$  resistors with a single  $30\ \Omega$  resistor, leaving  $30\ \Omega$  in parallel with  $120\ \Omega$ .

$$30\ \Omega \parallel 120\ \Omega = 30\ \Omega \cdot 1 \parallel 4 = 30\ \Omega \cdot \frac{1 \cdot 4}{1 + 4} = 30\ \Omega \cdot \frac{4}{5} = 24\ \Omega$$

We replace the  $50\ \Omega$ ,  $75$ , and  $120\ \Omega$  resistors with a single  $24\ \Omega$  resistor, leaving two resistors in series, ( $24\ \Omega$  and  $15\ \Omega$ ), whose values sum:

$$R_{ab} = 24\ \Omega + 15\ \Omega = 39\ \Omega$$

By coincidence,  $39\ \Omega$  is a standard 10% tolerance resistor value sold in the EE Stockroom.

The alternative approach using the sum of conductances proceeds as follows:

$$120\ \Omega \parallel 50\ \Omega \parallel 75\ \Omega = \frac{1}{\frac{1}{120} + \frac{1}{50} + \frac{1}{75}}$$

Multiplying top and bottom by the least common multiple of the resistances yields the parallel resistance value:

$$120\ \Omega \parallel 50\ \Omega \parallel 75\ \Omega = \frac{1\ \Omega}{\frac{1}{120} + \frac{1}{50} + \frac{1}{75}} \cdot \frac{600}{600} = \frac{600\ \Omega}{5 + 12 + 8} = \frac{600\ \Omega}{25} = 24\ \Omega$$

The calculation of the total resistance then proceeds as before by summing the series resistances to obtain  $R_{ab} = 29\ \Omega$ .