
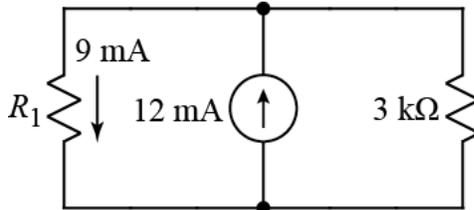


Ex:

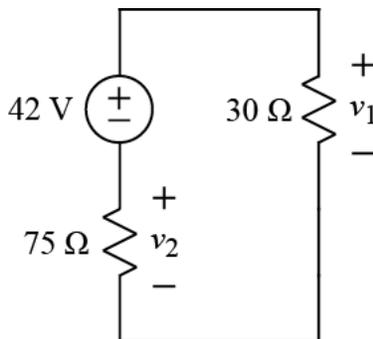

- a) Use the current-divider formula to determine what the value of R_1 must be.



- b) Use the voltage-divider formula to calculate v_1 and v_2 . (Be careful about signs.)

SOL'N: a) The two resistors are in parallel across the current source. Current flows up through the current source and back down through the two resistors. The current-divider formula gives the value of the current on the left side:

$$9 \text{ mA} = 12 \text{ mA} \cdot \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{3 \text{ k}\Omega}}$$

We wish to solve this equation for R_1 , which appears in two places. If we multiply top and bottom by R_1 , we are left with only one R_1 in the equation:

$$9 \text{ mA} = 12 \text{ mA} \cdot \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{3 \text{ k}\Omega}} \cdot \frac{R_1}{R_1} = 12 \text{ mA} \frac{1}{1 + \frac{R_1}{3 \text{ k}\Omega}}$$

Multiplying both sides by the denominator of the right side brings R_1 into the numerator.

$$9\text{ mA} \cdot \left(1 + \frac{R_1}{3\text{ k}\Omega}\right) = 12\text{ mA}$$

The remaining steps are straightforward.

$$9\text{ mA} + \frac{9\text{ mA}}{3\text{ k}\Omega} R_1 = 12\text{ mA}$$

or

$$9\text{ mA} + \frac{9\text{ mA}}{3\text{ k}\Omega} R_1 = \frac{12\text{ mA} - 9\text{ mA}}{\frac{9\text{ mA}}{3\text{ k}\Omega}} = \frac{3\text{ mA}}{3\text{ }\mu\text{A}/\Omega} = 1\text{ k}\Omega$$

NOTE: The ratio of the resistances in a current divider is the inverse of the ratio of the currents.

b) This is a standard voltage divider configuration for v_1 :

$$v_1 = 42\text{ V} \cdot \frac{30\text{ }\Omega}{30\text{ }\Omega + 75\text{ }\Omega} = 12\text{ V}$$

For v_2 , we must reverse the sign of the answer.

$$v_2 = -42\text{ V} \cdot \frac{75\text{ }\Omega}{30\text{ }\Omega + 75\text{ }\Omega} = -30\text{ V}$$

NOTE: To determine whether the sign of the answer must be reversed, trace a path from the + sign of the measurement back to the source. (Go in the direction away from the resistor and the – sign of the resistor's voltage drop.) If the path leads to the + sign of the voltage source, then all is well. If the path leads to the – side of the voltage source, then use a minus sign in your answer. Of course, "voltage source" may be any total voltage drop across series resistors. It need not be a voltage source.