
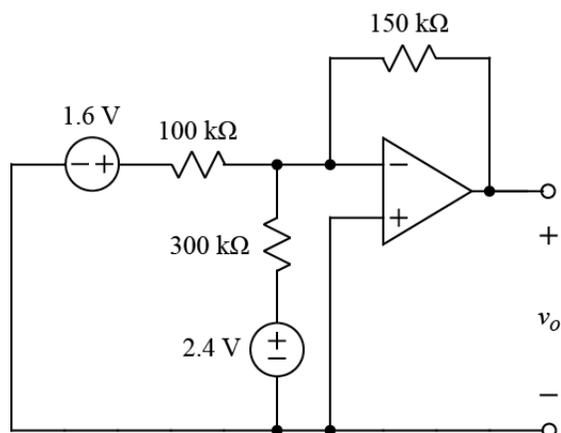


Ex:

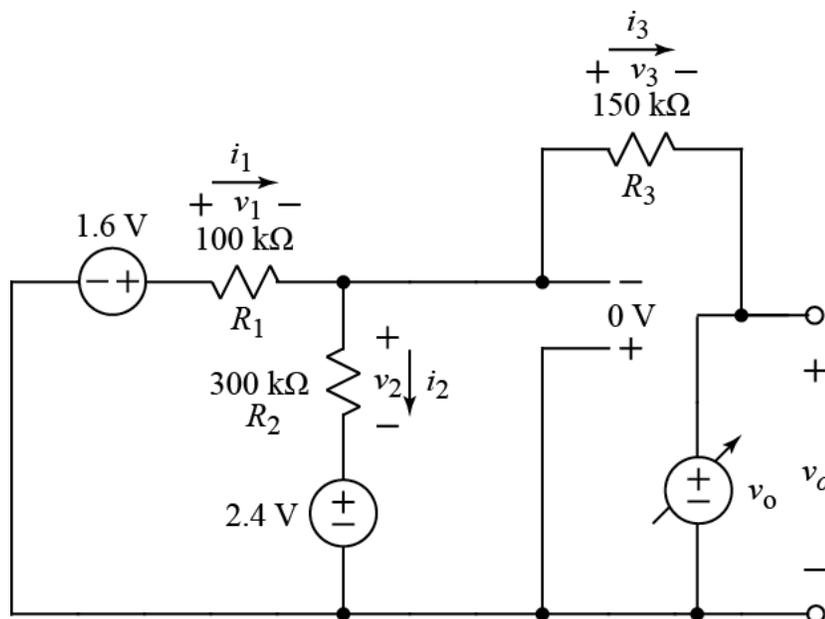

The op-amp operates in the linear mode. Using an appropriate model of the op-amp, find the value of v_o .

SOL'N: The figure below shows the circuit with one possible way of labeling voltages and currents for resistors.



There are three inner voltage loops:

$$\text{left-side: } 1.6 \text{ V} - v_1 - v_2 - 2.4 \text{ V} = 0 \text{ V}$$

$$\text{middle: } 2.4 \text{ V} + v_2 + 0 \text{ V} = 0 \text{ V}$$

$$\text{right-side: } -0 \text{ V} - v_3 - v_o = 0 \text{ V}$$

We write a current summation for the node at the $-$ input of the op-amp. Note that there is only one node where R_1 , R_2 , and R_3 meet since these R 's are connected by wires. The nodes above and below v_o are not candidates for current summations because they are connected to each other by only a voltage source.

$$i\text{-sum: } i_1 = i_2 + i_3$$

Ohm's law for the three resistors:

$$v_1 = i_1 R_1$$

$$v_2 = i_2 R_2$$

$$v_3 = i_3 R_3$$

We substitute for the voltages using the Ohm's law equations, and we eliminate i_1 using the i -sum equation.

$$\text{left-side: } 1.6 \text{ V} - (i_2 + i_3) R_1 - i_2 R_2 - 2.4 \text{ V} = 0 \text{ V}$$

$$\text{middle: } 2.4 \text{ V} + i_2 R_2 + 0 \text{ V} = 0 \text{ V}$$

$$\text{right-side: } -0 \text{ V} - i_3 R_3 - v_o = 0 \text{ V}$$

The middle-loop equation gives the value of i_2 .

$$i_2 = -\frac{2.4 \text{ V}}{R_2}$$

The middle-loop equation also says that the last two terms on the left side of the left-side equation sum to zero and may be dropped.

$$\text{left-side: } 1.6 \text{ V} - (i_2 + i_3) R_1 = 0 \text{ V}$$

Substituting for i_2 , we have the following left-side equation:

$$\text{left-side: } 1.6 \text{ V} - \left(-\frac{2.4 \text{ V}}{R_2} + i_3 \right) R_1 = 0 \text{ V}$$

Solving for i_3 :

$$\text{left-side: } 1.6 \text{ V} + \frac{2.4 \text{ V}}{R_2} R_1 - i_3 R_1 = 0 \text{ V}$$

or

$$\text{left-side: } i_3 = \frac{1.6 \text{ V} + \frac{2.4 \text{ V}}{R_2} R_1}{R_1}$$

Substituting this into the right-side equation gives the desired expression for v_o :

$$v_o = -i_3 R_3 = -\left(1.6 \text{ V} + 2.4 \text{ V} \frac{R_1}{R_2}\right) \frac{R_3}{R_1}$$

or

$$v_o = -\left(1.6 \text{ V} + 2.4 \text{ V} \frac{100 \text{ k}\Omega}{300 \text{ k}\Omega}\right) \frac{150 \text{ k}\Omega}{100 \text{ k}\Omega} = -3.6 \text{ V}$$