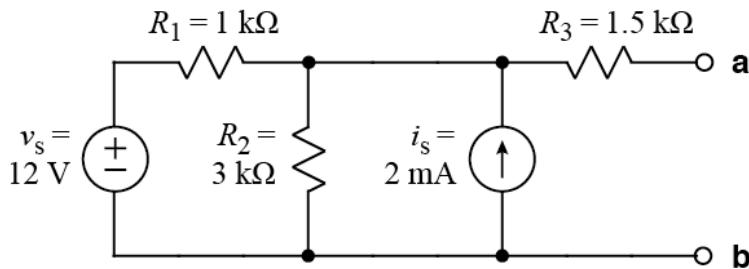


Ex:

Find the Thevenin equivalent circuit at terminals a-b.

SOL'N:

v_{Th} equals the voltage across the a, b terminals when nothing is connected from a to b.

Since no current flows in R_3 when we have nothing connected from a to b, there is no voltage drop across R_3 . Thus, v_{Th} equals the voltage at the node above R_2 and i_s . We could put a reference on the bottom of the circuit and label the top center node as v_{Th} , and we could use the node-v method to find v_{Th} :

$$\frac{v_{Th} - v_s}{R_1} + \frac{v_{Th}}{R_2} - i_s = 0 A$$

or

$$v_{Th} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_s}{R_1} + i_s$$


Multiplying both sides by $R_1 R_2$ gives

$$v_{Th} (R_2 + R_1) = v_s R_2 + i_s R_1 R_2$$


or

$$v_{Th} = \frac{v_s R_2 + i_s R_1 R_2}{R_1 + R_2} = \frac{36k + 6k}{4k} V = 10.5V$$

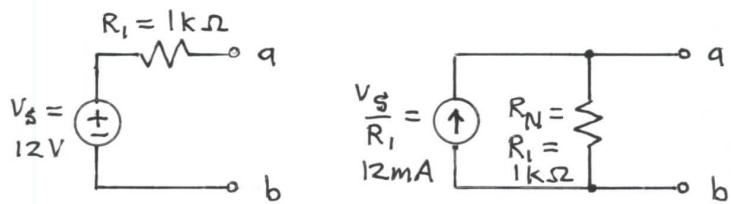
Another way to find V_{TH} is to use source transformations. V_S and R_1 on the left side are a Thevenin equivalent that we may transform into a Norton equivalent.



Our circuit now becomes the following:

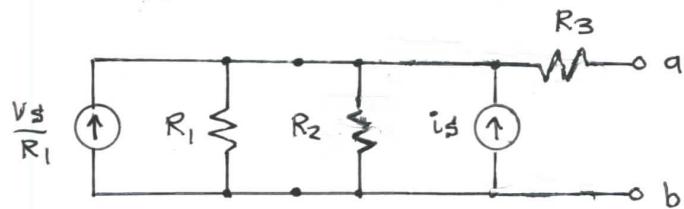

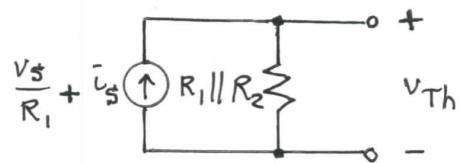Now we may combine current sources, and R_1 with R_2 . Once again, we may ignore R_3 .




$$\text{By Ohm's law, } V_{TH} = \left(\frac{V_S}{R_1} + i_S \right) R_1 \parallel R_2$$

$$\text{or } V_{TH} = \left(\frac{12V}{1k\Omega} + 2mA \right) \left(1k\Omega \parallel 3k\Omega \right) = 14mA \cdot \frac{3}{4} k\Omega$$

$$\text{or } V_{TH} = 10.5V$$

To find R_{TH} , we turn off the independent sources and look in from the a, b terminals.
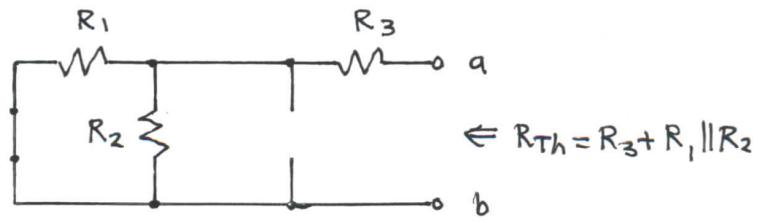
$$R_{TH} = R_3 + R_1 \parallel R_2 \quad (\text{see diagram, below})$$



Note: The voltage source becomes a wire when turned off, and the current source becomes an open when turned off. That is, $0V = \text{wire}$, $0A = \text{open}$.