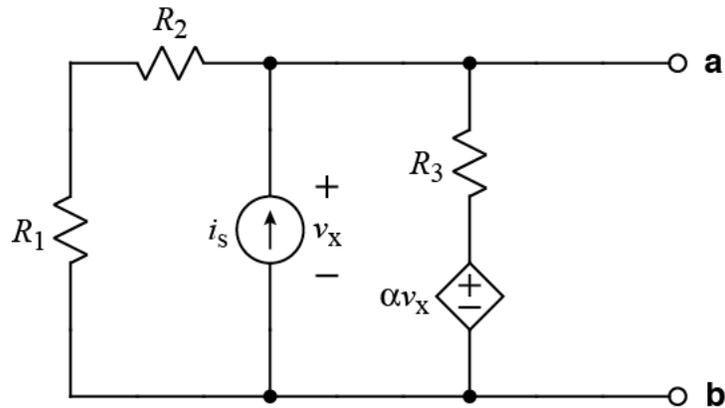




1.



Find the Thevenin equivalent circuit at terminals a-b. v_x must not appear in your solution. The expression must not contain more than circuit parameters α , R_1 , R_2 , R_3 , and i_s . **Note:** $0 < \alpha < 1$.

2.


Find the Norton equivalent of the circuit in problem 1.

3.


For the circuit in problem 1, assume the following component values:
 $i_s = 0.4 \text{ mA}$, $R_1 = 10 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 36 \text{ k}\Omega$, $\alpha = 2$

- Calculate the value of R_L that would absorb maximum power.
- Calculate that value of maximum power R_L could absorb.

4.

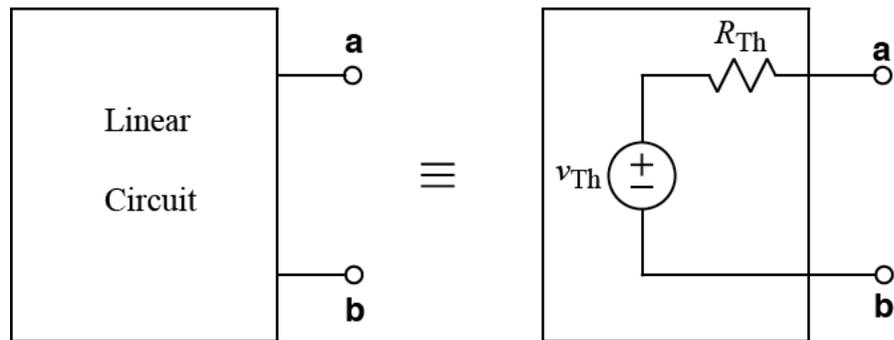


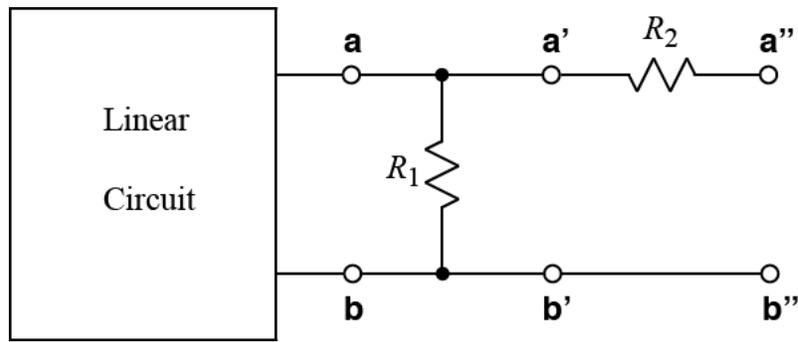A linear circuit has a Thevenin equivalent, as shown above. Now suppose that components are added to that circuit as shown below.



- a) Find the Thevenin equivalent circuit at terminals a'-b' in terms of the original v_{Th} and R_{Th} and the added R_1 . (Note that this is the circuit with only R_1 added to it.)
- b) Find the Thevenin equivalent circuit at terminals a''-b'' in terms of the original v_{Th} and R_{Th} and the added R_1 and R_2 .

5.

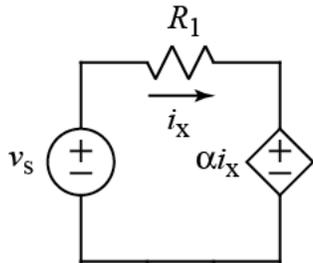

Find the equivalent resistance of the dependent source in the above circuit.

Answers:

1. $v_{Th} = i_s \cdot (R_1 + R_2) \parallel R_3 \parallel \frac{-R_3}{\alpha} = i_s \cdot R_{Th}$ 2. $i_N = i_s, R_N = R_{Th}$
3. a) $R_L = 18 \text{ k}\Omega$ b) $p_{max} = 0.72 \text{ mW}$
4. a) $v_{Th}' = v_{Th} R_1 / (R_1 + R_{Th}), R_{Th}' = R_1 \parallel R_{Th}$ b) $v_{Th}'' = v_{Th}', R_{Th}'' = R_{Th}' + R_2$
5. $R_{Eq} = \alpha$