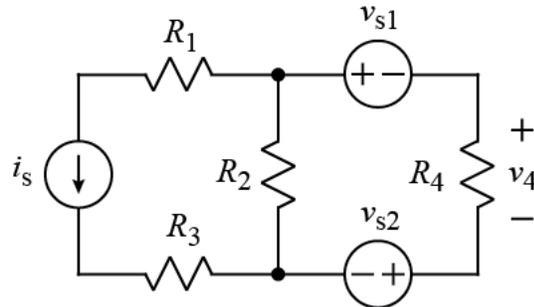





1.




Using superposition, derive an expression for v_4 that contains no circuit quantities other than i_s , v_{s1} , v_{s2} , R_1 , R_2 , R_3 , and R_4 .

2.

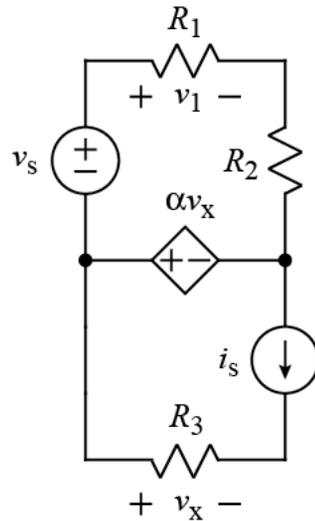

Using superposition, derive an expression for v_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , R_3 , and α , where $\alpha > 0$.

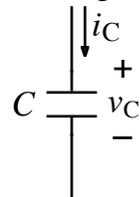
3. In (a) and (b), the voltage $v_C(t)$ across a 30 nF capacitor is listed. Find the current, $i_C(t)$, flowing in the capacitor in each case as a function of time:



a) $v_C(t) = 0 \text{ V}$

b) $v_C(t) = 4 \text{ V} + \frac{5V_s}{1s+t}$

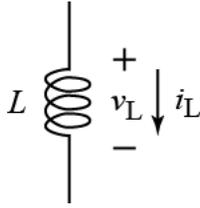4. In (a) and (b), the current $i_L(t)$ flowing into a $20 \mu\text{H}$ inductor is listed. Find the voltage, $v_L(t)$, across the inductor in each case as a function of time:



- a) $i_L(t) = 5 \text{ mA}$
 b) $i_L(t) = 5e^{-t/20\text{ms}} \text{ mA}$
5. a) The following equation describes the current, i_C , through a capacitor as a function of time. Find an expression for the voltage, $v_C(t)$, across the capacitor as a function of time. Assume that $v_C(t = 0) = 2 \text{ V}$ and $C = 1 \mu\text{F}$.
- $$i_C(t) = 5e^{-t/8\text{ms}} \text{ mA}$$
- b) Using your answer to (a), find the time, t , at which v_C is equal to 40 V .

Answers:

$$1. v_4 = \frac{-i_s R_2 R_4 - (v_{s1} + v_{s2}) R_4}{R_2 + R_4} \quad 2. v_1 = \frac{v_s R_1 - \alpha i_s R_1 R_3}{R_1 + R_2}$$

$$3. \text{a) } i_C = 0 \text{ A} \quad \text{b) } i_C = -\frac{150}{(1+t/s)^2} \text{ nA}$$

$$4. \text{a) } v_L = 0 \text{ V} \quad \text{b) } v_L = -5e^{-t/20\text{ms}} \mu\text{V}$$

$$5. \text{a) } v_C(t) = 1\text{M/F} \int_0^t 5e^{-t/8\text{ms}} \text{ mA} dt + 2 \text{ V} \quad (\text{compute the integral}) \quad \text{b) } t \approx 24 \text{ ms}$$