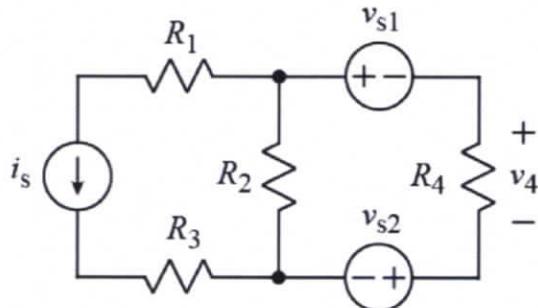



Ex:



Using superposition, derive an expression for v_4 that contains no circuit quantities other than i_s , v_{s1} , v_{s2} , R_1 , R_2 , R_3 , and R_4 .


Sol'n: We turn on one independent source at a time. We find v_4 for each circuit and sum them.

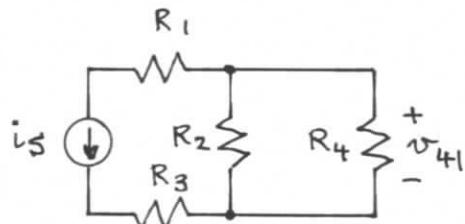case I: i_s on, v_{s1} off (wire), v_{s2} off (wire)




We may combine R_2 and R_4 into an equivalent resistance with v -drop v_{4I} across it. Then we have a resistance

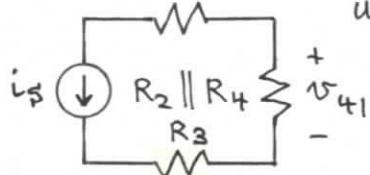R_1 in series with i_s . So we use Ohm's law.



$$v_{4I} = -i_s \frac{R_2 R_4}{R_2 + R_4}$$

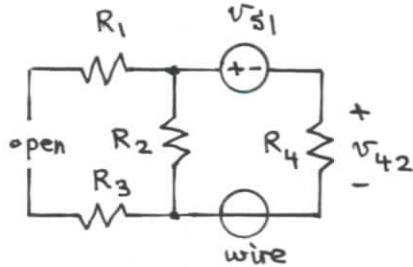
case II: i_S off (open), v_{S1} on, v_{S2} off (wire)



Here, R_1 and R_3 are dangling and may be ignored. That leaves a V -divider.

$$v_{42} = -v_{S1} \frac{R_4}{R_2 + R_4}$$

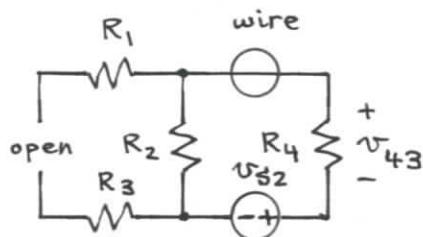case III: i_S off (open), v_{S1} off (wire), v_{S2} on



As in case II, we may ignore R_1 and R_3 , and we have a voltage divider.

$$v_{43} = -v_{S2} \frac{R_4}{R_2 + R_4}$$

We sum our results.

$$v_4 = v_{41} + v_{42} + v_{43} = \frac{-i_S R_2 R_4 - (v_{S1} + v_{S2}) R_4}{R_2 + R_4}$$