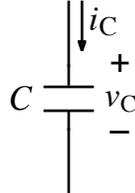




Ex: In (a) and (b), the voltage $v_C(t)$ across a 30 nF capacitor is listed. Find the current, $i_C(t)$, flowing in the capacitor in each case as a function of time:



a) $v_C(t) = 0 \text{ V}$

b) $v_C(t) = 4 \text{ V} + \frac{5 \text{ Vs}}{1s+t}$

SOL'N: We use the defining equation for a capacitor in each case:

$$i_C = C \frac{dv_C}{dt}$$

a)

$$i_C = C \frac{d}{dt} 0 \text{ V} = 0 \text{ A}$$

b)

$$i_C = C \frac{d}{dt} \left(4 \text{ V} + \frac{5 \text{ Vs}}{1s+t} \right) = 30 \text{ nF} \cdot \left[-\frac{5}{(1s+t)^2} \right] \text{ V/s} = -\frac{150}{(1+t/s)^2} \text{ nA}$$