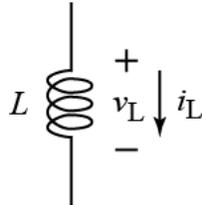


Ex: In (a) and (b), the current $i_L(t)$ flowing into a $20\ \mu\text{H}$ inductor is listed. Find the voltage, $v_L(t)$, across the inductor in each case as a function of time:



- a) $i_L(t) = 5\ \text{mA}$
b) $i_L(t) = 5e^{-t/20\ \text{ms}}\ \text{mA}$

SOL'N: a) The inductor voltage depends on the inductor current:

$$v_L = L \frac{di_L}{dt}.$$

The derivative is zero for a constant current in the inductor. Thus, the voltage is zero.

$$v_L = 20\ \mu\text{H} \frac{d5\ \text{mA}}{dt} = 0\ \text{V}$$

b) Again, we used the derivative formula.

$$v_L = 20\ \mu\text{H} \cdot \frac{d5e^{-t/20\ \text{ms}}\ \text{mA}}{dt}$$

or

$$v_L = 20\ \mu\text{H} \cdot \frac{-1}{20\ \text{ms}} \cdot 5e^{-t/20\ \text{ms}}\ \text{mA}$$

or

$$v_L = -5e^{-t/20\ \text{ms}}\ \mu\text{V}$$