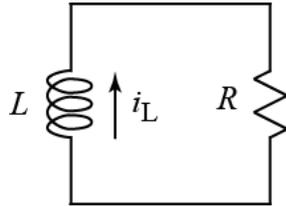


Ex:

- a) Write a differential equation for the above circuit in terms of variable i_L .
Hint: use a v -loop.
- b) Find an expression for the current, $i_L(t)$, through the inductor in the circuit for $t > 0$ if $R = 5 \text{ k}\Omega$, $L = 2 \text{ }\mu\text{H}$, and $i_L(t = 0) = 8 \text{ A}$.

SOL'N: a) The same current flows in both the L and R , and the voltages are the same except for a minus sign (+ sign on top for both v measurements):

$$v_L = L \frac{di_L}{dt} = -i_L R = -v_R$$

The differential equation is the center portion of the equation:

$$L \frac{di_L}{dt} = -i_L R$$

- b) The form of solution is an exponential (or exponentials if the circuit has more than just one L or C) for linear circuits with only R 's, L 's, and C 's. (If there is an independent source in the circuit for all time greater than zero, then the solution is an exponential or exponentials plus a constant.)

$$i_L(t) = A e^{-t/(L/R)}$$

The value of the constant, A , is chosen to match the initial voltage on L , since the exponential has a value of unity at $t = 0$: $e^0 = 1$.

$$i_L(t) = 8 e^{-t/(2\mu\text{H}/5\text{k}\Omega)} \text{ A}$$

or

$$i_L(t) = 8 e^{-t/0.4\text{ns}} \text{ A}$$