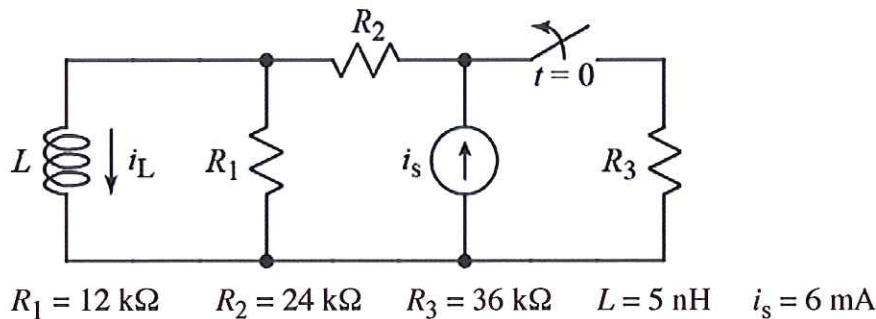



Ex:



After being closed for a long time, the switch opens at $t = 0$.

- Find $i_L(t = 0^+)$.
- Find $i_L(t)$ for $t > 0$.
- Find the time t when $i_L(t) = 4.5 \text{ mA}$.

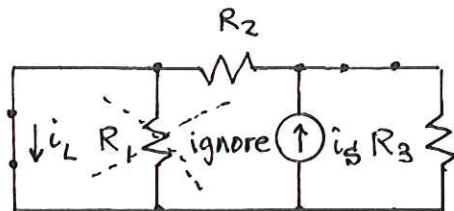sol'n: a) $t = 0^-$: switch is closed, L acts like wire



The wire for L bypasses R_1 with a short circuit, allowing us to ignore R_1 .

We have a current divider.

$$i_L(0^-) \approx i_s \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_3}} = i_s \frac{R_3}{R_2 + R_3}$$

$$i_L(0^-) = 6 \text{ mA} \cdot \frac{36 \text{ k}\Omega}{24 \text{ k}\Omega + 36 \text{ k}\Omega} = 3.6 \text{ mA}$$

b) We use the general form of sol'n:

$$i_L(t>0) = i_L(t \rightarrow \infty) + [i_L(0^+) - i_L(t \rightarrow \infty)] e^{-t/\tau}$$


where $\tau = L/R_{Th}$.

Since i_L is an energy variable, (as in $W_L = \frac{1}{2} L i_L^2$), it cannot change instantly:

$$i_L(0^+) = i_L(0^-) = 3.6 \text{ mA}$$

Now we find the Thevenin equivalent of the circuit as seen by the L and use that to find R_{Th} and $i_L(t \rightarrow \infty) = i_{sc}$ where $i_{sc} \equiv$ short circuit current for the Thevenin equivalent.

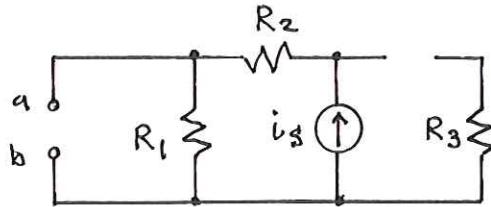Our circuit for which we are looking for the Thevenin equivalent:




The switch is open since $t > 0$.

$$v_{Th} = v_{a,b} = i_s R_1 \text{ since all of } i_s \text{ flows through } R_1.$$


To find R_{Th} , we turn off i_s , which makes it an open circuit. Then we look in from a,b. R_2 and R_3 dangle and may be ignored.

$$R_{Th} = R_1$$
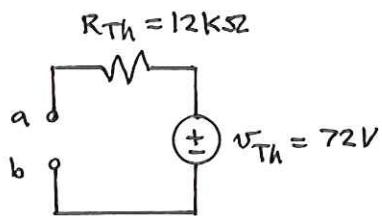
$$\text{Using numbers: } v_{Th} = 6 \text{ mA} \cdot 12 \text{ k}\Omega = 72 \text{ V}, \quad R_{Th} = 12 \text{ k}\Omega$$



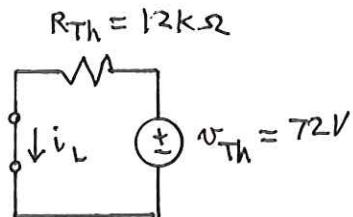If we consider $t \rightarrow \infty$, the L connected across a, b will act like a wire.



$$i_L(t \rightarrow \infty) = v_{Th}/R_{Th} = \frac{72V}{12k\Omega} = 6 \text{ mA}$$

Our time constant is

$$\tau = \frac{L}{R_{Th}} = \frac{5 \text{ nH}}{12k\Omega} \doteq 0.417 \text{ ps}$$

Putting the values into the general solution yields the following answer:

$$i_L(t > 0) = 6 \text{ mA} + (3.6 \text{ mA} - 6 \text{ mA}) e^{-t/0.417 \text{ ps}}$$

or

$$i_L(t > 0) = 6 \text{ mA} - 2.4 \text{ mA} e^{-t/0.417 \text{ ps}}$$

- c) To find the time t when $i_L = 4.5 \text{ mA}$, we use the answer to (b) and isolate the exponential term so we can take the natural log of both sides.

$$4.5 \text{ mA} = 6 \text{ mA} - 2.4 \text{ mA} e^{-t/0.417 \text{ ps}}$$

or

$$4.5 \text{ mA} - 6 \text{ mA} = -2.4 \text{ mA} e^{-t/0.417 \text{ ps}}$$

or

$$-1.5 \text{ mA} = -2.4 \text{ mA} e^{-t/0.417 \text{ ps}}$$

or

$$1.5 \text{ mA} = 2.4 \text{ mA} e^{-t/0.417 \text{ ps}}$$

or

$$\frac{1.5 \text{ mA}}{2.4 \text{ mA}} = e^{-t/0.417 \text{ ps}}$$

or

$$\frac{5}{8} = e^{-t/0.417 \text{ ps}}$$

or

$$\ln\left(\frac{5}{8}\right) = -t/0.417 \text{ ps}$$

or

$$-t = 0.417 \text{ ps} \cdot \ln\left(\frac{5}{8}\right)$$

or

$$t = 0.417 \text{ ps} \cdot \ln\left(\frac{8}{5}\right) = 0.417 \text{ ps} \cdot \ln(1.6)$$

or

$$t \approx 0.196 \text{ ps}$$