
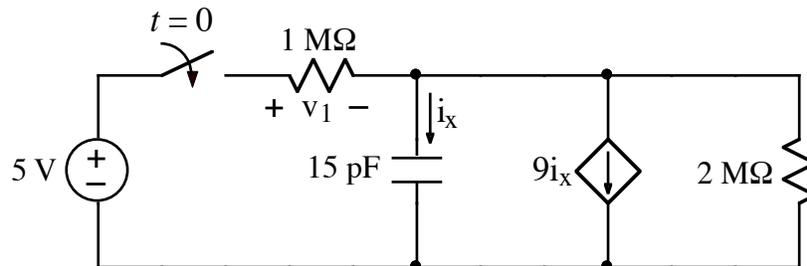


Ex:

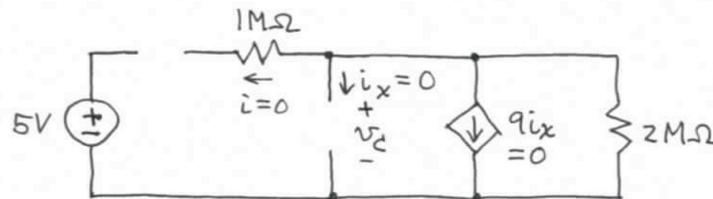

After being open for a long time, the switch closes at  $t = 0$ . Find  $v_1(t)$  for  $t > 0$ .

sol'n:  $t=0^-$  model: (to find  $v_c(0^-)$ )  $C = \text{open circuit}$



The total current flowing out of top node equals zero, and there is no current flowing in the  $1\text{M}\Omega$ , the  $C$ , and the dependent source. It follows that the current in the  $2\text{M}\Omega$  is  $0\text{A}$ . By Ohm's law, the voltage drop across the  $2\text{M}\Omega$  is  $0 \cdot 2\text{M}\Omega = 0\text{V}$ . This is also the voltage across the  $C$ .


$$\therefore v_c(0^-) = 0\text{V}$$

and

$$v_c(0^+) = v_c(0^-) = 0\text{V}$$


We use this value of  $v_c(t=0^+)$  as a voltage source in the  $t=0^+$  model to find  $v_1(0^+)$ .

$t = 0^+$  model:

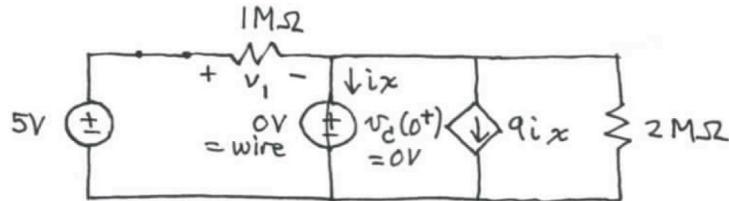

From a voltage loop on the left side, we have  $v_1(0^+) = 5V$ . Note: the components to the right of  $C$  are in parallel with the circuitry on the left and directly across the same voltage source, (namely  $0V$ ).

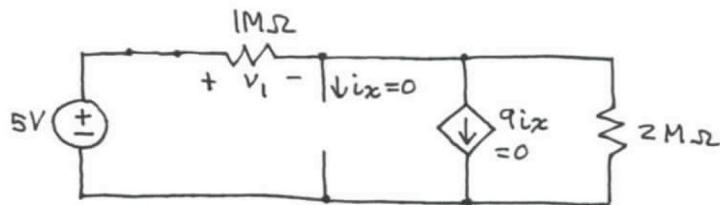
$t \rightarrow \infty$  model: (to find  $v_1(t \rightarrow \infty)$ )  $C = \text{open circ.}$



The dependent src is off and effectively disappears. This leaves a voltage divider:

$$v_1(t \rightarrow \infty) = 5V \cdot \frac{1M\Omega}{1M\Omega + 2M\Omega} = \frac{5}{3}V$$

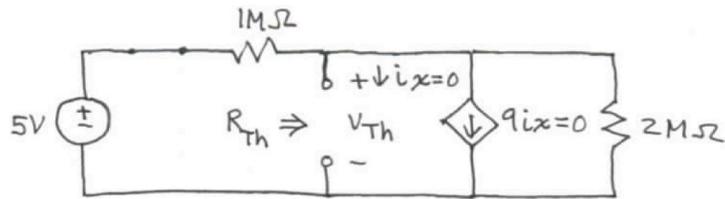
Finally, we have  $\tau = R_{Th}C$  where  $R_{Th}$  is the Thevenin equivalent resistance seen looking into the terminals where  $C$  is connected.



Because there is a dependent source, we find  $R_{Th}$  from  $R_{Th} = \frac{V_{Th}}{i_{sc}}$ .

$V_{Th}$ , as always, equals the voltage across the output terminals when nothing is connected across them. Since  $i_x = 0$  and  $9i_x = 0$ ,  $V_{Th}$  is given by a voltage divider formula:
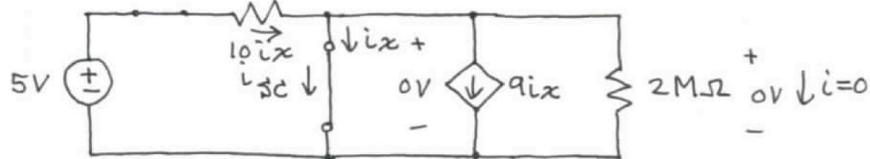
$$V_{Th} = 5V \cdot \frac{2M\Omega}{1M\Omega + 2M\Omega} = \frac{10}{3} V$$



If we short out the output terminals, we have 0V across the  $2M\Omega$  resistor. Thus, there is no current in the  $2M\Omega$  R.

A current summation for the top node reveals that the current in the  $1M\Omega$  must be  $10i_x$ . From a v-loop on the left side, we also have 5V across the  $1M\Omega$  R. Thus, the current in the  $1M\Omega$  R is  $5V/1M\Omega = 5\mu A$ . Thus, we have

$$5\mu A = 10i_x \quad \text{or} \quad i_x = 0.5\mu A$$

From the schematic diagram, we see that

$$i_{sc} = i_x = 0.5 \mu A.$$

$$\therefore R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{\frac{10}{3} V}{0.5 \mu A} = \frac{20}{3} M\Omega$$

$$\text{Thus, } \tau = R_{Th} C = \frac{20}{3} M\Omega \cdot 15 pF = 100 \mu s.$$

Using the general form of solution, we have

$$v_1(t) = v_1(t \rightarrow \infty) + [v_1(t=0^+) - v_1(t \rightarrow \infty)] e^{-t/\tau}$$

$$v_1(t) = \frac{5}{3} V + \left[ 5V - \frac{5}{3} V \right] e^{-t/100 \mu s}, \quad t > 0$$

$$\text{or } v_1(t) = \frac{5}{3} V + \frac{10}{3} V e^{-t/100 \mu s}, \quad t > 0$$

Note: A much simpler way to solve this problem is to observe <sup>that</sup> the dependent source acts like a capacitor that is 9 times  $C$ . Since the  $C$  and  $9C$  are in parallel, we have an equivalent capacitance of  $10C = 10 \cdot 15 pF = 150 pF$ . The dependent source is now gone, and the sol'n is easier to find. The solution, of course is the same as above.  $R_{Th} C$  is the same, but  $R_{Th} = 1M\Omega \parallel 2M\Omega$  and  $C = 150 pF$ .  $v_1(0^+)$  and  $v_1(t \rightarrow \infty)$  are the same as before.