



|           |  |
|-----------|--|
| <b>30</b> | <b>Communication</b>   |
| 4         | Work recorded in notebook (rather than pasted in)                                    |
| 8         | Complete information: task descriptions, diagrams, data, reproducible one year later |
| 4         | Written in Ink   |
| 4         | Student Signed every page  |
| 4         | Student Dated every page   |
| 6         | TA Signature for every lab session (-3 each session missed)                          |

**Lab 1.a****2 IV. CONSTRUCTION OF LED POWER INDICATORS**

- 1 Explanation of task (built power indicators)
- 1 Diagram of circuit from Fig. 3

**8 V. RESISTOR AND LED CURRENTS**

- A. *Measurements of Voltages*
  - 1 Explanation of task (measured voltages for  $R$  and LED)
  - 1 Table II filled in with measured values
- B. *Calculation of Current in Resistor and LED*
  - 1 Explanation of task (Used Ohm's law to calculate  $i_R = i_{LED}$ )
  - 1 Table III filled in with measured values
- C. *Plot of Current versus Voltage in LED*
  - 1 Explanation of task (Commented on plot of LED current versus voltage)
  - 3 Drew accurate plot of LED current vs voltage with all labels

**5 VI. CONSTRUCTION AND TESTING OF PRE-AMPS**

- A. *Construction*
  - 1 Explanation of task (constructed pre-amps circuits on breadboard)
  - 1 Schematic of pre-amps
  - 1 Explanation of testing (1 V 1 kHz sinusoid in, oscilloscope measure output)
- B. *Drawing of Waveforms*
  - 2 Careful drawing of oscilloscope screen

**Lab 1.b****6 V. DEMONSTRATING THE NEED FOR PRE-AMPS**

- B. *Procedure*
  - 1 Explanation of task (measured voltages for electrode model v-divider)
  - 2 Table II-A filled in with measured values
  - 1 Explanation of task (measured voltages for pre-amp model v-divider)
  - 2 Table II-B filled in with measured values

**18 VI. DERIVING AN EXPRESSION FOR THE DIFFERENTIAL AMPLIFIER OUTPUT**

- A. *Deriving the Expression for  $v_3$* 
  - 1 Explanation of task (deriving expression for output of diff-amp)
  - 1 Schematic of differential-amp
  - 12 Derivations:  $v_+$ ,  $v_-$ , and  $v_3$
- B. *Differential Gain*
  - 4 Derivation of  $v_3$  in terms of  $\mathfrak{R}$

**21 VII. DESIGNING, BUILDING, AND TESTING THE DIFFERENTIAL AMPLIFIER**

- A. *Resistor values for a gain of 500*
  - 3 Explanation of how  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$  chosen
  - 2 List of values for  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$
- B. *Building and Testing the Differential Amplifier*
  - 1 Schematic (for circuit in Fig. 6 or for own circuit layout)
  - 1 Explanation of test procedure including 6 V power supply and v-divider
  - 3 Table of values of measured diff-amp output vs input 1 voltage
  - 3 Table of values of measured diff-amp output vs input 2 voltage
- C. *Measuring the Gain of the Differential Amplifier*
  - 3 Plot of  $v_3$  vs  $v_2 - v_1$
  - 3 polyfit() straight line fit of data
  - 2 Calculation of gain of differential amplifier

**10 VIII. MEASURING AND ANALYZING EMG'S**

- A. *Measuring EMG's*
  - 1 Explanation of task (used electrodes on biceps to measure EMG)
  - 4 Printout of EMG waveform on oscilloscope
- B. *Power versus Weight for EMG signals*
  - 1 Explanation of task (Matlab<sup>®</sup> calculation of power in EMG waveform)
- C. *Plot of EMG Power versus Weight*
  - 4 Matlab<sup>®</sup> plot of power vs weight