



30	Communication
–	IEEE single column, double spaced format, title, author, etc. (–20 pts if not used)
5	Style (written in the style of article, rather than disjointed figures and tables)
5	English (grammar, punctuation, and etc.)
5	Clarity (purpose of each section clearly explained)
3	Succinctness and precise wording (detailed information in as few words as possible)
3	Organization (ease of locating figures/code/equations/etc.)
3	Section numbers and headings (use section numbers shown below)
3	Equations explained (at least one sentence between equations)
3	Figures complete (every figure numbered, captioned, and referred to in text)
5	Abstract (succinct summary of results, including numerical values as appropriate)
10	I. INTRODUCTION
8	Motivation/background for lab [create EMG circuit, useful for medical diagnostics]
2	State report organization [briefly describe contents of sections that follow]
10	II. PRE-AMP DESIGN, TEST, AND CONSTRUCTION (Lab 1b Section IV and V)
	A. <i>Electrode model and pre-amp model</i>
1	Introduce section [to demonstrate need for pre-amp to drive diff-amp]
1	Explain model of electrode [small v-source in series with 1 M Ω]
1	Describe why electrode driving diff-amp gives signal out ≈ 0 V [include Fig. 4a]
1	Comment on test results from your Table II [data not required]
	B. <i>Pre-amp model</i>
1	Explain model of pre-amp [small v-source in series with 10 Ω]
1	Describe why pre-amp driving diff-amp gives signal out \approx input [include Fig. 5a]
1	Comment on test results from your Table III [data not required]
1	Comment that pre-amp
	C. <i>Pre-amp circuit</i>
1	Describe pre-amp circuit you built [include Fig. 6b, crop out LED's]
1	Describe results of pre-amp tests in words
25	IV. DIFFERENTIAL AMPLIFIER DESIGN AND TEST (Lab 1b Section VI, VII.A,B)
	A. <i>Analysis of differential amplifier</i>
2	Describe differential amplifier circuit [Lab 1b Fig. 8]
3	Give the formula for v_3 versus v_1 for v_2
3	Give the formula for v_3 written in terms of v_{cm} and v_{dm}
2	Give the formula for v_3 written in terms of $\mathfrak{R}=R_1/R_2=R_3/R_4$
1	Explain that v_3 written in terms of \mathfrak{R} is only a function of v_{dm}
2	Explain why having v_3 be only a function of v_{dm} is desirable
	B. <i>Design of differential amplifier</i>
3	Explain how resistor values were chosen
4	List values of resistors used in diff-amp
	C. <i>Testing of differential amplifier</i>
2	Describe testing procedure [include Lab 1b Fig. 11]
3	Explain calculation of gain of diff-amp [= slope of plot] and list value of gain
15	V. EMG MEASUREMENT (Lab 1b Section VIII)
	A. <i>Measurement of EMG</i>
1	Explain how electrodes and oscilloscope connected for EMG
5	Show plot of EMG from oscilloscope [use Matlab [®] to make plot]
	B. <i>Power vs weight for EMG signal</i>
2	Explain how power for EMG calculated [Lab 1b Eqn (6)]
5	Show plot of power vs weight
2	Comment on plot [describe shape, possible measurement errors]
5	CONCLUSION (summarize key results; include numerical values as appropriate)