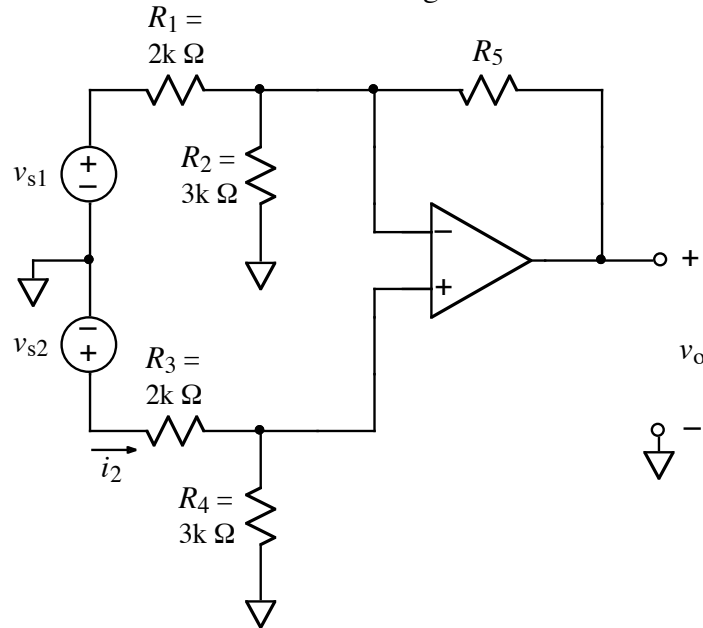


Ex: Find the value of each of the following:



- The above circuit operates in linear mode. Derive a symbolic expression for v_o . The expression must contain not more than the parameters v_{s1} , v_{s2} , R_1 , R_2 , R_3 , R_4 , and R_5 .
- If $v_{s1} = 0$ V and $v_{s2} = 1$ V, find the value of R_5 that will yield an output voltage of $v_o = 1$ V.
- Derive a symbolic expression for v_o in terms of common mode and differential input voltages:

$$v_{cm} \equiv \frac{(v_{s2} + v_{s1})}{2} \quad \text{and} \quad v_{dm} \equiv v_{s2} - v_{s1}$$

The expression must contain not more than the parameters v_{cm} , v_{dm} , R_1 , R_2 , R_3 , R_4 , and R_5 . Write the expression as v_{cm} times a term plus v_{dm} times a term.


Hint: start by writing v_{s1} and v_{s2} in terms of v_{cm} and v_{dm} :

$$v_{s1} = v_{cm} - \frac{v_{dm}}{2} \quad \text{and} \quad v_{s2} = v_{cm} + \frac{v_{dm}}{2}$$


- Find the numerical value of the circuit's input resistance, R_{in} , as seen by source v_{s2} . In other words, write a formula for voltage, v_{s2} , divided by i_2 :

$$R_{in} \equiv \frac{v_{s2}}{i_2}$$

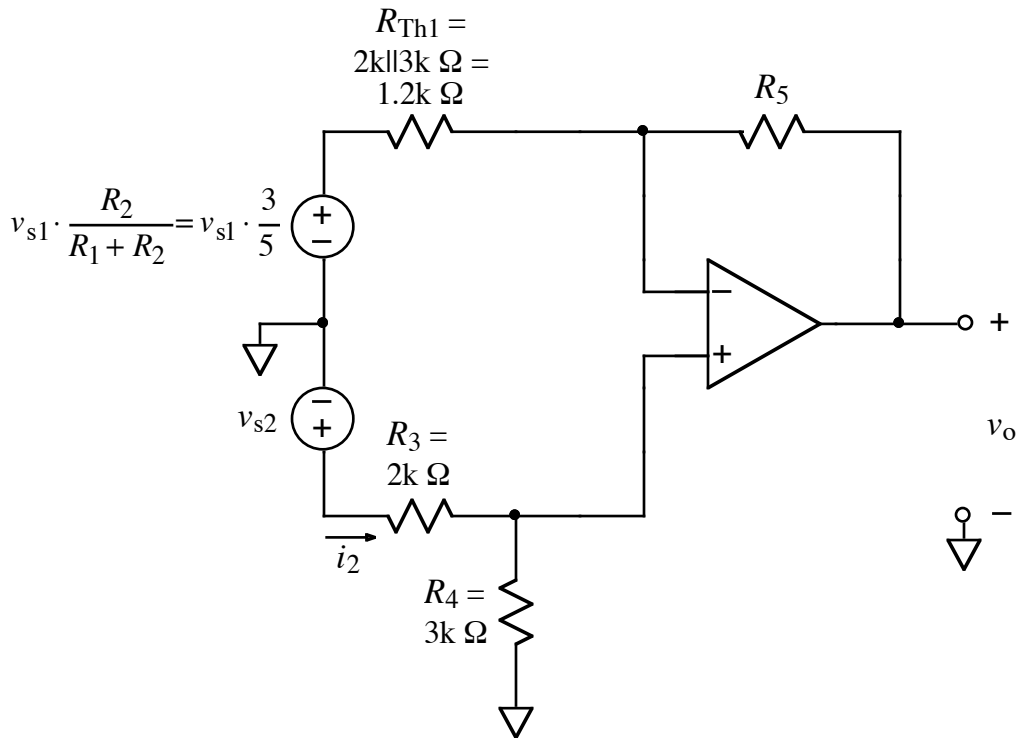
SOL'N: a) Converting the circuitry comprised of v_{s1} , R_1 , and R_2 into a Thevenin equivalent yields a standard differential amplifier.



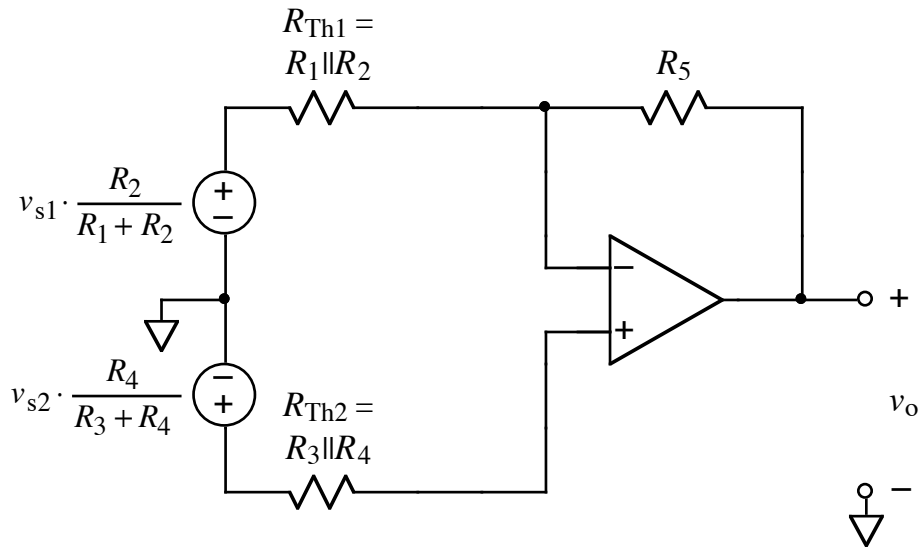Likewise, converting the circuitry comprising v_{s2} , R_3 , and R_4 into a Thevenin equivalent yields further simplification:




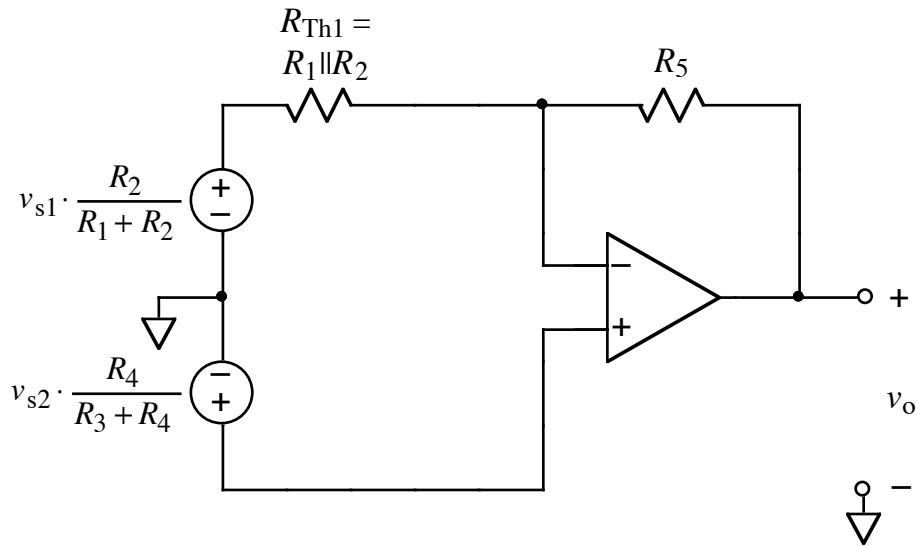Since no current flows into the + input of the op-amp, R_{Th2} has no voltage drop and may be removed.



Now, applying superposition reveals that this circuit is a combination of a standard negative-gain circuit and positive-gain circuit.

case I: (v_{s1} on, v_{s2} off = wire)

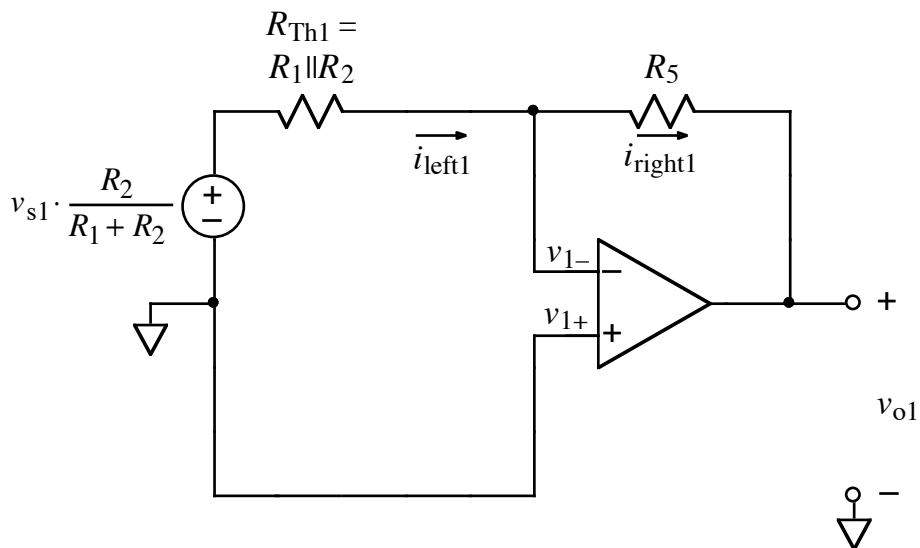


For this circuit, $v_{1-} = v_{1+} = 0$ V. (The "1" stands for "case I".) Using v_{1-} to calculate i_{left1} and i_{right1} gives the following equation:

$$i_{left1} = \frac{v_{s1} \cdot \frac{R_2}{R_1 + R_2}}{R_1 \parallel R_2} = \frac{-v_{o1}}{R_5} = i_{right1}$$

or

$$v_{o1} = -v_{s1} \frac{R_5}{R_1}$$

case II: (v_{s1} off = wire, v_{s2} on)

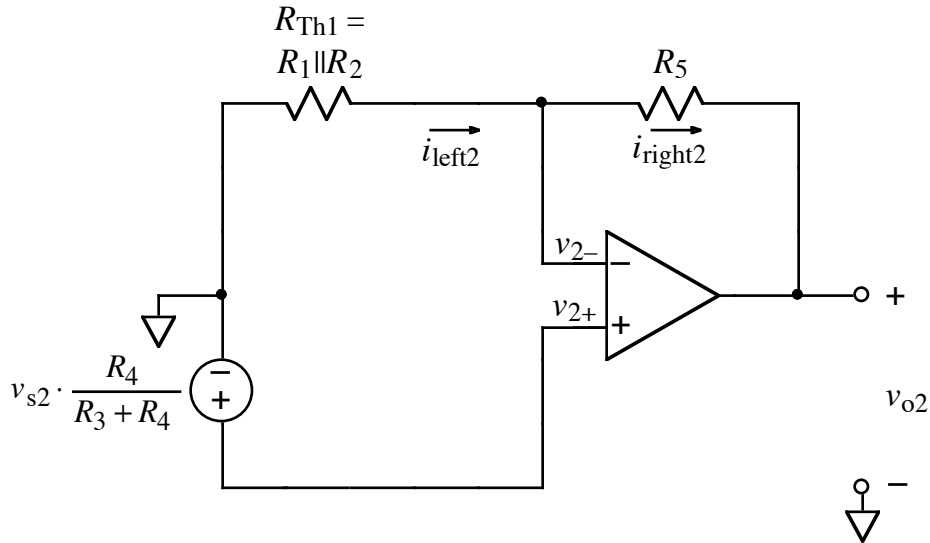

For this circuit, $v_{2-} = v_{2+} = v_{s2} \frac{R_4}{R_3 + R_4}$. (The "2" stands for "case II".)

Using v_{2-} to calculate i_{left2} and i_{right2} gives the following equation:

$$i_{left2} = \frac{v_{s2} \cdot \frac{R_4}{R_3 + R_4}}{R_1 \parallel R_2} = \frac{v_{s2} \cdot \frac{R_4}{R_3 + R_4} - v_{o2}}{R_5} = i_{right2}$$

or

$$v_{o2} = v_{s2} \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_5}{R_1 \parallel R_2} \right)$$

Summing results gives the final result.

$$v_o = -v_{s1} \frac{R_5}{R_1} + v_{s2} \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_5}{R_1 \parallel R_2} \right)$$

Node voltage may also be used. For the v_- node:

$$\frac{v_+}{R_4} + \frac{v_+ - v_{s2}}{R_3} = 0 \text{ A}$$

For the v_+ node:

$$\frac{v_- - v_{s1}}{R_1} + \frac{v_-}{R_2} + \frac{v_- - v_o}{R_5} = 0 \text{ A}$$

Setting $v_- = v_+ = 0 \text{ V}$ and solving for v_o yields the answer obtained earlier.

- b) The conditions match the superposition case II described in (a) but with $v_{s2} = 1 \text{ V}$.

$$v_o = 1 \text{ V} = v_{s2} \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_5}{R_1 \parallel R_2} \right) = 1 \text{ V} \frac{3 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} \left(1 + \frac{R_5}{2 \text{ k}\Omega \parallel 3 \text{ k}\Omega} \right)$$

or

$$1 \text{ V} = 1 \text{ V} \frac{3}{5} \left(1 + \frac{R_5}{1.2 \text{ k}\Omega} \right)$$

or

$$R_5 = 1.2 \text{ k}\Omega \left(\frac{5}{3} - 1 \right) = 1.2 \text{ k}\Omega \cdot \frac{2}{3} = 0.8 \text{ k}\Omega$$

- c) We make the suggested substitutions for v_{s1} and v_{s2} :

$$v_o = - \left(v_{\text{cm}} - \frac{v_{\text{dm}}}{2} \right) \frac{R_5}{R_1} + \left(v_{\text{cm}} + \frac{v_{\text{dm}}}{2} \right) \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_5}{R_1 \parallel R_2} \right)$$

or

$$v_o = v_{\text{cm}} \left[- \frac{R_5}{R_1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_5}{R_1 \parallel R_2} \right) \right] + \frac{v_{\text{dm}}}{2} \left[\frac{R_5}{R_1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_5}{R_1 \parallel R_2} \right) \right]$$

- d)

$$R_{\text{in}} = \frac{v_{s2}}{\frac{v_{s2}}{R_3 + R_4}} = R_3 + R_4 = 2 \text{ k}\Omega + 3 \text{ k}\Omega = 5 \text{ k}\Omega$$