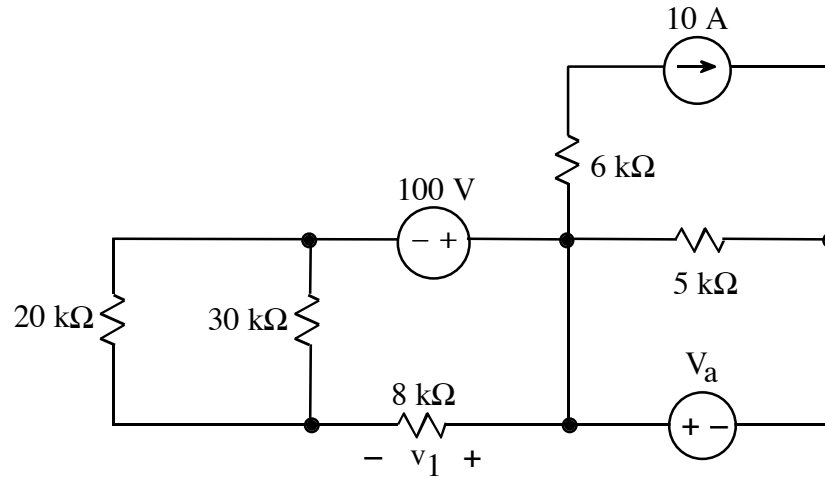





1. a. (5 points)

Calculate v_1 .




b. (5 points)

Calculate i_1 .

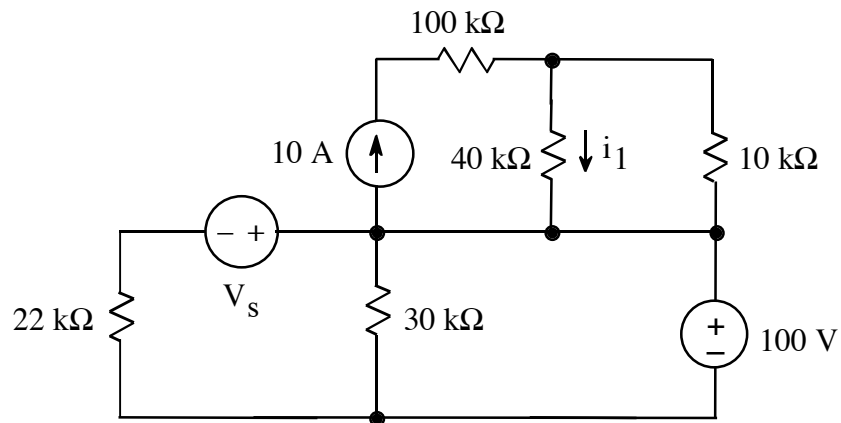


- ans:** a) 40 V
b) 2 A

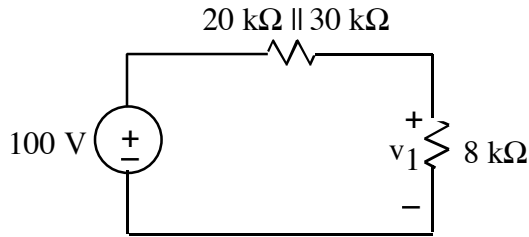sol'n: (a) The 100 V source is directly across $20\text{ k}\Omega \parallel 30\text{ k}\Omega$ in series with $8\text{ k}\Omega$. Thus, the rest of the circuit is irrelevant in the calculation of v_1 .



$$20\text{ k}\Omega \parallel 30\text{ k}\Omega = 10\text{ k}\Omega \cdot 2 \parallel 3 = 10\text{ k}\Omega \cdot \frac{2 \cdot 3}{2 + 3}$$

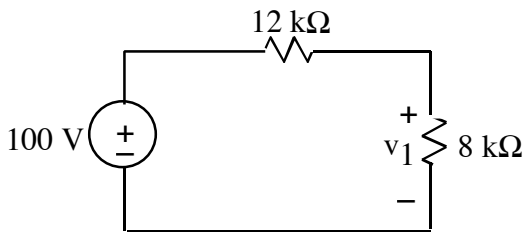
$$= 10\text{ k}\Omega \cdot \frac{6}{5} = 12\text{ k}\Omega$$



Now we have a voltage divider.

$$v_1 = 100\text{ V} \cdot \frac{8\text{ k}\Omega}{12\text{ k}\Omega + 8\text{ k}\Omega} = 40\text{ V}$$

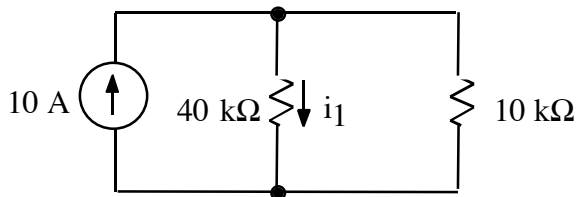(b) The 10 A source current is in series with $40\text{ k}\Omega \parallel 10\text{ k}\Omega$. Thus, all of the 10 A must flow through the $40\text{ k}\Omega \parallel 10\text{ k}\Omega$, and the rest of the circuit is irrelevant in the calculation of i_1 . We use the current divider formula, and we may ignore the $100\text{ k}\Omega$ resistor.



$$i_1 = 10\text{ A} \cdot \frac{10\text{ k}\Omega}{10\text{ k}\Omega + 40\text{ k}\Omega} = 2\text{ A}$$