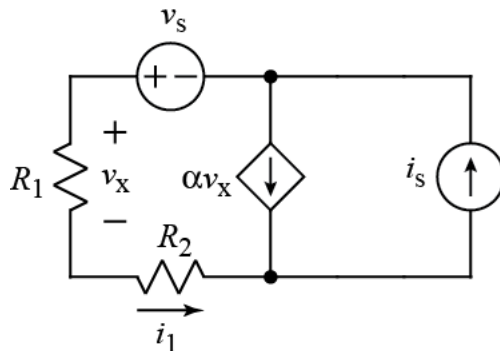



Ex:



Using superposition, derive an expression for i_1 that contains no circuit quantities other than i_s , v_s , R_1 , R_2 , and α . Note: $\alpha > 0$.

sol'n: We turn on one independent source at a time. Dependent sources are always on.

case I: v_s on, i_s off = open

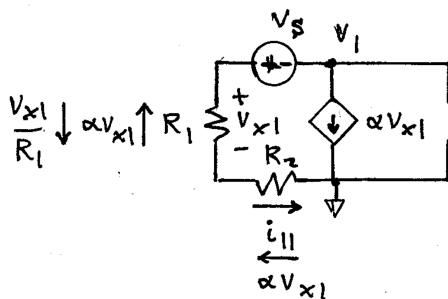

Because of the open circuit, the current αv_{x1} flows thru R_2 and up thru R_1 .

The current flowing down thru R_1 is v_{x1}/R_1 .

$$\frac{v_{x1}}{R_1} = -\alpha v_{x1}$$

The only possible sol'n is $v_{x1} = 0$, $i_{11} = 0A$.

Or we can use the node-voltage method.

$$v_1 \text{ node: } \frac{v_1 + v_s}{R_1 + R_2} + \alpha v_{x1} = 0A$$

$$\text{where } v_{x1} = (v_1 + v_s) \frac{R_1}{R_1 + R_2}$$


$$\text{So } (v_1 + v_s) \left(\frac{1 + \alpha R_1}{R_1 + R_2} \right) = 0A$$

$$\text{Since } \alpha > 0, \frac{1 + \alpha R_1}{R_1 + R_2} \neq 0.$$

$$\text{Thus, } v_1 + v_s = 0V \text{ or } v_1 = -v_s.$$

This means the voltage drop across $R_1 + R_2$ is 0V, giving $i_{11} = 0A$.

case II: v_s off = wire, i_s on

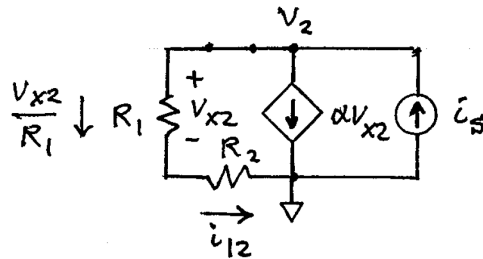

Using the node-voltage method, we have a current sum at v_2 :

$$\frac{v_2}{R_1 + R_2} + \alpha v_2 \frac{R_1}{R_1 + R_2} - i_s = 0A$$

$$\text{or } v_2 \frac{1 + \alpha R_1}{R_1 + R_2} = i_s$$

$$\text{or } v_2 = i_s \frac{R_1 + R_2}{1 + \alpha R_1}$$

$$i_{12} = \frac{V_2}{R_1 + R_2} = \frac{i_s}{1 + \alpha R_1}$$

Or we could use a current sum directly in terms of V_x :

$$i_s = \frac{V_{x2}}{R_1} + \alpha V_{x2} = V_{x2} \left(\frac{1}{R_1} + \alpha \right)$$

or

$$V_{x2} = i_s \frac{R_1}{1 + \alpha R_1}$$

$$i_{12} = \frac{V_{x2}}{R_1} = \frac{i_s}{1 + \alpha R_1}$$

The total i_1 is the sum of i_{11} and i_{12} .

$$i_1 = i_{11} + i_{12} = 0 + i_{12} = \frac{i_s}{1 + \alpha R_1}$$

$$\boxed{i_1 = \frac{i_s}{1 + \alpha R_1}}$$