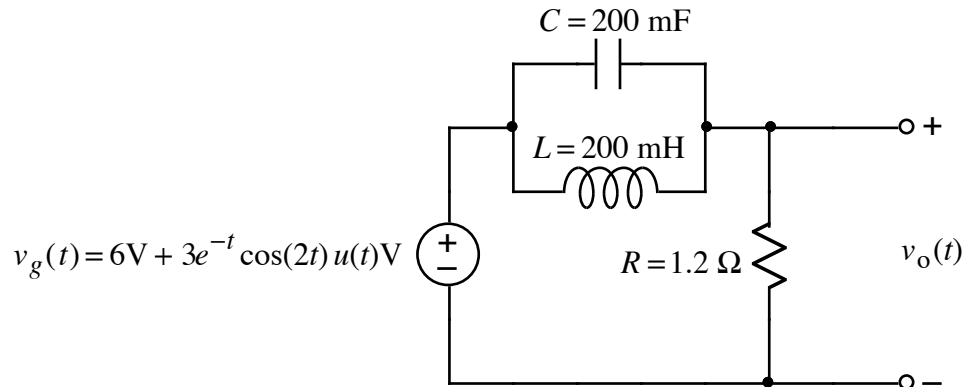


Ex:




**Note:** The 6 V in the  $v_g(t)$  source is always on.

- Write the Laplace transform,  $V_g(s)$ , of  $v_g(t)$ .
- Draw the  $s$ -domain equivalent circuit, including source  $V_g(s)$ , components, initial conditions for  $L$  and/or  $C$ , and terminals for  $V_o(s)$ .
- Write an expression for  $V_o(s)$ .
- Apply the final value theorem to find  $\lim_{t \rightarrow \infty} v_o(t)$ .

**SOL'N:** a) We consider only the value of  $v_g(t)$  for  $t > 0$  when finding the Laplace transform:

$$\mathcal{L}\{v_g(t)\} = \mathcal{L}\{6u(t) + 3e^{-t} \cos(2t)u(t)\}V = \frac{6}{s} + \frac{3(s+1)}{(s+1)^2 + 2^2}V$$

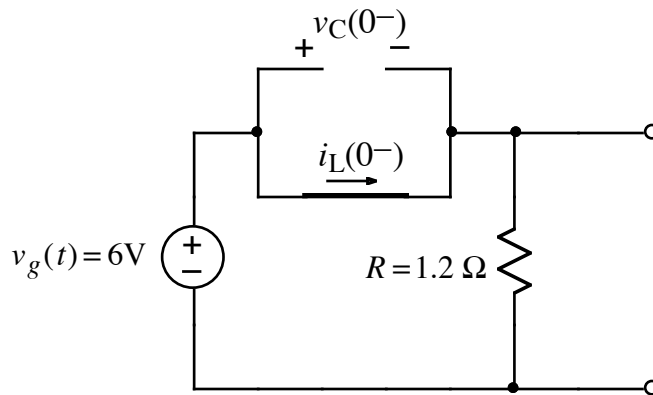- To find initial conditions, we assume that, since the circuit input is a constant 6 V, the circuit has reached a constant state where derivatives of voltages and currents are zero. Thus, we treat inductors as wires and capacitors as open circuits. We then find the energy variables,  $i_L(t)$  and  $v_C(t)$ :




We have the following results:

$$i_L(0^-) = \frac{6\ \text{V}}{1.2\ \Omega} = 5\ \text{A}$$

$$v_C(0^-) = v_L(0^-) = 0\ \text{V}$$

We have a choice of whether to use a current source or a voltage source for the initial conditions on the  $L$ . (We may omit the initial condition source for the  $C$ , since the initial value is zero.) The choice made here is to use a parallel current source. Note that the current source corresponds to a step function in the time domain that produces current  $i_L(0^-)$  in the direction that  $i_L(0^-)$  should flow.

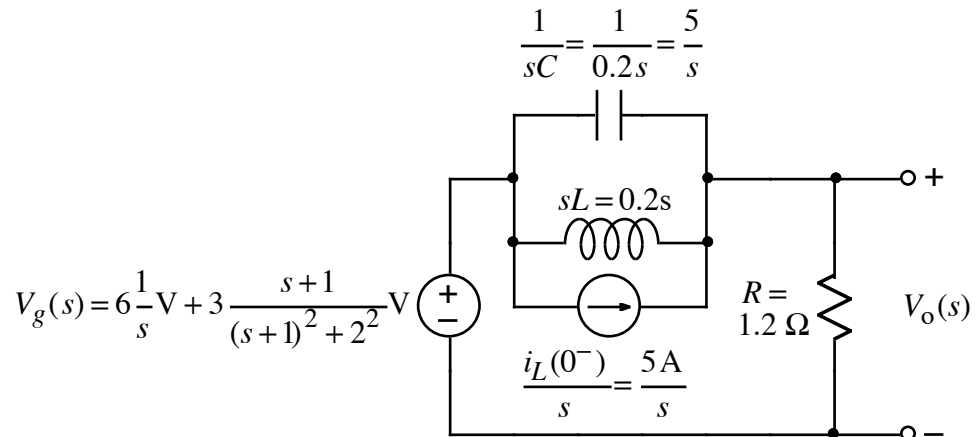

c) Using superposition, we turn on  $V_g(s)$  and then  $i_L(0^-)$  to find the total output signal  $V_o(s)$ :

$$V_o(s) = \left[ \frac{6}{s} + \frac{3(s+1)}{(s+1)^2 + 2^2} \right] \frac{R}{R + \frac{1}{sC} \parallel sL} + \frac{i_L(0^-)}{s} \left[ R \parallel \frac{1}{sC} \parallel sL \right]$$

or

$$V_o(s) = \left[ \frac{6}{s} + \frac{3(s+1)}{(s+1)^2 + 2^2} \right] \frac{1.2}{1.2 + \frac{1}{s0.2} \parallel s0.2} + \frac{5}{s} A \left[ 1.2 \parallel \frac{1}{s0.2} \parallel s0.2 \right]$$

d) The final value theorem statement is as follows:

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} sV_o(s)$$

or, in this case,

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} s \left( \left[ \frac{6}{s} + \frac{3(s+1)}{(s+1)^2 + 2^2} \right] \frac{R}{R + \frac{1}{sC} \parallel sL} + \frac{i_L(0^-)}{s} \left[ R \parallel \frac{1}{sC} \parallel sL \right] \right)$$

Unless we have zero divided by zero, we may evaluate each term as stated. We start by considering the value of the parallel  $L$  and  $C$ .

$$\lim_{s \rightarrow 0} \left( \frac{1}{sC} \parallel sL \right) = \frac{1}{0} \parallel 0 = 0 \text{ (anything in parallel with a short = short)}$$

Similarly, we have the parallel value of the  $R$ ,  $L$ , and  $C$ :

$$\lim_{s \rightarrow 0} \left( R \parallel \frac{1}{sC} \parallel sL \right) = R \parallel 0 = 0$$

Substituting the above results into the final-value-theorem expression yields the following:

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} s \left( \left[ \frac{6}{s} + \frac{3(s+1)}{(s+1)^2 + 2^2} \right] \frac{R}{R+0} + \frac{i_L(0^-)}{s} (0) \right)$$

or

---

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} s \left[ \frac{6}{s} + \frac{3(s+1)}{(s+1)^2 + 2^2} \right]$$

Now we multiply through by  $s$  and cancel factors of  $s^n$  common to numerator and denominator:

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} \left[ \frac{6s}{s} + \frac{s3(s+1)}{(s+1)^2 + 2^2} \right] = \lim_{s \rightarrow 0} \left[ 6 + \frac{s3(s+1)}{(s+1)^2 + 2^2} \right]$$

At this point, we may substitute  $s = 0$  without creating a zero-divided-by-zero problem, and we obtain our result:

$$\lim_{t \rightarrow \infty} v_o(t) = 6 + \frac{0 \cdot 3(0+1)}{(0+1)^2 + 2^2} = 6 \text{ V}$$

This result makes sense, since only the 6V is left in  $v_g(t)$  as time approaches infinity, and the inductor will act as a wire.