

1. Find the value of each of the following:

a) $\left[\frac{\cos(60^\circ)e^{2-j2} \cdot 16}{20} \right]^*$

e) $\mathbf{P}[5\sin(2\pi 100kt - 20^\circ)]$

b) Polar form of $\frac{2 + j1.5}{4e^{j45^\circ}}$

f) $\mathbf{P}^{-1}\left[\frac{5e^{j45^\circ}}{3 + j4} \right]$


c) Rectangular form of $\frac{16e^{j30^\circ}}{4e^{j45^\circ}}$

g) $\left| \frac{3e^{j\frac{\pi}{2}}}{5 - j12} \right|$

d) $\operatorname{Re}\left[\frac{j3(6 - j7)}{e^{j30^\circ}} \right]$

h) Rationalized value of $\frac{5 - j4}{1 - j}$

2.

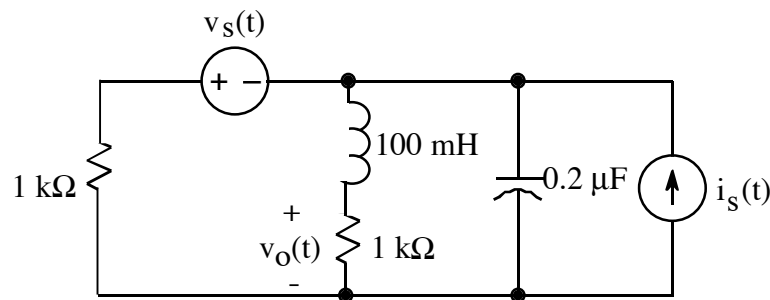


$$v_s(t) = 100 \cos(10^4 t) \text{ V}$$

$$i_s(t) = \sin(10^4 t) \text{ A}$$



- Find a numerical, time-domain expression for $v_o(t)$.
- Show \mathbf{V}_o on a phasor diagram.

3.

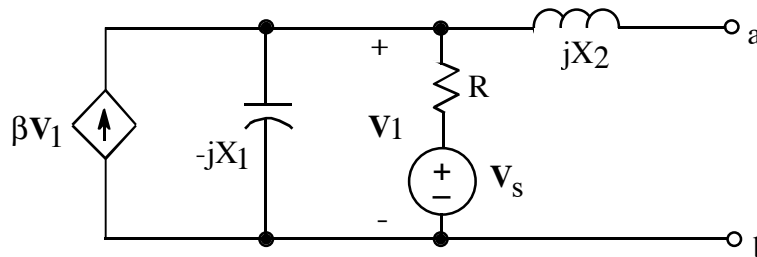

Construct a frequency-domain Thevenin's equivalent circuit at terminals **a** and **b**.

4.

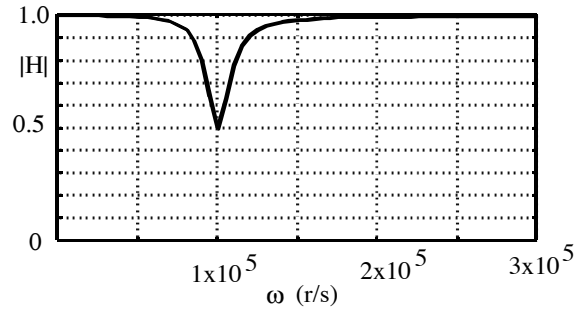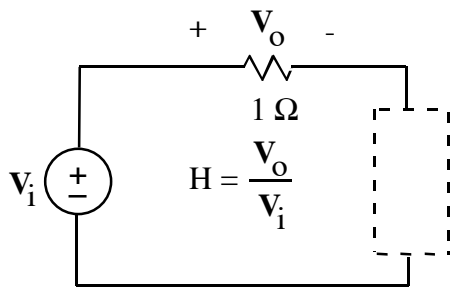

Using not more than one each R, L, and C, design a circuit to go in the dashed-line box that will produce the $|H|$ vs. ω shown above, that is:

$$|H| = 0.5 \text{ at } \omega = 100\text{k r/s}$$

$$|H| = 1 \text{ at } \omega = 0$$

$$|H| \rightarrow 1 \text{ as } \omega \rightarrow \infty$$

Specify values of R, L, and C, and show how they would be connected in the circuit. Note that a bandwidth is not specified, and you do not have to satisfy any more than the three requirements specified above.