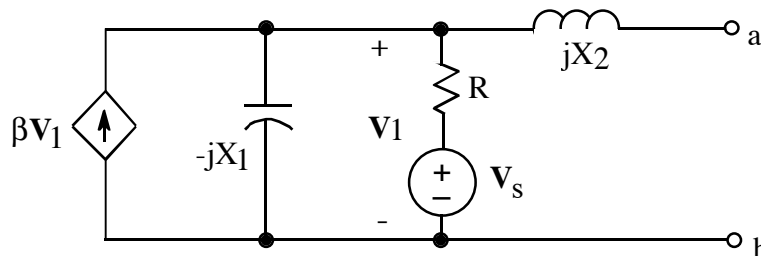


Ex:



Construct a frequency-domain Thevenin's equivalent circuit at terminals a and b.

SOL'N:

$$V_{Th} = \text{open circuit output } V \text{ (phasor)} = V_1 \text{ (since no drop across } jX_2)$$

$$\text{Use Node-V: } \frac{V_1 - V_s}{R} + \frac{V_1}{-jX_1} - \beta V_1 = 0 \text{ A}$$

$$V_1 \left(\frac{1}{R} - \frac{1}{jX_1} - \beta \right) = \frac{V_s}{R}$$

$$V_{Th} = V_1 = V_s \frac{(R \parallel -jX_1 \parallel \frac{1}{-\beta})}{R} \text{ or } V_s \left(1 \parallel \frac{jX_1}{R} \parallel \frac{1}{R\beta} \right)$$

$$Z_{Th} = \frac{140^\circ \text{ V}}{I_a} \text{ with } V_s \text{ set to } 0 \text{ V}$$

$$\text{Use Node-V: } \frac{V_1 - 140^\circ \text{ V}}{jX_2} + \frac{V_1}{R} + \frac{V_1}{-jX_1} - \beta V_1 = 0 \text{ A}$$

$$V_1 \left(\frac{1}{jX_2} + \frac{1}{R} - \frac{1}{jX_1} - \beta \right) = \frac{140^\circ \text{ V}}{jX_2}, \quad -I_a = \frac{V_1 - 140^\circ \text{ V}}{jX_2}$$

$$Z_{Th} = \frac{-jX_2 \cdot 140^\circ \text{ V}}{V_1 - 140^\circ \text{ V}} = -jX_2 \parallel \left(1 \parallel \frac{R}{jX_2} \parallel \frac{-X_1}{X_2} \parallel \frac{-1}{jX_2\beta} \parallel -1 \right)$$