
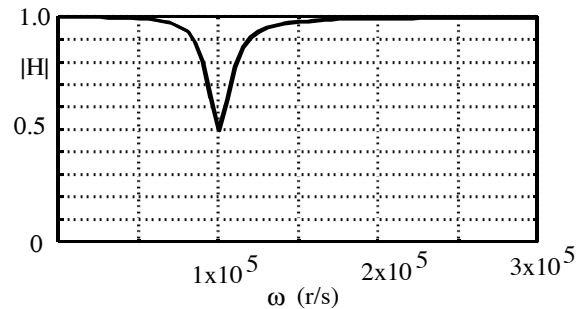


Ex:

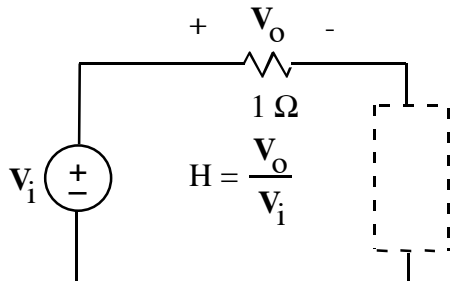

Using not more than one each R, L, and C, design a circuit to go in the dashed-line box that will produce the  $|H|$  vs.  $\omega$  shown above, that is:

$$|H| = 0.5 \text{ at } \omega = 100\text{k r/s}$$

$$|H| = 1 \text{ at } \omega = 0$$

$$|H| \rightarrow 1 \text{ as } \omega \rightarrow \infty$$

Specify values of R, L, and C, and show how they would be connected in the circuit. Note that a bandwidth is not specified, and you do not have to satisfy any more than the three requirements specified above.

**SOL'N:** Given the frequency response plot, we want something resembling a band-reject filter. Since  $V_o$  is measured across  $R_1$ , rather than across the dashed box, we want an L and C configuration that has maximum impedance at resonant frequency. Thus, we need an L in parallel with a C inside the dashed box.

If we denote dashed box by  $z$ , we have

$$V_o = V_i \cdot \frac{R_1}{R_1 + z} \quad (\text{V-divider}). \quad \therefore H(j\omega) \equiv \frac{V_o}{V_i} = \frac{R_1}{R_1 + z}$$

Note that if

$$z = j\omega L \parallel \frac{1}{j\omega C} = \frac{j\omega L}{j\omega L + \frac{1}{j\omega C}} = \frac{L/C}{j\omega L + \frac{1}{j\omega C}}$$

$$\text{then, at } \omega_0, \text{ we have } j\omega L = -\frac{1}{j\omega C}.$$

---


$$\text{So } z = \frac{L/C}{0} \Big|_{\omega=\omega_o} = \infty \text{ at } \omega = \omega_o \equiv \frac{1}{\sqrt{LC}}.$$

$$\text{Thus, } |H(j\omega)| \Big|_{\omega=\omega_o} = \frac{R_1}{R_1 + \infty} = 0.$$

We want a value of 1/2, which we'll correct later on. We do have the desired response at high and low frequencies:

At  $\omega = 0$ ,

$$z = \frac{L/C}{j \cdot 0 \cdot L + \frac{1}{j \cdot 0 \cdot C}} = \frac{L/C}{0 + \infty} = 0.$$

$$\therefore |H(j\omega)| \Big|_{\omega=0} = \left| \frac{R_1}{R_1 + z} \right| = \left| \frac{R_1}{R_1} \right| = 1 \quad \checkmark$$

At  $\omega \rightarrow \infty$ ,

$$z = \frac{L/C}{j \cdot \infty \cdot L + \frac{1}{j \cdot \infty \cdot C}} = \frac{L/C}{j \cdot \infty \cdot L + 0} = 0.$$

The remaining problem is to add an  $R_2$  in the dashed box so that

$|H(j\omega)| \Big|_{\omega=\omega_o} = \frac{1}{2}$  instead of zero. For the parallel L and C, we have

$$|H(j\omega)| = \left| \frac{R_1}{R_1 + R_2} \right| \text{ at } \omega = \omega_o.$$

If we put  $R_2$  in series with the L parallel C, then we would still have  $z = R_2 + \infty = \infty$ , at  $\omega = \omega_o$ . Thus, we must try something else.

If we put  $R_2$  in parallel with L parallel C, then we have  $z = R_2 \parallel \infty = R_2$  at  $\omega = \omega_o$ . This gives

$$|H(j\omega)| = \left| \frac{R_1}{R_1 + R_2} \right| \text{ at } \omega = \omega_o.$$

We use  $R_2 = R_1 = 1\Omega$  to get the required  $|H(j\omega)| = 1/2$  at  $\omega = \omega_o$ .

---

Now we must verify that we have the correct gain at  $\omega = 0$  and  $\omega \rightarrow \infty$ .

For both cases we have

$$j\omega L \parallel 1/j\omega C = 0.$$

The extra  $R_2$  in parallel still gives  $z = 0$ , as desired.

$$\therefore R_2 = 1\Omega.$$

Finally, we need  $\omega_o = 10^5$  rad/s (dip in plot). Since we have L parallel C even with the addition of  $R_2$ , we have the standard resonant frequency:


$$\omega_o = \frac{1}{\sqrt{LC}}.$$

Therefore, we have

$$LC = \frac{1}{\omega_o^2} = \frac{1}{(10^5)^2} = \frac{100}{10^{12}} = 100 \text{ ps}^2.$$

Any  $LC = 100 \text{ ps}^2$  is acceptable unless the L or C are too large or small to be reasonable. For example, one practical solution is
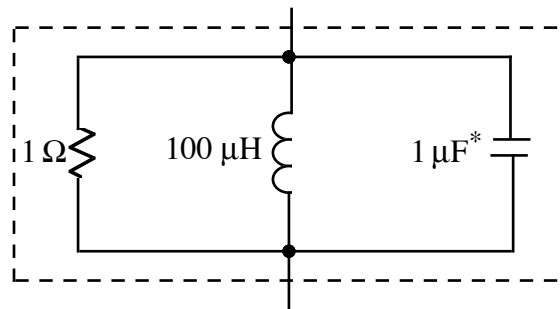
$$C = 1 \mu\text{F} \text{ and } L = 100 \mu\text{H}.$$



\* Any  $LC = 100 \text{ ps}$  is acceptable (if part values are practical).