
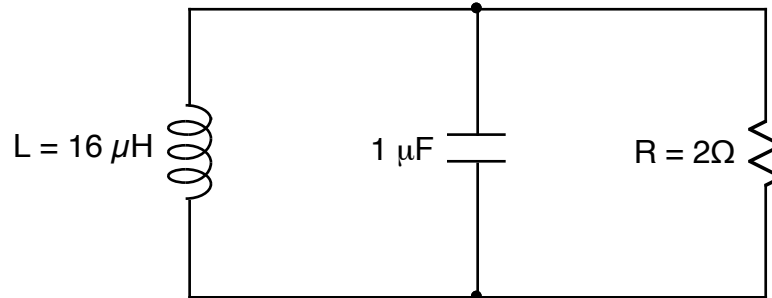


1.

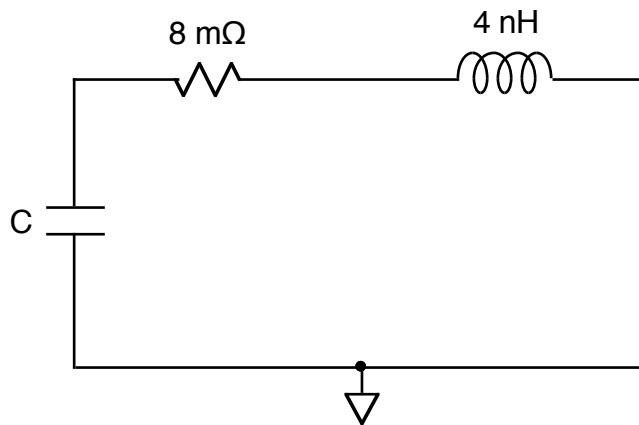

- Find the characteristic roots, s_1 and s_2 , for the above circuit.
- If C is reduced to 100 nF , which will the circuit be: overdamped or underdamped?
- Using the L and C values in the circuit, what value of R yields an underdamped circuit with damping frequency $\omega_d = 150 \text{ k rad/s}$?


2.



An engineer wishes to build a crude TV jammer circuit for Channel 9 using the above schematic. A 4 nH inductor with an internal resistance of $8 \text{ m}\Omega$ is available. (The circuit will be driven by an audio-frequency square-wave generator feeding a diode and resistor in series and connected to the top of the capacitor.) The circuit shown is supposed to produce a signal that oscillates at approximately 189 MHz and decays eventually to zero.

- Find the value of C . Remember to convert Hz to rad/s .
- Find the value of the damping factor, α .

3.

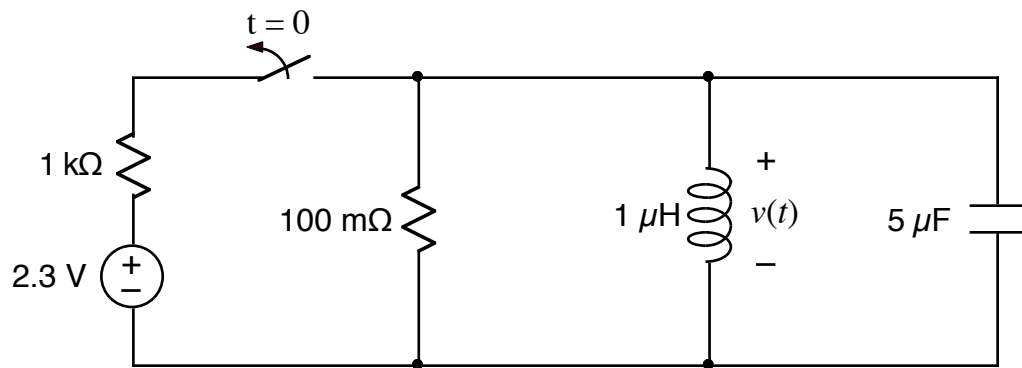

After being closed for a long time, the switch opens at $t = 0$.

Find $v(t)$ for $t > 0$.