
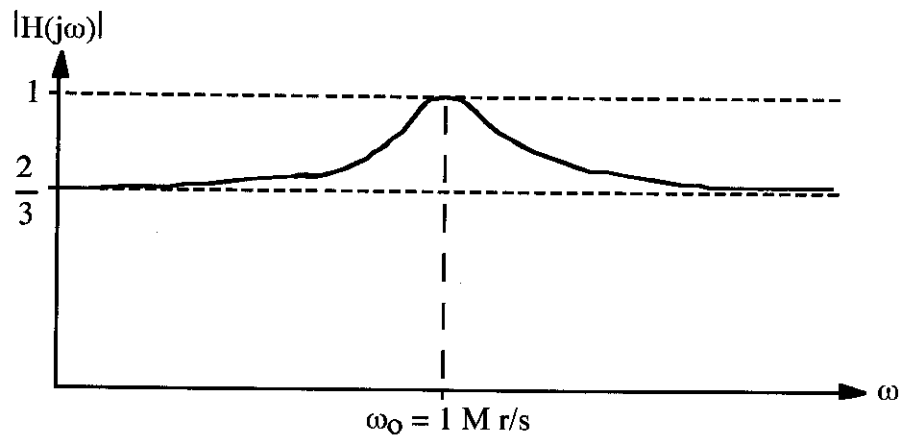


1. (30 points)

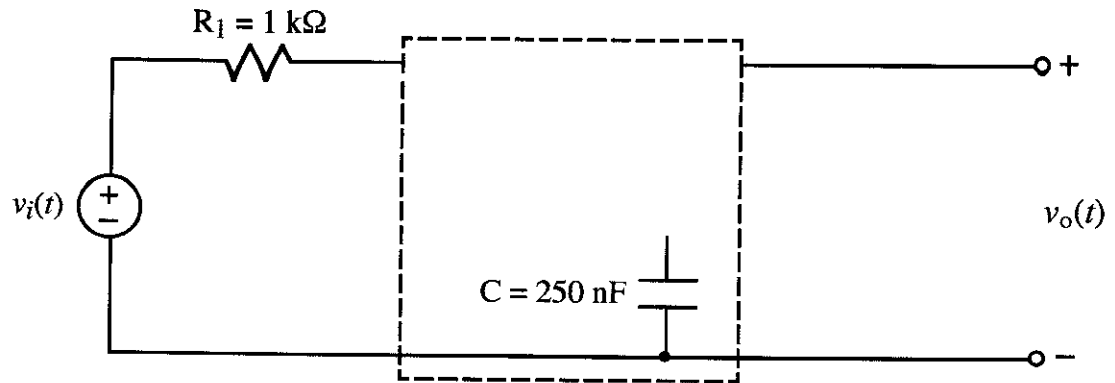

Given the capacitor connected as shown in the box and using not more than one each R and L, design a circuit to go in the dashed-line box that will produce the  $|H(j\omega)|$  vs.  $\omega$  shown above, that is:

$$|H(j\omega)| = \frac{2}{3} \text{ at } \omega = 0$$

$$|H(j\omega)| = 1 \text{ at } \omega_0 = 1 \text{ M rad/s}$$

$$|H(j\omega)| = \frac{2}{3} \text{ as } \omega \rightarrow \infty$$

sol'n: We have a modified band-pass filter.  
 We want higher gain at resonance, implying that we want the components placed between the top and bottom rails to act like an open circuit at frequency  $\omega_0$ .

An L and C in parallel act like an open circuit at frequency  $\omega_0$  where  $\omega_0^2 = 1/LC$ :

$$sL = -\frac{1}{sC} \quad \text{at } \omega_0 \Rightarrow sL \parallel \frac{1}{sC} = \frac{jX(-jX)}{jX-jX} = \frac{X^2}{0} \rightarrow \infty$$

Thus, we must have an L in parallel with the C.

$$\omega_0 = 1M \text{ r/s}, \quad \omega_0^2 = \frac{1}{LC} \quad \text{so } L = \frac{1}{\omega_0^2 C}$$

$$\text{or } L = \frac{1}{(1M)^2 \cdot 250n} \text{ H} = \frac{1}{250k} \text{ H} = \frac{4}{1M} \text{ H} = 4 \mu\text{H}$$

$$\boxed{L = 4 \mu\text{H}}$$

When the L and C become an open circuit at  $\omega_0$ , we want to have a gain of 1. Thus, any R that we add to the circuit must be in series with the LC or in series with  $R_1$ , as placing an R in parallel with L and C would eliminate the open circuit.

Now we consider  $\omega=0$  and  $\omega=\infty$ .

At  $\omega=0$ ,  $L = \text{wire}$  and  $C = \text{open}$ .  $\text{wire} \parallel \text{open} = \text{wire}$ .

At  $\omega \rightarrow \infty$ ,  $L = \text{open}$  and  $C = \text{wire}$ .  $\text{open} \parallel \text{wire} = \text{wire}$ .


So the LC acts like a wire at both extremes.

If we only have a wire across the top and bottom rails, (i.e. across  $v_o$ ), then  $|H| = 0$ .

Since  $|H(j\omega)| = \frac{2}{3}$  at  $\omega = 0$  and  $\omega \rightarrow \infty$ , we

must place an  $R$  in series with the LC to create a voltage divider.

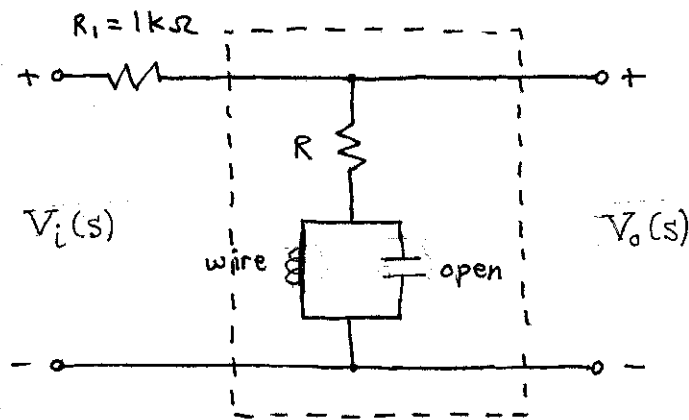At  $\omega = 0$  or  $\omega \rightarrow \infty$  we have the following model:



$$|H(s)| = \left| \frac{V_o(s)}{V_i(s)} \right| = \left| \frac{R}{R + R_1} \right| = \frac{R}{R + R_1} = \frac{2}{3}$$

Solving for  $R$  yields  $R = 2\text{k}\Omega$ .

Contents of box:

