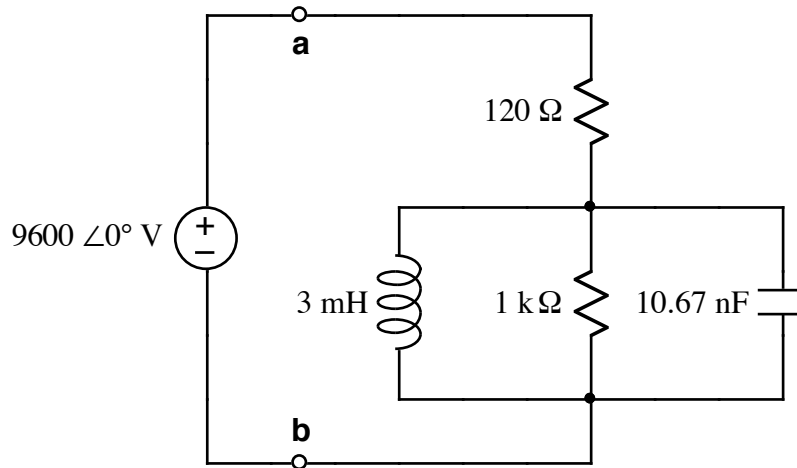


Ex:



Note:  $\omega = 250 \text{ kr/s}$ .

Do the following for the impedance to the right of the a, b terminals:

- Calculate complex power  $S = P + jQ$ .
- Calculate average (or DC) power.
- Calculate maximum instantaneous power.
- Sketch the power waveform,  $p(t)$ .

**SOL'N:** a) The phasor,  $S$ , describes the sinusoidal part of the AC power. By coincidence,  $P$  happens to be both the real part of  $S$  and the value of the average or DC part of the AC power waveform. Thus,  $P$  is referred to as the average, DC, or real power.  $Q$  is the imaginary part of  $S$  and is referred to as the reactive power.

A convenient formula for  $S$  is based on the magnitude of current:

$$S = \frac{1}{2} |\mathbf{I}|^2 z$$

where  $\mathbf{I}$  is the phasor current in the impedance,  $z$ , to the right of the  $a$  and  $b$  terminals.

We calculate  $z$  in the usual way:

$$z = 120 \Omega + 1 \text{ k}\Omega \parallel j\omega \cdot 3 \text{ mH} \parallel \frac{1}{j\omega \cdot 10.67 \text{ nF}}$$

---

or

$$z = 120 \Omega + 1 \text{ k}\Omega \parallel j250 \text{ kr/s} \cdot 3 \text{ mH} \parallel \frac{1}{j250 \text{ kr/s} \cdot 10.67 \text{ nF}}$$

or

$$z = 120 \Omega + 1 \text{ k}\Omega \parallel j750 \Omega \parallel -j375 \Omega$$

or

$$z = 120 \Omega + 1 \text{ k}\Omega \parallel (j375 \Omega \cdot 2 \parallel -1)$$

or

$$z = 120 \Omega + 1 \text{ k}\Omega \parallel -j750 \Omega$$

or

$$z = 120 \Omega + 250 \cdot 4 \parallel -j3$$

or

$$z = 120 \Omega + 250 \cdot \frac{-j12}{4 - j3}$$

or

$$z = 120 \Omega + -j120(4 + j3)$$

or

$$z = 480(1 - j) \Omega$$

Now we use Ohm's Law to find the phasor current:

$$\mathbf{I} = \frac{9600 \angle 0^\circ \text{ V}}{Z} = \frac{9600 \angle 0^\circ \text{ V}}{480(1 - j) \Omega} = \frac{20 \angle 0^\circ \text{ A}}{\sqrt{2} \angle -45^\circ} = \frac{20}{\sqrt{2}} \angle 45^\circ \text{ A}$$

or

$$\mathbf{I} = 14.14 \angle 45^\circ \text{ A}$$

**NOTE:** We actually only need the magnitude of the current, which is somewhat easier to compute. Since we will also be squaring the magnitude, we may omit the calculation involving the square-root of two, as well.

We now calculate  $S$ :

$$S = \frac{1}{2} |I|^2 z = \frac{1}{2} \left( \frac{20}{\sqrt{2}} \right)^2 480(1-j) \text{ VA}$$

or

$$S = 48\text{k}(1-j) \text{ VA} = 48\text{k} - j48\text{k} \text{ VA} = 48\text{k}\sqrt{2}\angle -45^\circ \text{ VA}$$

**NOTE:** We write the units of  $S$  as VA (volt·amps). This is mathematically the same as Watts, but it indicates that the quantity is  $S$  when it appears without being explicitly designated as  $S$ .

b) The average (or DC) power is the same as the real part of  $S$ , as noted above:

$$P = 48 \text{ kW}$$

c) The maximum instantaneous value of  $p(t)$  occurs when the sinusoidal portion of the AC power reaches its peak value. At that point, we have the DC power plus the magnitude of the sinusoid:

$$\max_t p(t) = P + |S| = 48\text{k} + 48\text{k}\sqrt{2} \approx 116 \text{ kW}$$

d) The waveform is the DC power,  $P$ , plus the sinusoid for phasor  $S$  (at frequency  $2\omega$ ):  $p(t) = P + |S|\cos(2\omega t + \angle S)$ .

